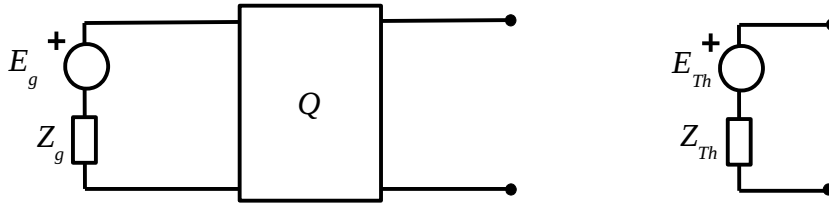


Proposed Exercise



1) Demonstrate that the equivalent Thevenin at the output gate of a two-port network, \mathbf{Q} , connected at the input gate to a real source (E_g, Z_g) is:

$$Z_{Th} = \frac{DZ_g + B}{CZ_g + A},$$

$$E_{Th} = \frac{E_g}{CZ_g + A},$$

where A, B, C, D are the transmission parameters of \mathbf{Q} .

2) If \mathbf{Q} is symmetric, what would be the equivalent Thevenin at the input gate when the real source is connected at the output gate?