

# PROBLEMS OF CHAPTER 1: Transient Circuits.

February 8, 2018

## Problem 1.1

For the circuit in Figure 1 the switch opens at  $t = 0$ . We know that the switch was closed from  $t = -\infty$ . Determine the evolution in time of the voltage of the inductor ( $v_L(t)$ ) as a function of the components ( $E, L, R_1$  and  $R_2$ ).

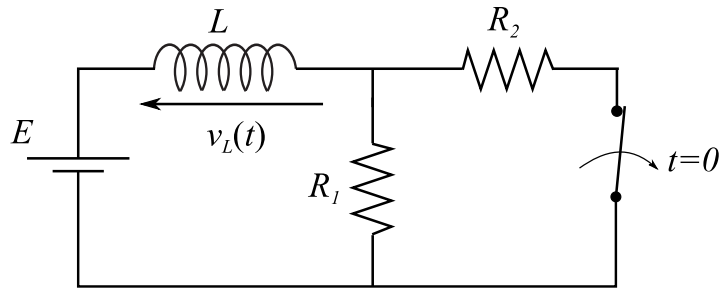


Figure 1

## Result

$$a) v(t) = \begin{cases} 0 & ; t < 0 \\ -\frac{E \cdot R_1}{R_2} \cdot e^{-\frac{R_1}{L}t} & ; t > 0 \end{cases}$$

## Problem 1.2

The circuit in Figure 1 can be used to measure the speed of a bullet. The bullet interrupts the current on the battery, when it breaks the source  $P_1$ . At that moment, the capacitor starts to discharge with  $R$  until the bullet breaks the surface  $P_2$ , at  $t_0$ . At that instant, the discharge process of the capacitor ends. When the bullet breaks  $P_2$  the voltmeter, with an infinite internal resistor, measures 100 V.

Determine:

- Time-domain expression of the voltage of the capacitor since the instant of time that the bullets breaks the surface  $P_1$ , until the bullets destroys the surface  $P_2$ .
- Time-domain expression of the voltage of the capacitor from the instant of time in which the bullets breaks the surface  $P_2$ .

- c) Time in which the bullet travels from  $P_1$  to  $P_2$ .
- d) Speed of the bullet if the distance between  $P_1$  and  $P_2$  is of 6 cm.

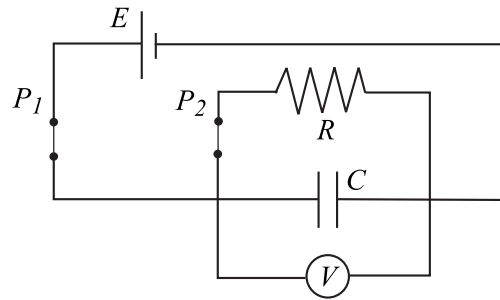


Figure 1

$$\text{Data : } C = 1 \mu\text{F} \ ; \ R = 1 \text{ k}\Omega \ ; \ E = 120 \text{ V}$$

### Result

- a)  $v_C(t) = 120 \cdot e^{-10^3 t} \cdot (u(t) - u(t - t_0)) \text{ V}$
- b)  $v_C(t) = 100 \cdot u(t - t_0) \text{ V}$
- c)  $t_0 = 182,3 \mu\text{s}$
- d)  $v = 1184,7 \text{ km/h}$

### Problem 1.3

In the circuit of the figure 1, the switcher is in position (1) since  $t = -\infty$ . At  $t = 0$ , the switcher changes to position (2) remaining in this position hence forth. Calculate:

- a) Initial conditions of the elements that store energy at the switching instant.
- b) Expression of the Laplace transform of the current  $i(t)$  for  $t > 0$ .
- c) Expression of  $i(t)$  of  $t > 0$ .

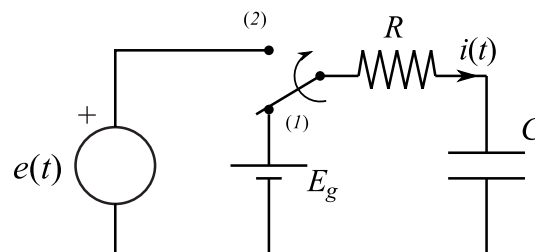


Figure 1

$$\text{Data: } R = 1 \ \Omega; \ C = 1 \ \text{F}; \ e(t) = \cos(t) \ \text{V}; \ E_g = 1 \ \text{V}$$

## Result

a)  $v_C(t = 0^-) = E_g = 1$

b)  $I(s) = -\frac{1}{(s^2 + 1)(s + 1)}$

c)  $i(t) = -\frac{1}{2} \cdot e^{-t} + \frac{1}{\sqrt{2}} \cdot \sin\left(t + \frac{3\pi}{4}\right)$  A ;  $t > 0$

## Problem 1.4

In the circuit of Figure 1, the switch  $S_1$  is in position (1) and the switch  $S_2$  is closed since  $t = -\infty$ . At  $t = 0$  s, the switch  $S_1$  changes to position (2) and the switch  $S_2$  is opened.

- At the switching instant  $t = 0$ , determine the initial conditions of the elements that store energy.
- Compute the Laplace transform of the voltage  $v(t)$  and the current  $i_C(t)$ , for  $t > 0$  s.
- Time-domain expression of the voltage  $v(t)$  for  $t > 0$  s.

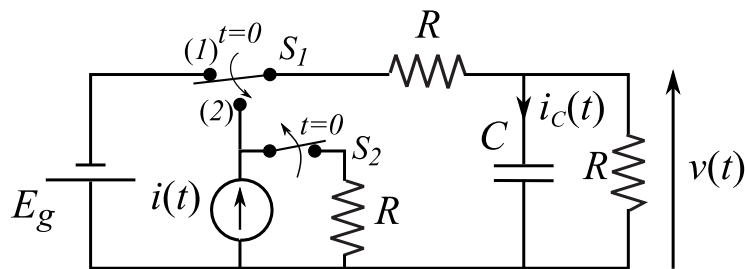


Figure 1

**Data:**  $E_g = 2$  V ;  $i(t) = \sin(t)$  A ;  $R = 1$   $\Omega$  ;  $C = 1$  F

## Result

a)  $v_C(0^-) = -1$  V

b)  $V(s) = -\frac{s^2}{(s^2 + 1) \cdot (s + 1)}$ ;  $I_C(s) = \frac{s^2 + s + 1}{(s^2 + 1) \cdot (s + 1)}$

c)  $v(t) = -\frac{e^{-t}}{2} - \frac{1}{\sqrt{2}} \cdot \sin\left(t + \frac{3\pi}{4}\right) = \frac{1}{\sqrt{2}} \cdot \sin\left(t - \frac{\pi}{4}\right) - \frac{e^{-t}}{2}$  V

## Problem 1.5

For the circuit in Figure 1, the switch  $S_1$  is open and the switch  $S_2$  is in position (2) since  $t = -\infty$ . At  $t = 0$  s switch  $S_1$  is closed and switch  $S_2$  commutes to position (1). At  $t = \frac{1}{2}$  s switch  $S_2$  commutes to position (2). With these conditions:

- a) Determine the temporal evolution of voltage  $v(t)$  from  $t = 0$  s to  $t = \frac{1}{2}$  s.
- b) Compute the temporal evolution of voltage  $v(t)$  once the switch  $S_2$  is open.

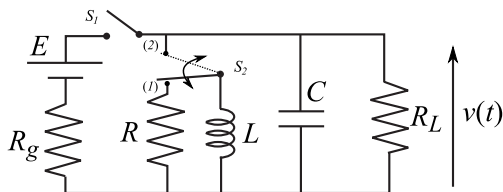



Figure 1

$$\text{Data: } L = 1 \text{ H} \quad ; \quad C = \frac{1}{4} \text{ F} \quad ; \quad R_g = R_L = 2 \Omega \quad ; \quad E = 1 \text{ V}$$

### Result

a)  $v(t) = 2t \cdot e^{-2t} \cdot (u(t) - u(t - \frac{1}{2}))$

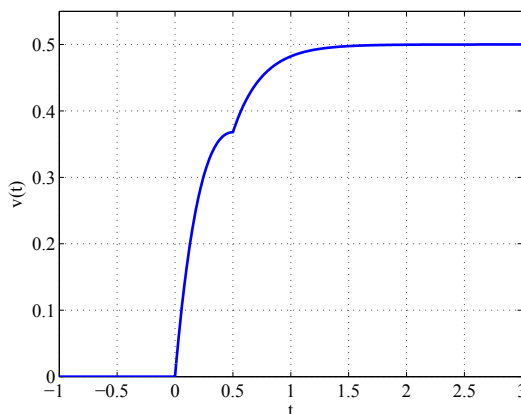b)  $v(t) = \left[ \frac{1}{2} - \left( \frac{1}{2} - \frac{1}{e} \right) \cdot e^{-4 \cdot (t - \frac{1}{2})} \right] \cdot u(t - \frac{1}{2})$



### Problem 1.6

For the  $RLC$  circuit shown in Figure 1 (a) we know that it contains with one resistor, one inductor and one capacitor. We know as well that the switch is position (1) since  $t = -\infty$ , and that the switch commutes to position (2) at  $t = 0$ . The response of the circuit, for  $v(t)$ , is shown in Figure 1 (b). Obtain one possible internal structure for the circuit.


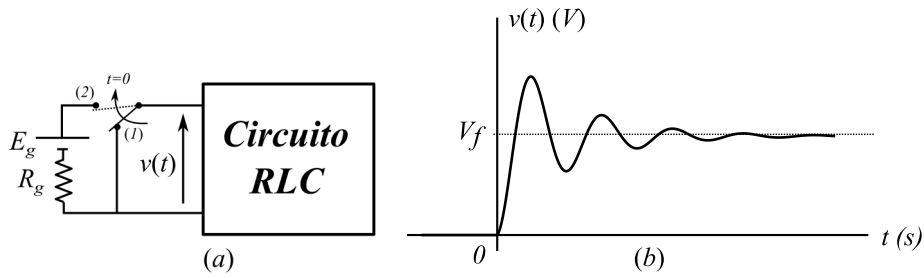


Figure 1

## Result

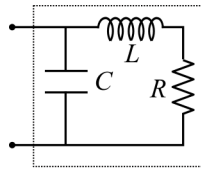

## Problem 1.7

For the circuit of the Figure 1 the switch is closed. If we open the switch at  $t = 0$  s, determine:

- Current in the inductor  $i_L(t)$  and the voltage of the capacitor,  $v_C(t)$ , just before we open the switch.
- Laplace's transform expression of  $v_C(t)$  for  $t > 0$  s.
- Undamped natural frequency,  $\omega_n$ , and damping coefficient,  $\xi$ , of the second order system. Justify the type of damping of the circuit.
- Time-domain expression of the voltage in the capacitor,  $v_C(t)$ , for  $t > 0$  s.

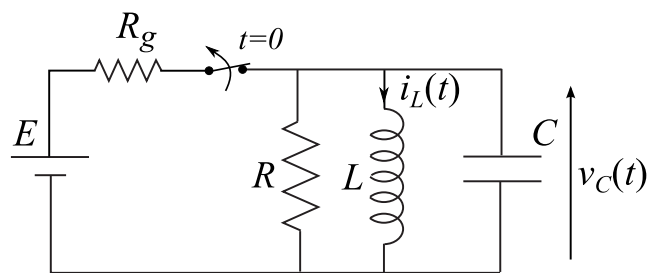


Figure 1

$$\text{Data: } E = 1 \text{ V} ; C = 1 \text{ F} ; L = 1 \text{ H} ; R_g = 1 \Omega ; R = 1 \Omega$$


## Result

- $I_L(0^-) = 1 \text{ A} ; V_C(0^-) = 0 \text{ V}$

$$b) V_C(s) = \frac{-1}{\left(s + \frac{1}{2}\right)^2 + \frac{3}{4}}$$

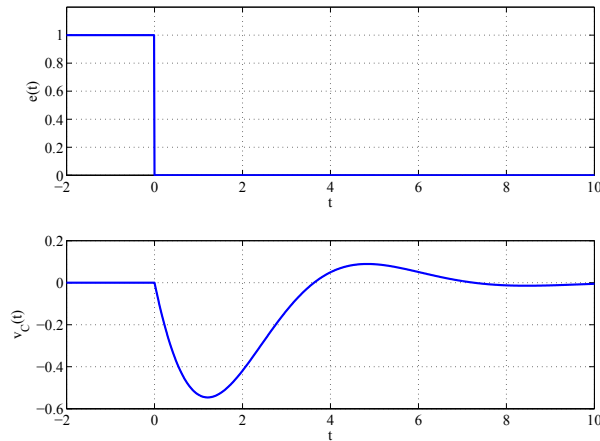c)  $\omega_n = 1 \text{ rad/s}$  ;  $\xi = \frac{1}{2}$  ; Underdamped system

$$d) v_C(t) = \frac{2}{\sqrt{3}} \cdot e^{-\frac{t}{2}} \cdot \sin\left(\frac{\sqrt{3}}{2}t + \pi\right) \cdot u(t) \text{ V}$$



## Problem 1.8

For the circuit of the Figure 1, the switch is in the position (1). At  $t_0 = \frac{\pi}{4} \text{ s}$  the switch commutes to position (2):

- Obtain the current of the inductor  $i_L(t)$ , for  $t \geq t_0$
- Determine the value of the resistor  $R$ , if  $L$  and  $C$  do not change, so as to have a critically damped current  $i_L(t)$ .

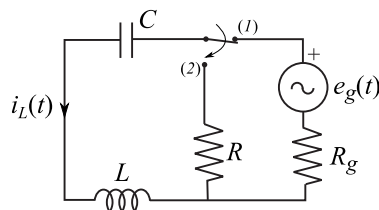



Figure 1

$$Data : e_g(t) = 4 \cdot \sin(t) \text{ V} ; L = 2 \text{ H} ; C = \frac{1}{4} \text{ F} ; R_g = 2 \Omega ; R = 4 \Omega$$

## Result

$$a) i_L(t) = 2 \cdot e^{-(t-\frac{\pi}{4})} \cdot \sin\left(t + \frac{\pi}{2}\right) \cdot u\left(t - \frac{\pi}{4}\right)$$

$$b) R = 4\sqrt{2} \Omega$$

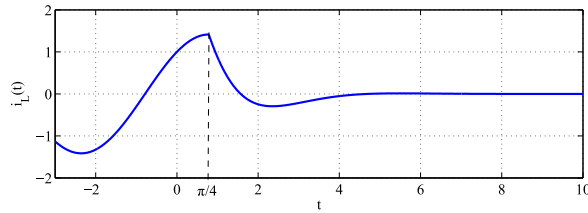

## Problem 1.9

For the circuit shown in Figure 1, the switch  $I_1$  is in position since  $t = -\infty$  s. At  $t = 0$  s, this switch commutes to position 2. Switch  $I_2$  is open until the instant of time  $t = t_1$  s, when the voltage of the capacitor is of 30 V. At this instant of time,  $t_1$ , switch  $I_2$  is closed.

- Determine this instant of time  $t_1$  for which the voltage in the capacitor reaches the value of 30 V.
- Finde the time-domain expression of the current  $i_L(t)$  for  $t > t_1$ .

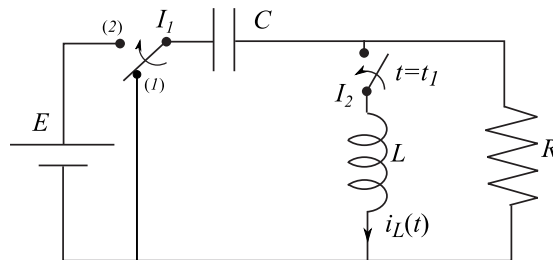



Figure 1

$$\text{Data : } R = 8 \Omega \quad ; \quad E = 40 \text{ V} \quad ; \quad L = 4 \text{ H} \quad ; \quad C = \frac{1}{8} \text{ F}$$
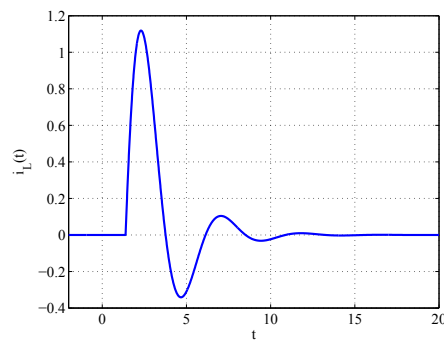
## Result

$$\text{a) } t_1 = Ln(4)$$

$$\text{b) } i_L(t) = \frac{5}{\sqrt{7}} \cdot e^{-\frac{t-t_1}{2}} \cdot \sin\left(\frac{\sqrt{7}}{2}(t-t_1)\right) \cdot u(t-t_1) \text{ A}$$



## Problem 1.10

For the circuit of the Figure 1 the switch is open from  $t = -\infty$  s. At  $t = 0$ , the switch is closed. Determine:

- Value of the current in the inductor,  $i_L(t)$ , and the voltage of the capacitor,  $v_C(t)$ , for the instant  $t = 0^-$ . Value of the current of the capacitor and the voltage of the inductor for  $t = 0^+$ .
- Proof that the Laplace's transform expression of the voltage of the capacitor is given by:

$$V_C(s) = \frac{\frac{5}{s} + 5(R_1 + s)}{s^2 + \frac{2R_1+1}{2}s + \frac{R_1+2}{2}}$$

- Value of  $R_1$  in order to have an undamped natural frequency of  $\sqrt{2}$  rad/s, and the value for the damping coefficient.

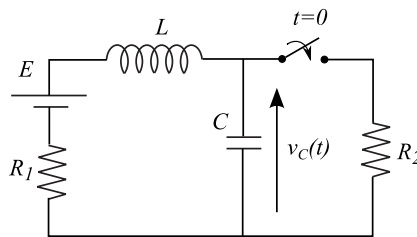


Figure 1

$$\text{Data : } E = 5 \text{ V} ; L = 1 \text{ H} ; C = 1 \text{ F} ; R_2 = 2 \Omega$$

### Result

$$\text{a) } \begin{cases} I_L(0^-) = 0 \\ V_C(0^-) = E = 5 \text{ V} \\ V_L(0^+) = 0 \\ I_C(0^+) = \frac{5}{2} \text{ A} \end{cases}$$

b) It is correct

c)  $R_1 = 2 \Omega$  ;  $\xi = \frac{5\sqrt{2}}{8} < 1$  Under damped.

## Problem 1.11

For the circuit of the Figure 1 the switch is closed from  $t = -\infty$  s. At  $t = 0$  s. the switch is open, remaining on this state indefinitely. Determine:

- Initial conditions of the elements of the circuit able to save energy.
- Expression of  $I_L(s)$  as a function of  $R_2$  for  $t > 0$ .
- Value of  $R_2$  in order to obtain a damping coefficient of  $\xi = \frac{3}{4}$ .



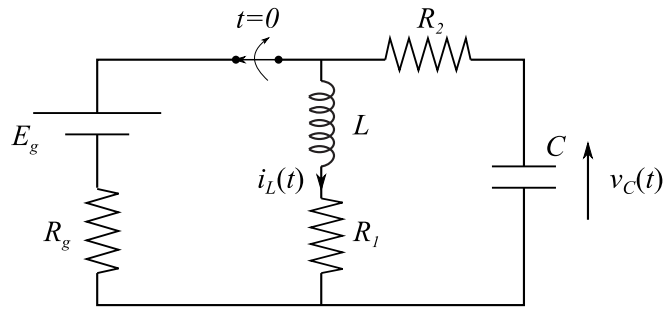


Figure 1

Data:  $E_g = 5 \text{ V}$ ;  $R_g = 2\Omega$ ;  $R_1 = 3\Omega$ ;  $C = 0.1 \text{ F}$ ;  $L = 10 \text{ H}$ .

### Result

a)  $I_L(0^-) = 1 \text{ A}$ ,  $V_C(0^-) = 3 \text{ V}$ .

b) 
$$I_L(s) = \frac{s + \frac{3}{10}}{s^2 + \frac{3 + R_2}{10}s + 1}$$

c)  $R_2 = 12 \Omega$ .

### Problem 1.12

For the circuit of the Figure 1, at  $t = 0 \text{ s}$  the capacitor has a voltage of  $v(t = 0) = 5 \text{ V}$ . At  $t = t_0$ , when this voltage is  $v(t = t_0) = 3 \text{ V}$ , the switch is closed, remaining in this new position indefinitely.

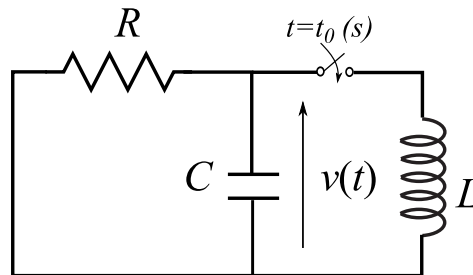


Figure 1

Data:  $R = 0,5\Omega$ ;  $C = 1\text{F}$ ;  $L = 0,5\text{H}$

Determine:

- The expression of  $v(t)$  for  $0 \leq t \leq t_0$  seg. Value of  $t_0$ .
- The expression of  $v(t)$  for  $t \geq t_0$  seg.
- The undamped natural frequency and the damping coefficient once the switch is closed. What is the type of damping of the circuit, according to the damping coefficient?

## Result

- a)  $v(t) = 5 \cdot e^{-2t} \quad 0 \leq t \leq t_0, t_0 = 0.2554 \text{ s.}$
- b)  $v(t) = 3\sqrt{2} \cdot e^{-(t-t_0)} \cdot \sin\left(t - t_0 + \frac{3\pi}{4}\right) \quad t > t_0.$
- c) Underdamped.  $\omega_n = \sqrt{2} \text{ rad/s}, \xi = \frac{1}{\sqrt{2}} < 1.$

## Problem 1.13

In the circuit of the figure 1, where the current generator is a continuous source, the switcher is in position (1) since  $t = -\infty$ . At  $t = 0$ , the switcher changes to position (2), remaining in this position. Knowing that the voltage at the capacitor and the current through the inductor at  $t = 0^-$  are respectively  $V_C(0^-) = 10 \text{ V}$  and  $I_L(0^-) = 5 \text{ A}$ . Calculate:

- a) Values of  $I_g, R_g$  y  $R$  so that the initial conditions are fulfilled.

Supposing for the next section that  $R = 2 \Omega$ ,

- b) Obtain the temporal expression for the voltage at the capacitor  $v_C(t)$  for  $t > 0$ , indicating the type of circuit according to the damping ratio.
- c) At  $t = t_1$ , when the voltage at the capacitor reaches the value of  $2 \text{ V}$ , the value of  $R$  is duplicated. Obtain the new value of the damping ratio and the corresponding type of circuit for  $t > t_1$ .

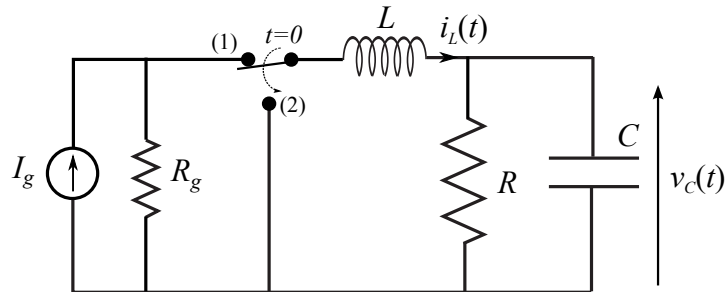


Figure 1

Data:

$$R_g = R; \quad L = 8 \text{ H}; \quad C = \frac{1}{2} \text{ F}$$

## Result

- a)  $\begin{cases} R = R_g = 2 \Omega \\ I_g = 10 \text{ AV} \end{cases}$
- b)  $v_C(t) = (5t + 10) \cdot e^{-\frac{t}{2}}; \quad t > 0, \text{ Circuit critically damped.}$
- c) Under damped circuit with  $\xi = \frac{1}{2}$  y  $\omega_n = \frac{1}{2} \text{ rad/s}$

### Problem 1.14

For the circuit of the Figure 1 the switch is in position (1) from  $t = -\infty$  s. At  $t = 0$  s, the switch is in position (2). Compute the time-domain expression of the current  $i_L(t)$  for  $t > 0$  s


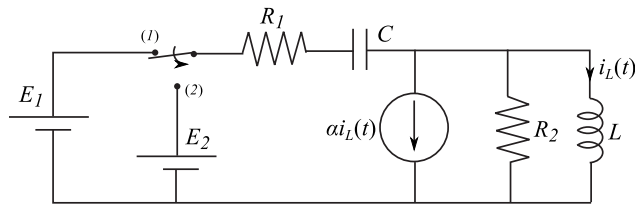


Figure 1

Data :  $L = 2 H$  ;  $C = 1 F$  ;  $\alpha = 1$  ;  $R_1 = R_2 = 1 \Omega$  ;  $E_1 = 5 V$   
 $E_2 = 10 V$
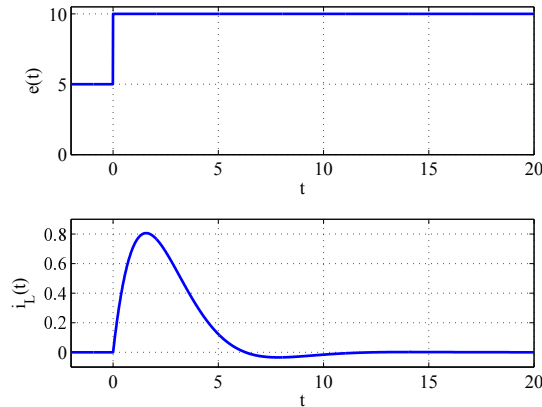
### Result

$$i_L(t) = \frac{5}{2} \cdot e^{-\frac{t}{2}} \cdot \sin\left(\frac{t}{2}\right)$$



### Problem 1.15

For the circuit of the Figure 1, the switch is in the position (1). At  $t = 0$  s the switch commutes to position (2), remaining in this position. Determine the expression of  $v_C(t)$  for all  $t$ .


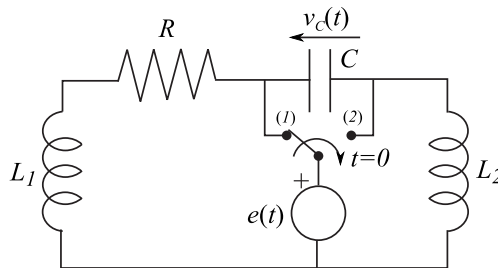


Figure 1

Data :  $L_1 = 1 H$  ;  $L_2 = 3 H$  ;  $C = \frac{1}{2} F$  ;  $R = 2 \Omega$  ;  $e(t) = 10 \cdot \sin(2t) V$
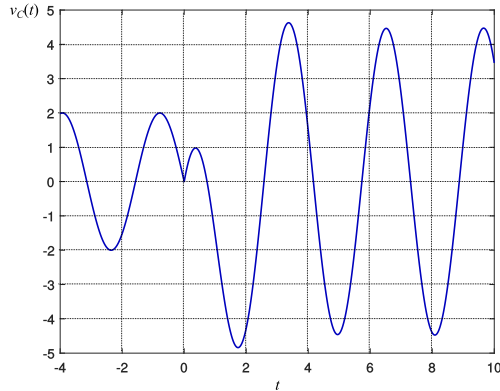
## Result

$$v_C(t) = \begin{cases} 2 \cdot \text{sen}(2t + \pi) \text{ V} & t < 0 \\ 4 \left( \frac{\sqrt{5}}{2} \cdot \text{sen}(2t + 1.107) - \frac{5}{4} \cdot e^{-t} \cdot \text{sen}(t + 0.927) \right) \text{ V} & t > 0 \end{cases}$$



## Problem 1.16

For the circuit of the Figure 1(a) the switches  $S_1$  and  $S_2$  are in position (1) from  $t = -\infty$  s. At  $t = 0$  s the switch  $S_1$  commutes to position (2) remaining the switch ( $S_2$ ) at position (1). Under these conditions we observe that the current in the inductor is the one shown in the Figure 1(b). Determine:

- Value of the voltage of the source  $E_0$  and of  $L$ .
- Time-domain expression of the current in the inductor,  $i_L(t)$ , assuming that  $L$  is real, with internal resistor  $r = 8 \Omega$ . Indicate the type of damping of the circuit, and the damping coefficient.
- Given the conditions of the previous section (real inductor  $L$ ), at  $t_0$  the switch  $S_2$  commutes to position (2), while switch  $S_1$  remains at position (2). Assuming that at  $t_0^-$  the circuit has reaches the steady-state, obtain the time-domain expression of the current in the inductor,  $i_L(t)$ , for  $t > t_0$ .
- Compute the value of the current in the inductor passed 5 s since  $t = t_0$ .

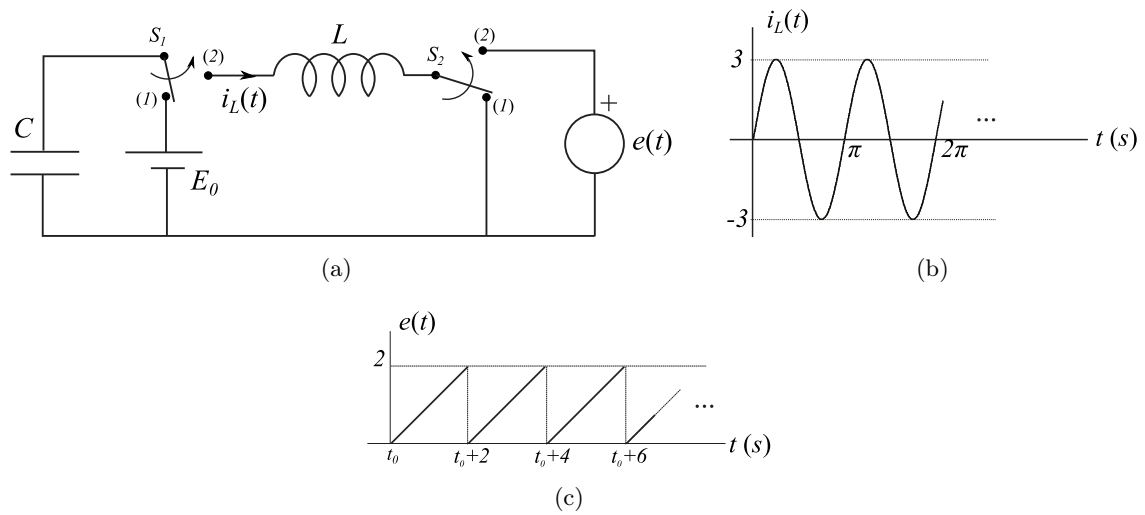


Figure 1

Data :  $C = \frac{1}{8} F$

**Result**

a)  $L = 2 H$  ;  $E_0 = 12 V$

b)  $i_L(t) = 6 \cdot t \cdot e^{-2t}$   $0 < t < t_0$ , Critically damped ( $\xi = 1$ )

c) 
$$i_L(t) = -\frac{1}{8} \cdot (1 - e^{-2(t-t_0)} - 2(t-t_0) \cdot e^{-2(t-t_0)}) \cdot u(t-t_0) + \sum_{n=1}^{\infty} (t-t_0-2n) \cdot e^{-2(t-t_0-2n)} \cdot u(t-t_0-2n)$$

d)  $i_L(t = t_0 + 5) = 0.0178 A$

| UNILATERAL LAPLACE TRANSFORM |   |  |                                   |
|------------------------------|---|--|-----------------------------------|
| Nº                           | $F(s)$  | $f(t) \quad t \geq 0$  | Observations                      |
| 1.-                          | 1   | $\delta(t)$  | Delta function $t = 0$            |
| 2.-                          | $\frac{1}{s}$   | $u(t)$   | Step function $t = 0$             |
| 3.-                          | $\frac{1}{s^2}$   | $tu(t)$  |                                   |
| 4.-                          | $\frac{1}{s^n}$   | $\frac{1}{(n-1)!} \cdot t^{n-1}$   | $n$ Positive integer              |
| 5.-                          | $\frac{1}{s} \cdot e^{-as}$   | $u(t-a)$   | Step function starting at $t = a$ |
| 6.-                          | $\frac{1}{s} \cdot (1 - e^{-as})$                                     | $u(t) - u(t-a)$  | Rectangular pulse $a$             |
| 7.-                          | $\frac{1}{s+a}$   | $e^{-at}$  |                                   |
| 8.-                          | $\frac{1}{(s+a)^n}$   | $\frac{1}{(n-1)!} \cdot t^{n-1} \cdot e^{-at}$   | $n$ Positive integer              |
| 9.-                          | $\frac{1}{s(s+a)}$  | $\frac{1}{a} \cdot (1 - e^{-at})$  |                                   |
| 10.-                         | $\frac{1}{s(s+a)(s+b)}$   | $\frac{1}{ab} \cdot \left(1 - \frac{b}{b-a} \cdot e^{-at} + \frac{a}{b-a} \cdot e^{-bt}\right)$  |                                   |
| 11.-                         | $\frac{s+\alpha}{s(s+a)(s+b)}$  | $\frac{1}{ab} \cdot \left(\alpha - \frac{b(\alpha-a)}{b-a} \cdot e^{-at} + \frac{a(\alpha-b)}{b-a} \cdot e^{-bt}\right)$                   |                                   |
| 12.-                         | $\frac{1}{(s+a)(s+b)}$  | $\frac{1}{b-a} \cdot (e^{-at} - e^{-bt})$  |                                   |
| 13.-                         | $\frac{s}{(s+a)(s+b)}$  | $\frac{1}{a-b} \cdot (a e^{-at} - b e^{-bt})$  |                                   |
| 14.-                         | $\frac{s+\alpha}{(s+a)(s+b)}$   | $\frac{1}{b-a} \cdot [(\alpha-a) e^{-at} - (\alpha-b) e^{-bt}]$  |                                   |
| 15.-                         | $\frac{s+\alpha}{(s+a)^2}$  | $[(\alpha-a)t + 1] \cdot e^{-at}$  |                                   |
| 16.-                         | $\frac{1}{(s+a)(s+b)(s+c)}$   | $\frac{e^{-at}}{(b-a)(c-a)} + \frac{e^{-bt}}{(c-b)(a-b)} + \frac{e^{-ct}}{(a-c)(b-c)}$   |                                   |
| 17.-                         | $\frac{s+\alpha}{(s+a)(s+b)(s+c)}$                                    | $\frac{(\alpha-a) \cdot e^{-at}}{(b-a)(c-a)} + \frac{(\alpha-b) \cdot e^{-bt}}{(c-b)(a-b)} + \frac{(\alpha-c) \cdot e^{-ct}}{(a-c)(b-c)}$  |                                   |
| 18.-                         | $\frac{\omega}{s^2 + \omega^2}$                                       | $\sin(\omega t)$   |                                   |
| 19.-                         | $\frac{s}{s^2 + \omega^2}$  | $\cos(\omega t)$   |                                   |
| 20.-                         | $\frac{s+\alpha}{s^2 + \omega^2}$                                     | $\frac{\sqrt{\alpha^2 + \omega^2}}{\omega} \cdot \sin(\omega t + \phi) \quad ; \quad \phi = \text{atan}\left(\frac{\omega}{\alpha}\right)$ |                                   |
| 21.-                         | $\frac{s \cdot \sin(\phi) + \omega \cdot \cos(\phi)}{s^2 + \omega^2}$ | $\sin(\omega t + \phi)$  |                                   |
| 22.-                         | $\frac{s \cdot \cos(\phi) - \omega \cdot \sin(\phi)}{s^2 + \omega^2}$ | $\cos(\omega t + \phi)$  |                                   |

| Nº   | $F(s)$   | $f(t) \quad t \geq 0$   | Observations  |
|------|--|---|---------------|
| 23.- | $\frac{1}{s(s^2 + \omega^2)}$                    | $\frac{1}{\omega^2} \cdot [1 - \cos(\omega t)]$   |               |
| 24.- | $\frac{s + \alpha}{s(s^2 + \omega^2)}$           | $\frac{\alpha}{\omega^2} - \frac{\sqrt{\alpha^2 + \omega^2}}{\omega^2} \cdot \cos(\omega t + \phi) \quad ; \quad \phi = \text{atan}\left(\frac{\omega}{\alpha}\right)$  |               |
| 25.- | $\frac{1}{(s + a)(s^2 + \omega^2)}$              | $\frac{1}{a^2 + \omega^2} \cdot e^{-at} - \frac{1}{\omega\sqrt{a^2 + \omega^2}} \cdot \sin(\omega t + \phi) \quad ; \quad \phi = \text{atan}\left(\frac{\omega}{-a}\right)$   |               |
| 26.- | $\frac{s^2}{(s + a)(s^2 + \omega^2)}$            | $\frac{a^2}{a^2 + \omega^2} \cdot e^{-at} + \frac{\omega}{\sqrt{a^2 + \omega^2}} \cdot \sin(\omega t + \phi) \quad ; \quad \phi = \text{atan}\left(\frac{\omega}{-a}\right)$  |               |
| 27.- | $\frac{1}{s^2 + 2\xi\omega_n s + \omega_n^2}$    | $\frac{1}{\omega_n\sqrt{1 - \xi^2}} \cdot e^{-\xi\omega_n t} \cdot \sin(\omega_n\sqrt{1 - \xi^2} t)$  | $0 < \xi < 1$ |
| 28.- | $\frac{1}{(s + a)^2 + b^2}$                      | $\frac{1}{b} \cdot e^{-at} \cdot \sin(bt)$  |               |
| 29.- | $\frac{s + a}{(s + a)^2 + b^2}$                  | $e^{-at} \cdot \cos(bt)$  |               |
| 30.- | $\frac{s + \alpha}{(s + a)^2 + b^2}$             | $\frac{\sqrt{(\alpha - a)^2 + b^2}}{b} \cdot e^{-at} \cdot \sin(bt + \phi) \quad ; \quad \phi = \text{atan}\left(\frac{b}{\alpha - a}\right)$   |               |
| 31.- | $\frac{1}{s(s^2 + 2\xi\omega_n s + \omega_n^2)}$ | $\frac{1}{\omega_n^2} - \frac{1}{\omega_n^2\sqrt{1 - \xi^2}} \cdot e^{-\omega_n\xi t} \cdot \sin(\omega_n\sqrt{1 - \xi^2} t + \phi) \quad ; \quad \phi = \text{acos}(\xi)$  | $0 < \xi < 1$ |
| 32.- | $\frac{1}{s[(s + a)^2 + b^2]}$                   | $\frac{1}{a^2 + b^2} + \frac{1}{b\sqrt{a^2 + b^2}} e^{-at} \cdot \sin(bt - \phi) \quad ; \quad \phi = \text{atan}\left(\frac{b}{-a}\right)$   |               |
| 33.- | $\frac{s + \alpha}{s[(s + a)^2 + b^2]}$          | $\frac{\alpha}{a^2 + b^2} + \frac{1}{b} \cdot \sqrt{\frac{(\alpha - a)^2 + b^2}{a^2 + b^2}} \cdot e^{-at} \cdot \sin(bt + \phi)$<br>$\phi = \text{atan}\left(\frac{b}{\alpha - a}\right) - \text{atan}\left(\frac{b}{-a}\right)$  |               |
| 34.- | $\frac{1}{(s + c)[(s + a)^2 + b^2]}$             | $\frac{1}{(c - a)^2 + b^2} \cdot e^{-ct} + \frac{1}{b\sqrt{(c - a)^2 + b^2}} \cdot e^{-at} \cdot \sin(bt - \phi)$<br>$\phi = \text{atan}\left(\frac{b}{c - a}\right)$   |               |
| 35.- | $\frac{1}{s(s + c)[(s + a)^2 + b^2]}$            | $\frac{1}{c(a^2 + b^2)} - \frac{e^{-ct}}{c[(c - a)^2 + b^2]} + \frac{e^{-at} \cdot \sin(bt - \phi)}{b\sqrt{a^2 + b^2}\sqrt{(c - a)^2 + b^2}}$<br>$\phi = \text{atan}\left(\frac{b}{-a}\right) + \text{atan}\left(\frac{b}{c - a}\right)$  |               |
| 36.- | $\frac{s + \alpha}{s(s + c)[(s + a)^2 + b^2]}$   | $\frac{\alpha}{c(a^2 + b^2)} - \frac{(c - \alpha) \cdot e^{-ct}}{c[(c - a)^2 + b^2]} + \frac{\sqrt{(\alpha - a)^2 + b^2} \cdot e^{-at} \cdot \sin(bt + \phi)}{b\sqrt{a^2 + b^2}\sqrt{(c - a)^2 + b^2}}$<br>$\phi = \text{atan}\left(\frac{b}{\alpha - a}\right) - \text{atan}\left(\frac{b}{-a}\right) - \text{atan}\left(\frac{b}{c - a}\right)$ |               |
| 37.- | $\frac{1}{s^2(s + a)}$                           | $\frac{1}{a^2} \cdot (at - 1 + e^{-at})$  |               |
| 38.- | $\frac{1}{s(s + a)^2}$                           | $\frac{1}{a^2} \cdot (1 - e^{-at} - at e^{-at})$  |               |
| 39.- | $\frac{s + \alpha}{s(s + a)^2}$                  | $\frac{1}{a^2} \cdot [\alpha - \alpha e^{-at} + a(a - \alpha)t e^{-at}]$  |               |

| Nº   | $F(s)$   | $f(t) \quad t \geq 0$   | Observations |
|------|--|---|--------------|
| 40.- | $\frac{s^2 + \alpha_1 s + \alpha_0}{s(s+a)(s+b)}$      | $\frac{\alpha_0}{ab} + \frac{a^2 - \alpha_1 a + \alpha_0}{a(a-b)} \cdot e^{-at} - \frac{b^2 - \alpha_1 b + \alpha_0}{b(a-b)} \cdot e^{-bt}$   |              |
| 41.- | $\frac{s^2 + \alpha_1 s + \alpha_0}{s[(s+a)^2 + b^2]}$ | $\frac{\alpha_0}{a^2 + b^2} +$<br>$+\frac{\sqrt{a^2 - b^2 - \alpha_1 a + \alpha_0)^2 + b^2(\alpha_1 - 2a)^2}}{b(a^2 + b^2)} \cdot e^{-at} \cdot \sin(bt + \phi)$<br>$\phi = \text{atan}\left(\frac{b(\alpha_1 - 2a)}{a^2 - b^2 - \alpha_1 a + \alpha_0}\right) - \text{atan}\left(\frac{b}{-a}\right)$  |              |
| 42.- | $\frac{1}{(s^2 + \omega^2)[(s+a)^2 + b^2]}$            | $\frac{1}{\omega} \cdot \frac{\sin(\omega t + \phi_1) + \frac{1}{b} \cdot e^{-at} \cdot \sin(bt + \phi_2)}{\sqrt{4a^2\omega^2 + (a^2 + b^2 - \omega^2)^2}}$<br>$\phi_1 = \text{atan}\left(\frac{-2a\omega}{a^2 + b^2 - \omega^2}\right) \quad ; \quad \phi_2 = \text{atan}\left(\frac{2ab}{a^2 - b^2 + \omega^2}\right)$  |              |
| 43.- | $\frac{s + \alpha}{(s^2 + \omega^2)[(s+a)^2 + b^2]}$   | $\frac{1}{\omega} \cdot \sqrt{\frac{\alpha^2 + \omega^2}{(2a\omega)^2 + (a^2 + b^2 - \omega^2)^2}} \cdot \sin(\omega t + \phi_1) +$<br>$+\frac{1}{b} \cdot \sqrt{\frac{(\alpha - a)^2 + b^2}{(2a\omega)^2 + (a^2 + b^2 - \omega^2)^2}} \cdot e^{-at} \cdot \sin(bt + \phi_2)$<br>$\phi_1 = \text{atan}\left(\frac{\omega}{\alpha}\right) - \text{atan}\left(\frac{2a\omega}{a^2 + b^2 + \omega^2}\right)$<br>$\phi_2 = \text{atan}\left(\frac{b}{\alpha - a}\right) + \text{atan}\left(\frac{2ab}{a^2 - b^2 + \omega^2}\right)$ |              |
| 44.- | $\frac{s + \alpha}{s^2[(s+a)^2 + b^2]}$                | $\frac{1}{a^2 + b^2} \cdot \left(\alpha t + 1 - \frac{2\alpha a}{a^2 + b^2}\right) + \frac{\sqrt{b^2 + (\alpha - a)^2}}{b(a^2 + b^2)} \cdot e^{-at} \cdot \sin(bt + \phi)$<br>$\phi = 2\text{atan}\left(\frac{b}{\alpha - a}\right) + \text{atan}\left(\frac{b}{\alpha - a}\right)$   |              |
| 45.- | $\frac{s^2 + \alpha_1 s + \alpha_0}{s^2(s+a)(s+b)}$    | $\frac{\alpha_1 + \alpha_0 t}{ab} - \frac{\alpha_0(a+b)}{(ab)^2} - \frac{1}{a-b} \cdot \left(1 - \frac{\alpha_1}{a} + \frac{\alpha_0}{a^2}\right) \cdot e^{-at}$<br>$+\frac{1}{a-b} \cdot \left(1 - \frac{\alpha_1}{b} + \frac{\alpha_0}{b^2}\right) \cdot e^{-bt}$   |              |