

PROBLEMS OF CHAPTER 2: Two-port networks.

February 22, 2018

Problem 2.1

The two-port network Q of figure 1(a) is connected in the circuit shown in Figure 1(b). Obtain:

- a) The family of z -parameters for the two-port network.
- b) The power absorbed by the load Z_R .

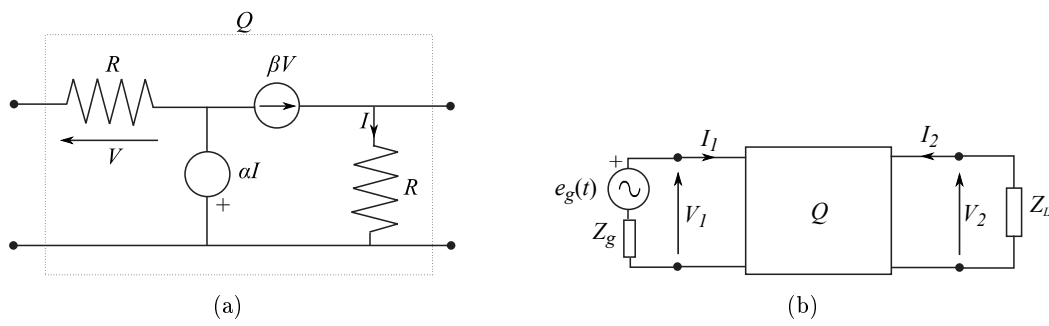


Figure 1

$$\begin{aligned}
 \text{Data : } R &= 1 \Omega \quad ; \quad \alpha = 1 \Omega \quad ; \quad \beta = 1 \Omega^{-1} \\
 Z_g &= 1 \Omega \quad ; \quad Z_R = 1 + j \Omega \quad ; \quad e_g(t) = 4 \sin(t) \text{ V}
 \end{aligned}$$

Result

$$\text{a) } \begin{pmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{pmatrix} = \begin{pmatrix} 0 & -1 \\ 1 & 1 \end{pmatrix}$$

$$\text{b) } P_{Z_R} = \frac{4}{5} \cdot W$$

Problem 2.2

- a) On the quadripole Q_1 we obtain the measurements shown in figure 1(a) and 1(b), obtaining the following results:

$$\text{Circuit (a) : } \begin{cases} i_1(t) = 2 \sin(\omega t) \text{ A} \\ i_2(t) = 2 \sin\left(\omega t - \frac{\pi}{2}\right) \text{ A} \end{cases} \quad ; \quad \text{Circuit (b) : } \begin{cases} i_3(t) = 2 \sin\left(\omega t - \frac{\pi}{2}\right) \text{ A} \\ v_4(t) = \sin\left(\omega t + \frac{\pi}{2}\right) \text{ V} \end{cases}$$

Obtain the h -parameters of the quadripole.

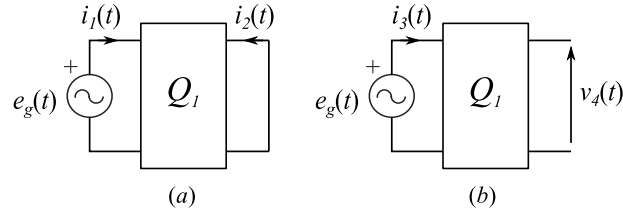


Figure 1

Data: $e_g(t) = 4 \sin(\omega t)$ V

b) Obtain the T -parameters of the quadripole with the structure shown in figure 2.

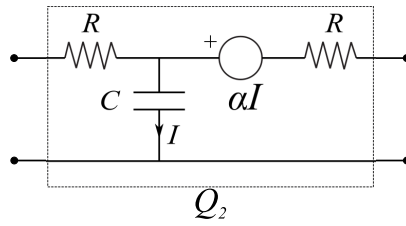


Figure 2

Data: $R = \alpha = \frac{1}{2} \Omega$; $Z_C = -\frac{1}{2}j \Omega$.

Result

$$\text{a) } (h_{Q_1}) = \begin{pmatrix} 2 \Omega & 4 - 4j \\ -j & -2j \Omega^{-1} \end{pmatrix}$$

$$\text{b) } (T_{Q_2}) = \begin{pmatrix} j & \frac{1+j}{2} \Omega \\ (-1+j) \Omega^{-1} & \frac{1+j}{2} \end{pmatrix}$$

Problem 2.3

The quadripole Q_1 of the associated quadripoles shown in figure 2 is RLC and measurements on this quadripole are shown in figure 1(a) and (b). The quadripole Q_2 is symmetrical and two of his parameters are $h_{11} = 5 \Omega$ and $h_{12} = 1$.

- Obtain a family of parameters that characterizes the association of the quadripoles Q_1 and Q_2 as it is shown in Figure 2.
- Obtain the impedance Z_e .
- Obtain $i_2(t)$.

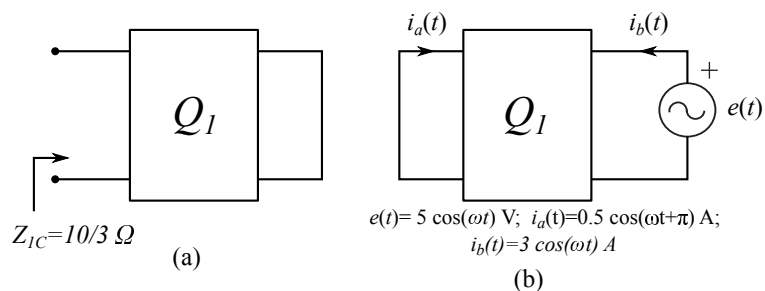


Figure 1

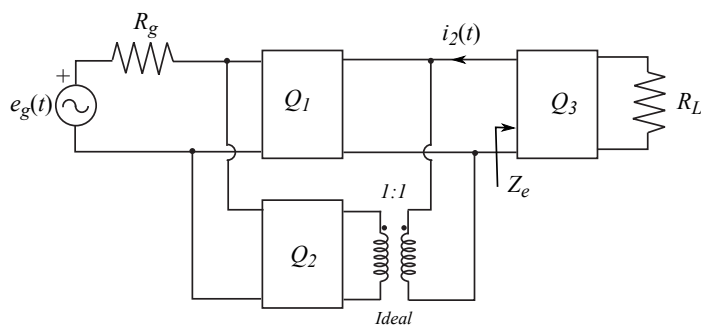


Figure 2

DATOS: $R_g = 10 \Omega$; $R_L = 50 \Omega$; $e_g(t) = 10 \cos(\omega_0 t) V$

$$Q_3 = \begin{pmatrix} A = \frac{\sqrt{2}}{2} & B = 25\sqrt{2}j \Omega \\ C = \frac{\sqrt{2}}{100}j \Omega^{-1} & D = \frac{\sqrt{2}}{2} \end{pmatrix}$$

Result

$$a) \begin{pmatrix} y_{11}^T & y_{12}^T \\ y_{21}^T & y_{22}^T \end{pmatrix} = (y_{Q_1}) + (y_{Q_2}) = \begin{pmatrix} \frac{3}{10} & -\frac{1}{10} \\ -\frac{1}{10} & \frac{3}{5} \end{pmatrix} + \begin{pmatrix} \frac{1}{5} & -\frac{1}{5} \\ -\frac{1}{5} & \frac{1}{5} \end{pmatrix} = \begin{pmatrix} \frac{1}{2} & -\frac{3}{10} \\ -\frac{3}{10} & \frac{4}{5} \end{pmatrix}$$

$$b) Z_e = 50 \Omega$$

$$c) i_2(t) = \frac{1}{67} \cdot \cos(\omega_0 t + \pi) A$$

Problem 2.4

In figure 1(a) an association of two quadripoles, Q_A and Q_B , is shown and their circulation currents are zero. The quadripole Q_A is symmetrical and some measurements on Q_A are shown in figure 1(b). The quadripole Q_B is RLC and for this quadripole it is known $Z_{1,O} = \frac{4}{5} \Omega$, $Z_{1,S} = 0 \Omega$, $Z_{2,O} = \frac{1}{5} \Omega$ and the phase of the inverse voltage gain with input port in open circuit is zero. Calculate a family of parameters that characterizes the association of the two quadripoles as it is shown in Figure 1(a)

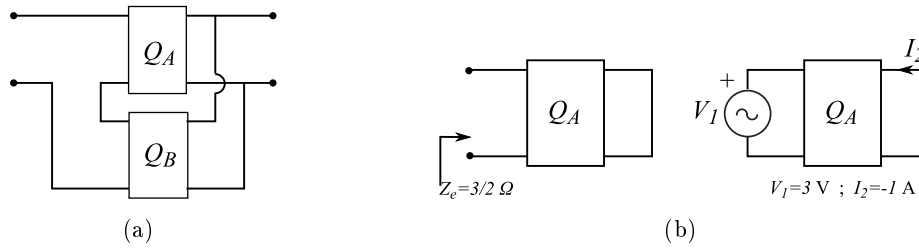


Figure 1

Result

$$(h_{Q_T}) = (h_{Q_A}) + (h_{Q_B}) = \begin{pmatrix} \frac{3}{2} \Omega & \frac{1}{2} \\ -\frac{1}{2} & \frac{1}{2} \Omega^{-1} \end{pmatrix} + \begin{pmatrix} 0 \Omega & 2 \\ -2 & 5 \Omega^{-1} \end{pmatrix} = \begin{pmatrix} \frac{3}{2} \Omega & \frac{5}{2} \\ -\frac{1}{2} & \frac{11}{2} \Omega^{-1} \end{pmatrix}$$

Problema 2.5

In the circuit of the figure 1(a) the currents $i_1(t)$ and $i_2(t)$ are known. Furthermore, the internal structure of the quadripole Q is the one shown in figure 1(b).

- a) Calculate the values of R_1 and R_2 .
- b) Obtain $i_1(t)$ if $Z_L \rightarrow \infty$.

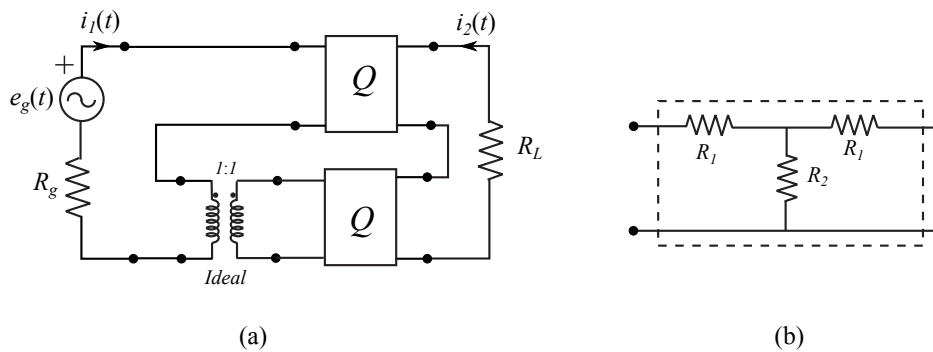


Figure 1

DATOS : $e_g(t) = 4 \cdot \cos(\omega t)$ V. ; $i_1(t) = \cos(\omega t)$ A ; $i_2(t) = \frac{1}{4} \cdot \cos(\omega t + \pi)$ A
 $R_g = 1 \Omega$; $R_L = 2 \Omega$

Result

- a) $R_1 = 1 \Omega$; $R_2 = \frac{2}{3} \Omega$
- b) $i_1(t) = \frac{12}{13} \cos(\omega t)$ A

Problem 2.6

For a symmetrical quadripole, Q , we have performed the measurements shown in figure 1(a). Calculate a family of parameters to characterize the association shown in figure 1(b) of two of these quadripoles.

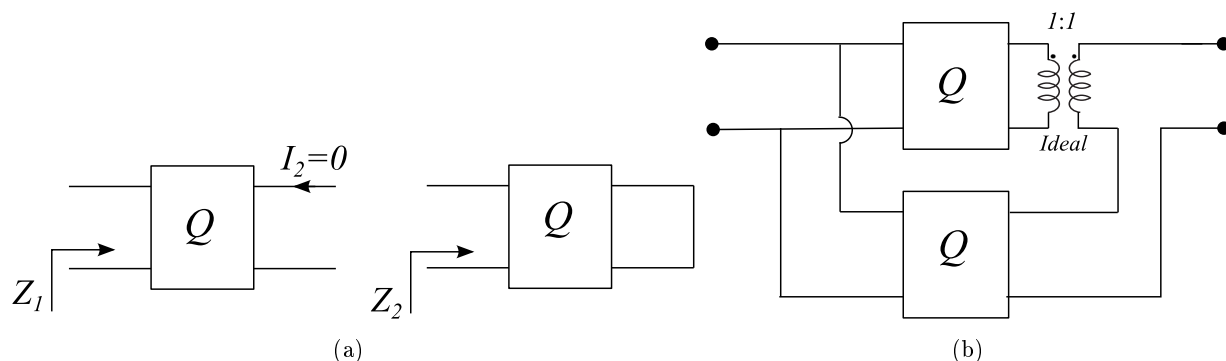


Figure 1

Data: $Z_1 = 2 \Omega$ and $Z_2 = 4 \Omega$.

Result

$$(g_{Q_T}) = \begin{pmatrix} 1 \Omega^{-1} & \pm 2j \\ \mp 2j & 8 \Omega \end{pmatrix}$$

Problem 2.7

For the associated quadripoles shown in Figure 1, calculate:

- The most adequate family of parameters for the association of quadripoles Q , which is shown in Figure 2.
- The time-domain expression of the current that goes through the source $e_g(t)$.

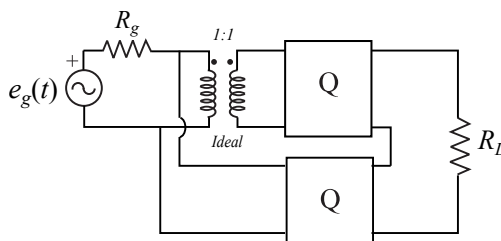


Figure 1

$$DATA: e_g(t) = 17 \text{ sen}(t) \text{ V} ; R_g = \frac{2}{5} \Omega ; R_L = \frac{15}{2} \Omega$$

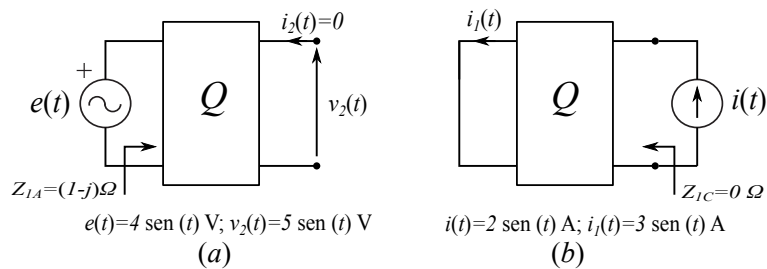


Figure 2


Result

a) $(g_Q) = \begin{pmatrix} \frac{1}{2} \cdot (1+j) \Omega^{-1} & -\frac{3}{2} \\ \frac{5}{4} & 0 \Omega \end{pmatrix}$

b) $i_1(t) = 5\sqrt{17} \text{ sen}(t + 0.245) \text{ A}$

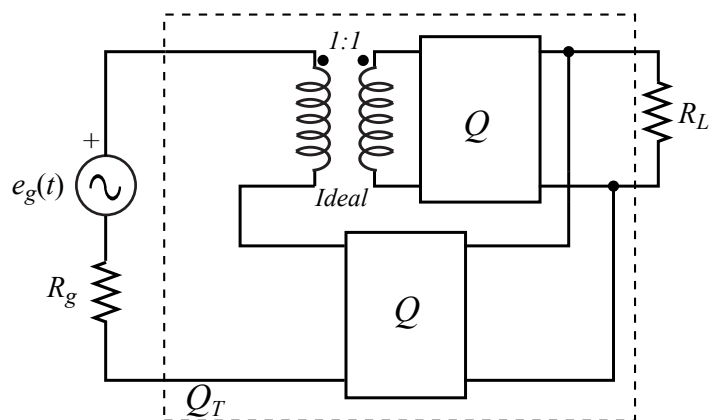Problem 2.8

In the circuit of the figure 1, we know the h -parameters of the two-port network (Q_T). Note that this quadripole Q_T represents the association of two identical quadripoles (Q). However, the internal structure of the quadripole Q is not known, but it can be one of the structures shown in figure 2(a) or (b).



$$(h)_{Q_T} = \begin{pmatrix} 5 \Omega & 1 \\ -\frac{1}{2} & \frac{1}{2} \Omega^{-1} \end{pmatrix}$$

Figure 1

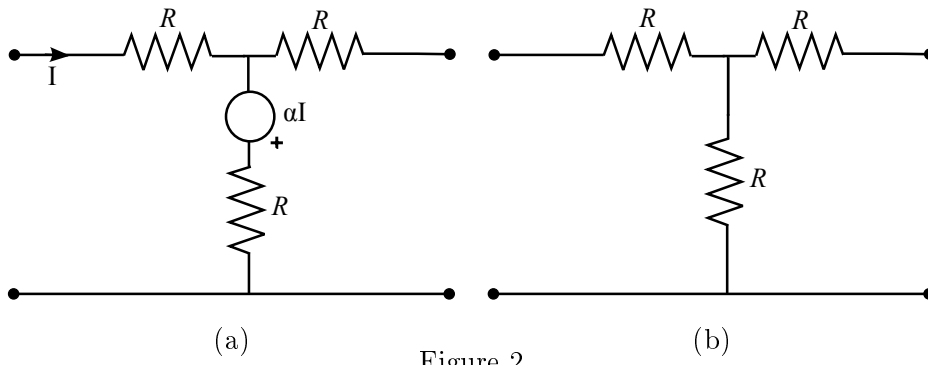


Figure 2

Answer the following questions:

- Reason and choose, without performing any calculation, which of the two circuits (a) or (b) shown in figure 2 corresponds to the quadripole Q of the figure 1.
- Calculate the values of the elements of the quadripole Q : (R and α if the selected Q is (a), or R if the selected Q is (b)).
- Calculate the power dissipated by R_L .

Data : $e_g(t) = 13 \cos(\omega t) \text{ V}; \quad R_g = 1 \Omega; \quad R_L = 2 \Omega$

Result

- a) (a).
- b) $R = 2 \Omega$; $\alpha = 1 \Omega$
- c) $P_{R_L} = \frac{1}{4} \text{ W}$

Problem 2.9

We want to associate the two quadripoles Q_A and Q_B , as it is shown in figure 1. For the quadripole Q_A the z -parameters are known. From the quadripole Q_B we know that it is reciprocal and the measurements shown in figure 2.

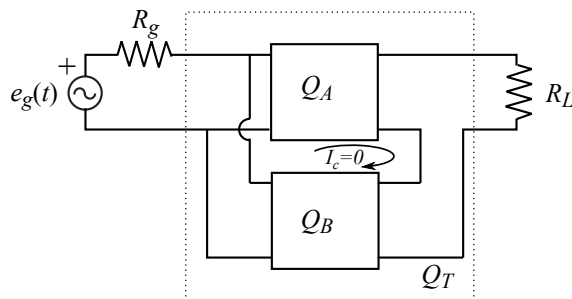


Figure 1

DATOS: $R_g = R_L = 2 \Omega$; $e_g(t) = \cos(t) \text{ V}$, $(z_{Q_A}) = \begin{pmatrix} -4j \Omega & -2j \Omega \\ -2j \Omega & 0 \Omega \end{pmatrix}$.

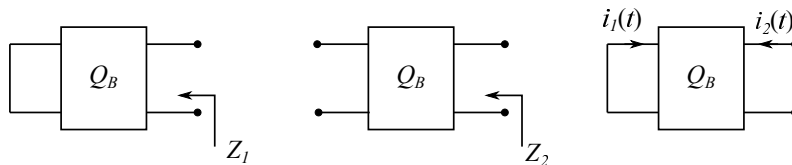


Figure 2

DATA: $Z_1 = 1 \Omega$; $Z_2 = 2 \Omega$; $i_1(t) = \cos(t) \text{ A}$; $i_2(t) = 2 \cos(t) \text{ A}$

- a) Obtain the adequate family of parameters for Q_A y Q_B so that they can be association to the Q_T .
- b) The power dissipated by the resistor R_L in the circuit of the figure 1.

Result

$$\text{a) } (g_{Q_A}) = \begin{pmatrix} \frac{j}{4} \Omega^{-1} & -\frac{1}{2} \\ \frac{1}{2} & j \Omega \end{pmatrix}, (g_{Q_B}) = \begin{pmatrix} \frac{1}{4} \Omega^{-1} & \frac{1}{2} \\ -\frac{1}{2} & 1 \Omega \end{pmatrix}$$

$$\text{b) } P_{R_L} = 0 \text{ W}$$

Problem 2.10

For the association of quadripoles shown in Figure 2 we know that the circulation currents are zero ($I_c = 0$)

- Obtain a family of parameters to characterize the *RLC* quadripole (Q_B) on which the measurements shown in figure 1 have been done.
- Obtain the equivalent impedance between the points *C* and *D* to the left (Z_S) in the circuit of the figure 2.

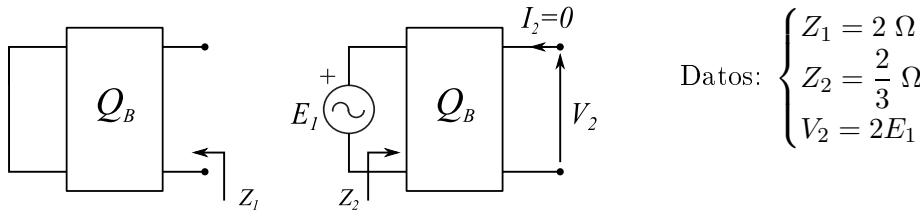


Figure 1

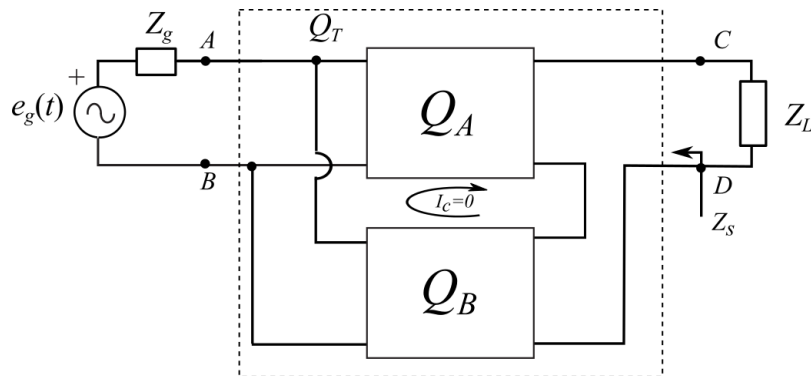


Figure 2

$$\text{DATA: } (z_{Q_A}) = \begin{pmatrix} 2 \Omega & 2 \Omega \\ 2 \Omega & (2 - 2j) \Omega \end{pmatrix}; Z_g = 1 \Omega$$

Result

$$\text{a) } (g_{Q_A}) = \begin{pmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{pmatrix} = \begin{pmatrix} \frac{1}{2} \Omega^{-1} & -1 \\ 1 & -2j \Omega \end{pmatrix}; (g_{Q_B}) = \begin{pmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{pmatrix} = \begin{pmatrix} \frac{3}{2} \Omega^{-1} & -2 \\ 2 & 2 \Omega \end{pmatrix}$$

$$\text{b) } Z_S = (5 - 2j) \Omega$$

Problem 2.11

For the associated quadripoles Q_A and Q_B shown in figure 3 it is known that the circulation currents are zero and also that:

- The quadripole Q_A is *RLC* and on measurements on this quadripole are shown in figure 1(a) y 1(b)

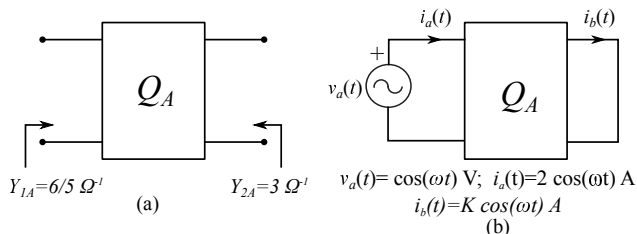


Figure 1

- The quadripole Q_B is symmetrical and measurements on this quadripole are shown in figure 2(a) y 2(b).

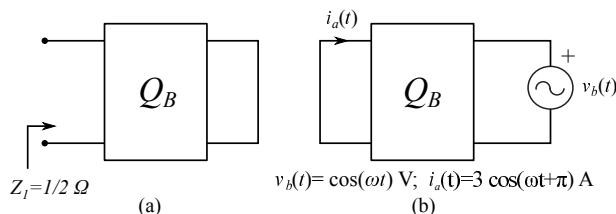


Figure 2

Optain:

- A family of parameters that characterizes the association of the quadripoles Q_A y Q_B shown in figure 3.
- Power delivered by the real generator $(e_g(t), R_g)$.
- Temporal expression of the current $i_x(t)$.

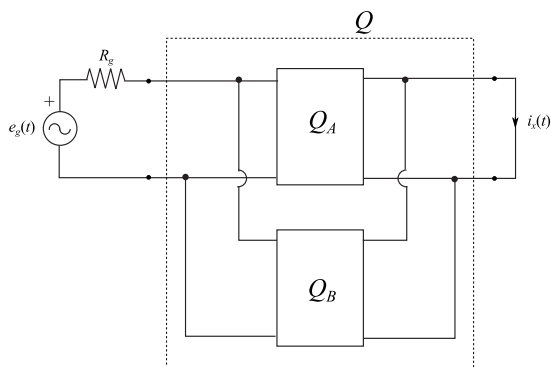


Figure 3

DATA: $e_g(t) = 4 \cos(\omega t) \text{ V}$; $R_g = \frac{1}{4} \Omega$

Result

$$\text{a) } (y_{Q_T}) = (y_{Q_A}) + (y_{Q_B}) = \begin{pmatrix} 2 \Omega^{-1} & -2 \Omega^{-1} \\ -2 \Omega^{-1} & 5 \Omega^{-1} \end{pmatrix} + \begin{pmatrix} 2 \Omega^{-1} & -3 \Omega^{-1} \\ -3 \Omega^{-1} & 2 \Omega^{-1} \end{pmatrix} = \begin{pmatrix} 4 \Omega^{-1} & -5 \Omega^{-1} \\ -5 \Omega^{-1} & 7 \Omega^{-1} \end{pmatrix}$$

$$\text{b) } P_{E_g, R_g} = 8 \text{ W}$$

$$\text{c) } i_x(t) = 10 \cos(\omega t) \text{ A}$$