

PROBLEMS OF CHAPTER 3: Transfer of power. Image Parameters.

March 13, 2017

Problem 3.1

For the circuit in Figure 1, it is known that the real source $(e_g(t), R_g)$ delivers the maximum power to the network LC . If we know the measurements of the voltmeter and ammeter are $V_v = \sqrt{5} V_{ef}$ and $I_A = 2 A_{ef}$, respectively, obtain:

- a) The power absorbed by resistor R .
- b) Value of C .
- c) Equivalent impedance from the output of the LC network.

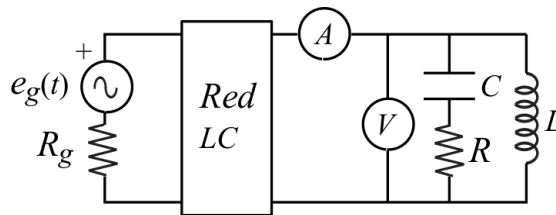


Figure 1

Data: $e_g(t) = 4 \cos(t) \text{ V}$; $R_g = 1 \Omega$; $R = 2 \Omega$

Result

- a) $P_R = 2 \text{ W}$.
- b) $C = 1 \text{ F}$.
- c) $Z_S = \frac{1 - 2j}{2} \Omega$

Problem 3.2

For the circuit in Figure 1 there is impedance matching in section CD . We know that the network 2 has a power transmission loss of $\alpha_T = 6 \text{ dBs}$. Determine:

- a) Value of voltage V_{AB} .
- b) Power in impedance Z_L .

c) Transmission and insertion loss for the set of two networks.

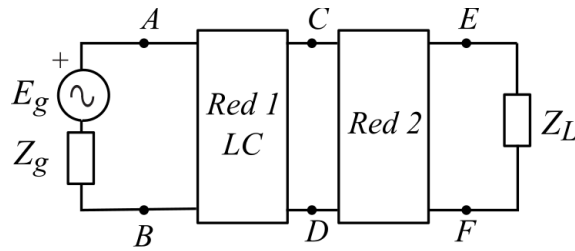


Figure 1

Data: $E_g = (1 + j) \text{ V}$; $Z_g = (2 - 2j) \Omega$; $Z_L = (2 + 5j) \Omega$.

Result

a) $V_{AB} = j \text{ V}$.

b) $P_{Z_L} = \frac{1}{32} \text{ W}$

c) $\alpha_{Total} = \alpha_T = 6 \text{ dBs}$, $\alpha_I = 4.08 \text{ dBs}$

Problem 3.3

In the circuit of Figure 1 we have impedance matching in section CD . Network 2 introduces a power transmission loss of $\alpha_T = 3 \text{ dBs}$ and the measurement of the voltmeter is of $\sqrt{2} V_{ef}$. Determine:

a) Power of the impedance Z_L .

b) Value of impedance Z_C .

c) Transmission and insertion loss for the set of two networks.

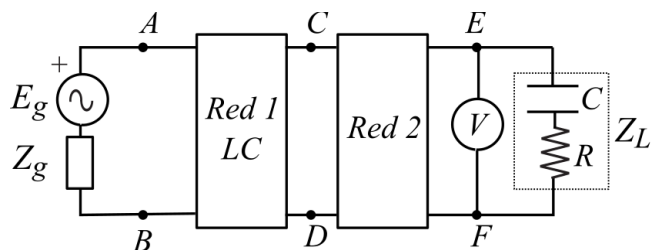


Figure 1

Data: $E_g = -8j \text{ V}$; $Z_g = (4 - 4j) \Omega$; $R = 1 \Omega$.

Result

a) $P_{Z_L} = 1 \text{ W}$.

b) $Z_C = -j \Omega$.

c) $\alpha_T = 3 \text{ dBs}$, $\alpha_I = -1.94 \text{ dBs}$

Problem 3.4

In the circuit of Figure 1, we have impedance matching in section AB , and the voltmeter measures a voltage of $5 V_{ef}$. Obtain:

- Input impedance for network 2, Z_{CD} .
- Power absorbed in R_2 .
- The value of inductor L_2 .

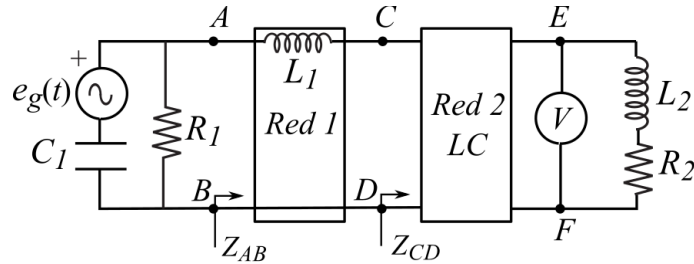


Figure 1

Data: $e_g(t) = 4 \cos(t) \text{ V}$; $R_1 = 2 \Omega$; $R_2 = 9 \Omega$; $L_1 = 2 \text{ H}$; $C_1 = \frac{1}{2} \text{ F}$.

Result

- $Z_{CD} = (1 - j) \Omega$.
- $P_{R_2} = 1 \text{ W}$.
- $L_2 = \text{ H}$

Problem 3.5

For the circuit shown in Figure 1(a), we know that the quadripoles have the internal structure shown in Figure 1(b). Compute:

- The image parameters (Z_0 y γ) of the quadripoles.
- Value for a , in order to guarantee that the power of the source $i_g(t)$ is 0 W .
- Power for impedance Z_L .

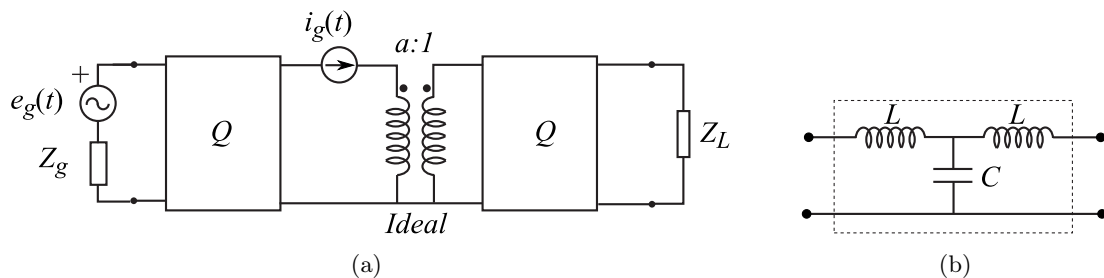


Figure 1

$$\begin{aligned}
 \text{Data : } \quad i_g(t) &= \frac{2}{\sqrt{3}} \sin(\omega t) \text{ A} \quad ; \quad \omega L = 5 \Omega \quad ; \quad \frac{1}{\omega C} = 10 \Omega \\
 e_g(t) &= 20 \sin\left(\omega t + \frac{\pi}{3}\right) \text{ V} \quad ; \quad Z_g = Z_L = 5\sqrt{3} \Omega
 \end{aligned}$$

Result

- a) $Z_0 = 5\sqrt{3} \Omega$; $\gamma = j\frac{\pi}{3}$
- b) $a = 1$
- c) $P_{Z_L} = \frac{10\sqrt{3}}{3} \text{ W}$

Problem 3.6

For the circuit in Figure 1(a), networks Q_A and Q_B have the same impedance Z_0 . If quadripole Q_A has the internal structure shown in Figure 1(b), determine:

- a) Image parameters of quadripole Q_A .
- b) Power absorbed by the load.

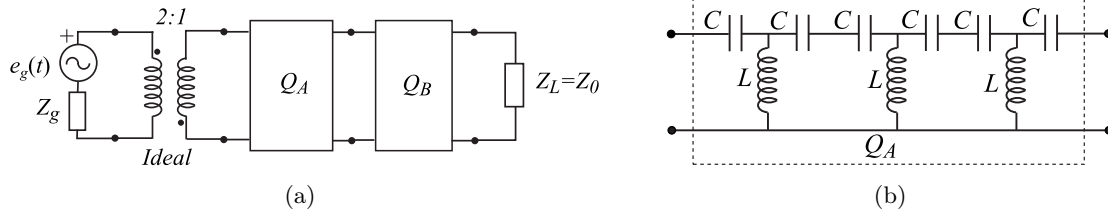


Figure 1

$$\begin{aligned}
 \text{Data : } \quad e_g(t) &= 24 \sin(\omega t) \text{ V} \quad ; \quad Z_g = 12 \Omega \\
 Q_A \quad \left\{ \omega L = 5 \Omega \quad ; \quad \frac{1}{\omega C} = 1 \Omega \right\} \quad ; \quad Q_B \quad \left\{ Z_0 = Z_0^A \quad ; \quad \gamma = \ln(2) \text{ Np} \right\}
 \end{aligned}$$

Result

- a) $Z_{01} = 3 \Omega$; $\gamma_A = 1.9305j$
- b) $P_{Z_L} = 1.5 \text{ W}$

Problem 3.7

For the circuit shown in Figure 1(a) we know the image parameters of quadripole Q_A and the internal structure of two-port network Q_B , see Figure 1(b).

- a) Obtain the value of the impedance Z in order to guarantee that the source (E_g, Z_g) delivers the maximum power.
- b) Find the power absorbed by the impedance Z obtained in the previous section, as well as the time-domain expression of current $i_Z(t)$.

c) Justify why the insertion loss of quadripole Q_B is 0.

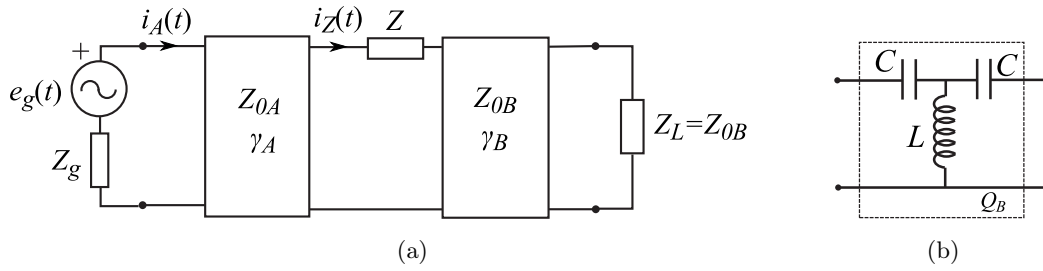


Figure 1

Data : $e_g(t) = 6 \sin(\omega t)$ V

$Z_g = 6 \Omega$

; $Z_L = Z_{0B}$

$Q_A \{ Z_{0A} = 6 \Omega ; \gamma = \ln(2) \text{ Np} \}$; $Q_B \{ \omega L = 5 \Omega ; \frac{1}{\omega C} = 1 \Omega \}$

Result

a) $Z = 3 \Omega$

b) $P_Z = \frac{3}{32} \text{ W}$; $i_Z(t) = \frac{1}{4} \cdot \sin(\omega t)$ A

Problem 3.8

For the association of quadripoles shown in Figure 1(a), the three networks Q are identical and their internal structure is shown in figure 1(b). If the load impedance Z_L is equal to the characteristic impedance of the networks, obtain:

a) The image parameters of the quadripole Q .

b) The time-domain expression of voltage $V_{CD}(t)$.

c) The maximum number of quadripoles Q that we can connect in cascade, between the source (E_g, R_g) and the load Z_L in order to guarantee that the load receives a power $\geq 1 \text{ mW}$.

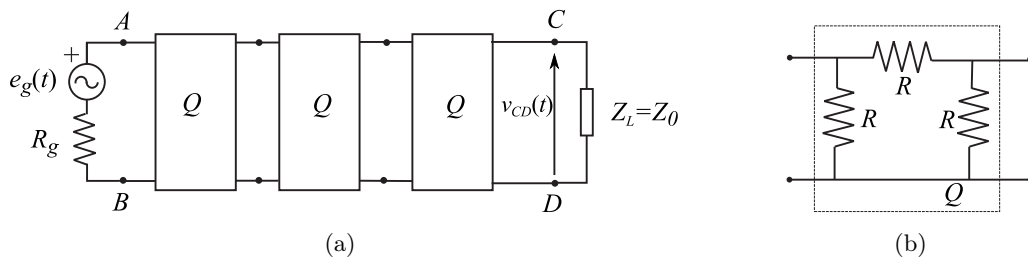


Figure 1

Data : $e_g(t) = 75 \cos(\omega t)$ V ; $R = 6 \Omega$; $R_g = 2Z_0$

Result

- a) $Z_0 = 2\sqrt{3} \Omega$; $\gamma = 1.3170 \text{ Np}$
- b) $V_{CD} = 0.4809$
- c) $n = 4$

Problem 3.9

The quadripole shown in Figure 1(a), which is bilateral and symmetric, has the following parameters: $z_{11} = 8 \Omega$ and $y_{11} = \frac{1}{2} \Omega^{-1}$.

- a) Obtain the image parameters Z_0 and γ .
- b) Determine the power absorbed by the load Z_L , using the circuit shown in Figure 1(b), where the quadripoles have the same internal structure of the two-port networks shown in Figure 1(a).

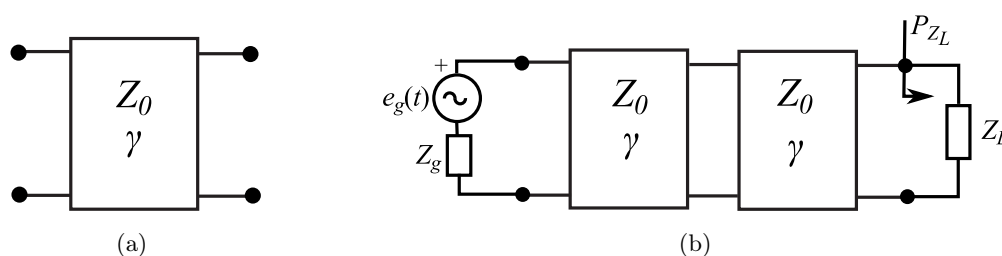


Figure 1

$$\text{Data : } e_g(t) = 4 \sin(\omega t) \text{ V; } Z_g = Z_L = Z_0$$

Result

- a) $Z_0 = 4 \Omega$, $\gamma = \frac{\text{Ln}(3)}{2} \text{ Np}$
- b) $P_2 = \frac{1}{18} \text{ W}$

Problem 3.10

For the circuit shown in Figure 1 all the quadripoles are identical and symmetric. The measurements shown in Figure 2 have been done with these quadripoles.

- a) Compute the image parameters (Z_0 and γ) for the quadripole Q .
- b) Determine the value of a so as to guarantee that the source ($e_g(t)$, Z_g) delivers the maximum power.
- c) Obtain the power absorbed by the load Z_L and the time-domain expression of the current $i_L(t)$.
- d) Determine the power transmission and insertion loss introduced by the set of quadripoles and the transformer.

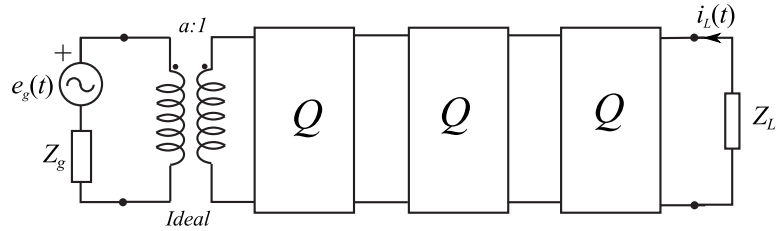


Figure 1

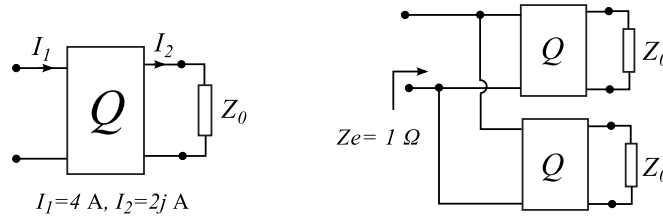


Figure 2

Data : $e_g(t) = 16 \cdot \cos(\omega t) \text{ V}$; $Z_g = 4Z_0$; $Z_L = Z_0$.

Result

a)
$$\begin{cases} Z_0 = 2 \Omega \\ \gamma = \ln(2) - j\frac{\pi}{2} \end{cases}$$

b) $a = 2$

c) $P_{Z_L} = \frac{1}{16} \text{ W}$; $i_L(t) = \frac{1}{4} \cos(\omega t + \frac{3\pi}{2}) \text{ A}$

d) $\alpha_T = 2.08 \text{ Np}$; $\alpha_I = 1.86 \text{ Np}$

Problem 3.11

For the circuit shown in Figure 1 determine the power of the source $i(t)$.

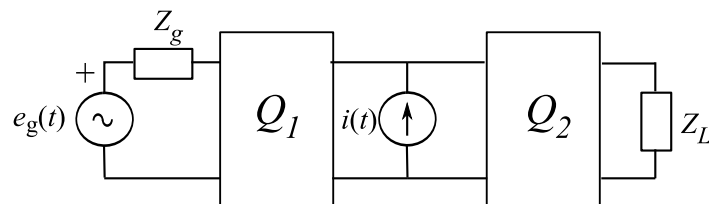


Figure 1

Data:

$e_g(t) = 8 \cdot \sin(\omega t) \text{ V}$; $i(t) = \cos(\omega t) \text{ A}$; $Z_g = Z_L = 3 \Omega$

$Q_1 \equiv \begin{cases} Z_{01} = 3 \Omega \\ Th(\gamma_1) = \frac{3}{5} \end{cases}$; $Q_2 \equiv \begin{cases} Z_{02} = 5 \Omega \\ \gamma_2 = -j\frac{\pi}{3} \end{cases}$

Result

$$P_I = 0.8260 \text{ W}$$

Problem 3.12

In the circuit of Figure 1 we know that each quadripole Q is RLC . We also know that its transmission parameters are: $A = 3$, $B = 8 \Omega$, $C = 1 \Omega^{-1}$, $D = 3$.

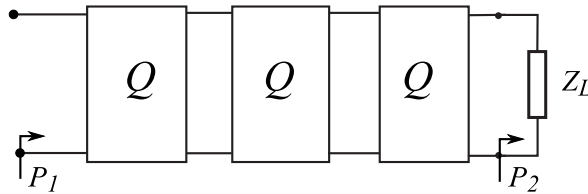


Figure 1

Data: $Z_L = 2\sqrt{2} \Omega$

- Justify if quadripole Q is bilateral and symmetric. If so, obtain its image parameters (Z_0 and γ).
- Find the ratio between the input power, P_1 , and the output power, P_2 , of the association given in Figure 1.
- Compute the ratio between the power absorbed by the load before and after one of the quadripoles is removed from the association shown in Figure 1.

Result

- Quadripole bilateral and symmetric.
$$\begin{cases} Z_0 = 2\sqrt{2} \Omega \\ \gamma = 1.763 \text{ Np} \end{cases}$$
- $\frac{P_1}{P_2} = 39261.5$
- $\frac{P'_2}{P_2} = 33.99$

Problem 3.13

In the circuit shown in Figure 1, the three bilateral and symmetric quadripoles are characterized by their image parameters. They all have the same characteristic impedance Z_0 . Moreover, we know that $Z_g = Z_L = Z_0$.

- Compute the power absorbed by the load Z_L .
- Compute the power of the voltage sources $e(t)$ and $e_g(t)$, and of the current source $i(t)$.

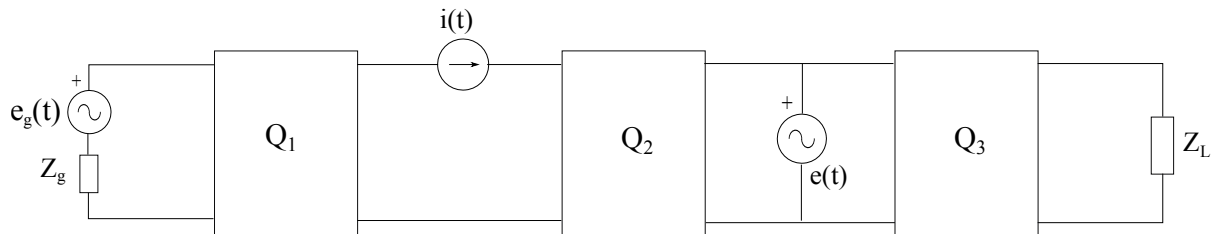


Figure 1

Data : $e_g(t) = 30 \sin(\omega t + \frac{\pi}{2})$ V; $e(t) = 10 \sin(\omega t)$ V; $i(t) = 5 \sin(\omega t)$ A;

$$Q_1 \begin{cases} Z_0 = 5 \Omega \\ \gamma_1 = j\frac{\pi}{2} \end{cases} \quad Q_2 \begin{cases} Z_0 = 5 \Omega \\ \gamma_2 = j\pi \end{cases} \quad Q_3 \begin{cases} Z_0 = 5 \Omega \\ \gamma_3 = \ln(2) \text{ Np} \end{cases}$$

Result

- $P_{Z_L} = \frac{5}{2}$ W
- $P_{E_g} = 15$ W; $P_E = 35$ W; $P_I = -\frac{75}{2}$ W

Problem 3.14

For the association of quadripoles shown in Figure 1, it is known that the two-port network Q_2 is bilateral, and that its output impedance with an open-circuit input is $Z_{2A} = \frac{1}{2} \Omega$. Moreover, the measurements shown in Figure 2 have been done.

- Determine a family of parameters to characterize the quadripole Q_2 .
- Find the value for resistor R in order to guarantee that the source delivers the maximum power.
- Determine the transmission loss of the network between the real source (E_g, Z_g) and the load (Z_L).


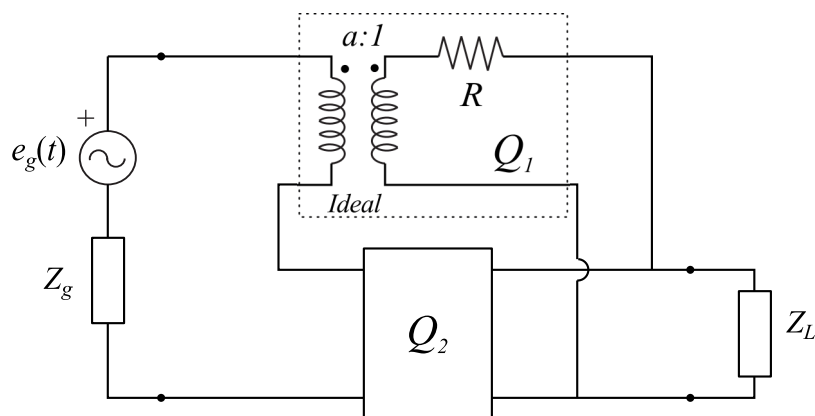


Figure 1

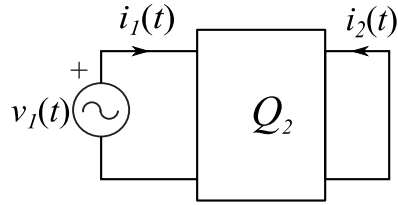

$$v_I(t) = 22 \sin(\omega t) \text{ V};$$

$$i_1(t) = 2 \sin(\omega t) \text{ A};$$

$$i_2(t) = 4 \sin(\omega t - \pi) \text{ A}.$$

Figure 2

Data: $Z_g = 35 \Omega$; $Z_L = \frac{1}{2} \Omega$; $a = 2$.

Result

a) $h_{Q_2} = \begin{pmatrix} 11 \Omega & 2 \\ -2 & 2 \Omega^{-1} \end{pmatrix}$

b) $R = 5 \Omega$.

c) $\alpha_T = 1.4311 \text{ Np} = 12.43 \text{ dB}$.

Problem 3.15

Given the association of quadripoles in Figure 1, determine:

- The image parameters of quadripoles Q_1 and Q_2 .
- The insertion loss produced by quadripole Q_2 and the transmission loss of quadripole Q_1 .

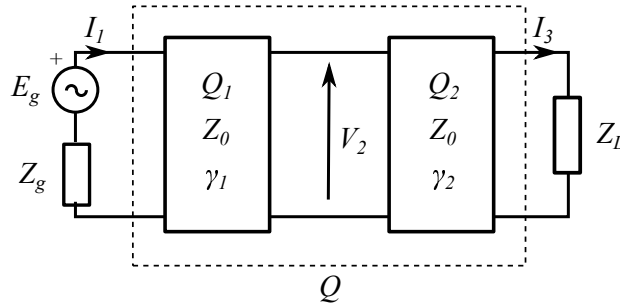


Figure 1

Data : $E_g = 100 \text{ V}$; $Z_g = (6 - 2j) \Omega$; $Z_L = Z_0$; $I_1 = (4 + 3j) \text{ A}$; $V_2 = (7 - j) \text{ V}$
 $I_3 = -\frac{4 + 3j}{10} \text{ A}$

Result

a) $Z_0 = (10 - 10j) \Omega$, $\gamma_1 = \text{Ln}(10) \text{ Np}$, $\gamma_2 = j\pi \text{ rad}$.

b) $\alpha_{I_2} = \alpha_2 = 0 \text{ Np}$, $\alpha_{T_1} = \alpha_1 = \text{Ln}(10) \text{ Np}$

Problem 3.16

Quaripoles Q_A and Q_B have been connected as it is shown in Figure 1. Of quaripole Q_A we know the value of $Z_{0A} = \frac{1-j}{3}\Omega$. Of quaripole Q_B we know that it is bilateral and symmetric, and we also know its transmission parameters A and B.

- Compute the image parameters of quadripole Q_B .
- Determine the time-domain expression of the current $i_L(t)$, if the load Z_L coincides with the characteristic impedance of the quadripole Q_B .
- Compute the transmission and insertion loss of the set of two quadripoles Q_B connected in cascade.

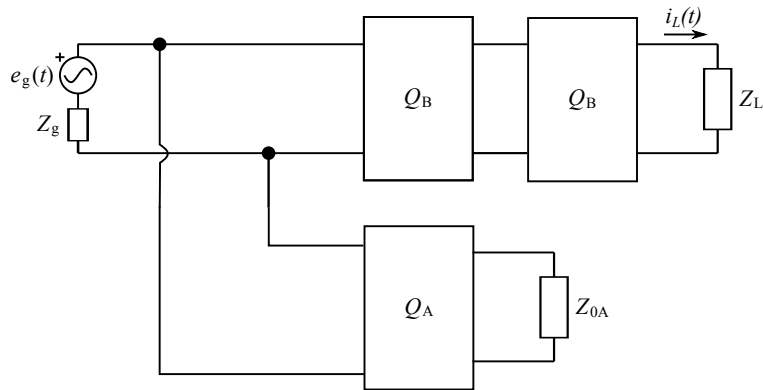


Figure 1

Data:

$$e_g(t) = 2 \cos(\omega t) \text{ V} \quad ; \quad Z_g = \frac{1+j}{4}$$

$$Q_B \begin{cases} A = \frac{1}{\sqrt{2}} \\ B = \frac{1+j}{\sqrt{2}} \Omega \end{cases}$$

Result

- $Z_{0B} = (1 - j) \Omega$ y $\gamma_B = j\frac{\pi}{4}$.
- $i_L(t) = \cos(\omega t - \frac{\pi}{2}) \text{ A}$.
- $\alpha_T = \alpha_I = 2\alpha_B = 0 \text{ Np}$.

Problem 3.17

In the circuit of Figure 1, quadripole Q_A is bilateral and symmetric, with transmission parameters $B = 4 \Omega$ and $D = 3$, and the source $(e_g(t), R_g)$ is delivering the maximum power. With these

conditions, we know that $i_x(t) = \cos(\omega t - \pi/4)$ A. Determine:

- The value of the characteristic impedance of quadripole Q_B , Z_{0B} .
- The value of γ_B for quadripole Q_B .
- The time-domain expression of the voltage at the output of quadripole Q_A , $v(t)$.
- Transmission and insertion loss for the quadripole Q_B . Justify your answer.

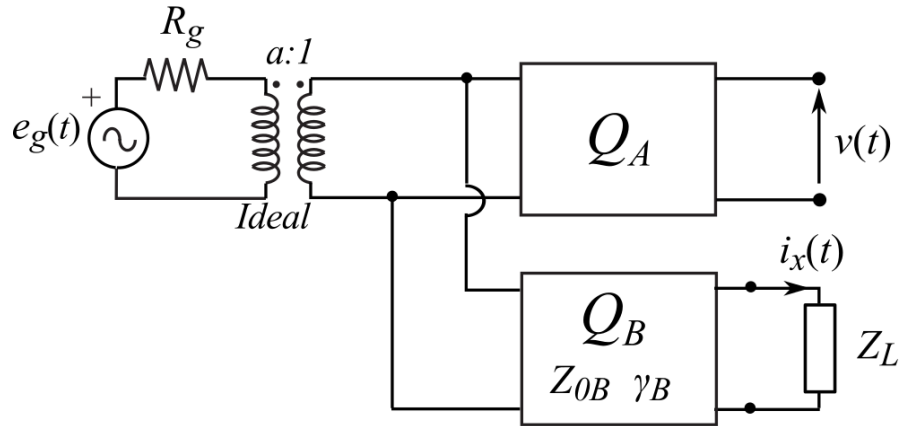


Figure 1

Data: $e_g(t) = 12 \cos(\omega t)$ V ; $R_g = 3 \Omega$; $a = 2$; $Z_L = Z_{0B}$

Result

- $Z_{0B} = \frac{3}{2} \Omega$
- $\gamma_B = \ln(2) + j\frac{\pi}{4}$
- $v(t) = \cos(\omega t)$ V
- $\alpha_T = \alpha_I = \Re\{\gamma_B\} = \alpha_B = \ln(2)$ Np