

PROBLEMS OF CHAPTER 4: INTRODUCTION TO PASSIVE FILTERS.

April 4, 2017

Problem 4.1

For the circuit shown in Figure 1(a) we want to design a filter with the zero-pole diagram shown in Figure 1 (b).

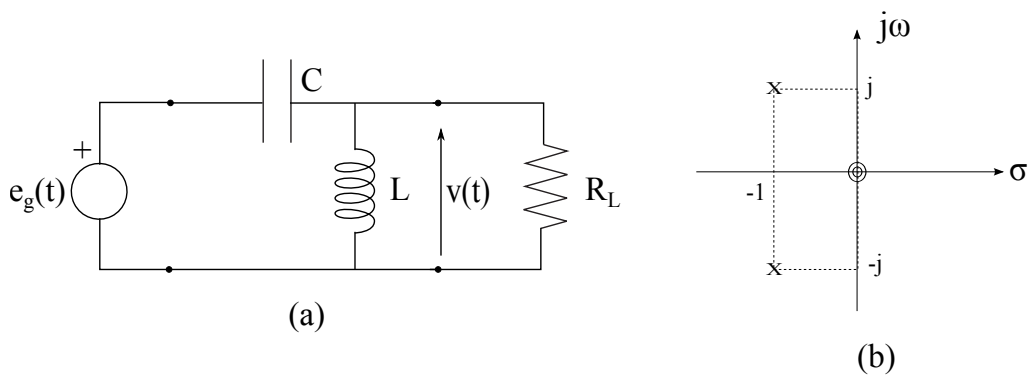


Figure 1

- a) Justify the type of filter proposed.
- b) Obtain the literal expression of the transfer function of the circuit, which is defined as $H(s) = \frac{V(s)}{E_g(s)}$, as a function of the components of the circuit.
- c) Obtain the values for L and C in order to build a circuit that satisfies the zero-pole diagram given. Consider $R_L = 1 \Omega$.

Result

a) High-pass filter.

b)
$$H(s) = \frac{s^2}{s^2 + \frac{1}{CR_L}s + \frac{1}{LC}}$$

c) $K = 1, C = \frac{1}{2} F, L = 1 H$

Problem 4.2

Given the circuit of Figure 1:

- Obtain the literal expression of the transfer function of the circuit, as a function of the components of the circuit, defined as $H(s) = \frac{V_2(s)}{E_g(s)}$.
- Plot the zero-pole diagram, and approximately represent the modulus of the frequency response of the filter. Justify the type of filter obtained.
- Compute $v_2(t)$ considering that $e_g(t) = 3 \cdot \text{sen}(4t) \text{ V}$.

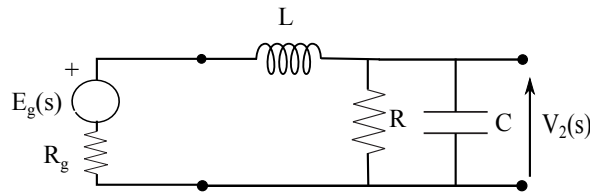



Figure 1

Data: $R = R_g = 1 \Omega$; $L = 1H$; $C = 1F$.

Result

$$\text{a) } H(s) = \frac{R}{R_g + R} \cdot \frac{\frac{R_g + R}{LCR}}{s^2 + \left(\frac{R_g}{L} + \frac{1}{RC}\right)s + \frac{R_g + R}{LCR}}$$

- Low-pass filter.

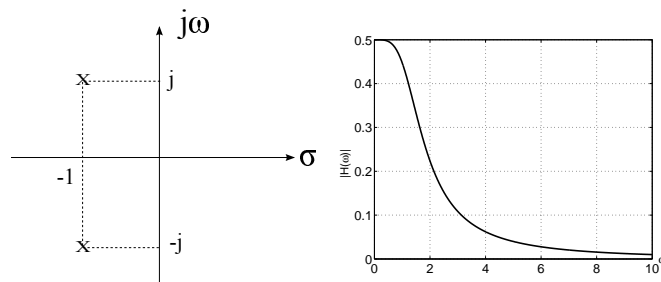

$$\text{c) } v_2(t) = 0.186 \text{ sen}(4t - 2.6224) \text{ V}$$

Problem 4.3

For the circuit in Figure 1(a), its transfer function $H(s) = \frac{V_{R_L}(s)}{E_g(s)}$ has the zero-pole diagram shown in Figure 1(b). Moreover, we know that $H(s)|_{s=0} = \frac{1}{2}$ and that $R_L = 1 \Omega$.


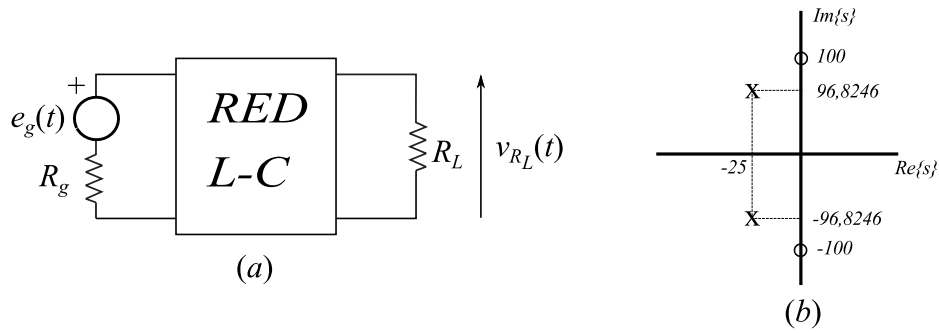


Figure 1

- Justify the type of filter provided.
- Computer the parameters of the filter:
 - H_0 and cur frequency.
 - Central frequency and bandwidth.
- Compute the value of R_g and a possible $L-C$ network specifying the value of all the components..

Result

- Bad-stop filter.
- $H_0 = \frac{1}{2}$, $\omega_0 = 100$ rad/s, $B = 50$ rad/s, $Q = \frac{\omega_0}{B} = 2$, $\omega_{C_i} = 78.078$ rad/s, $\omega_{C_s} = 128.078$ rad/s
- $R_g = 1 \Omega$, $C = 10$ mF, $L = 10$ mH

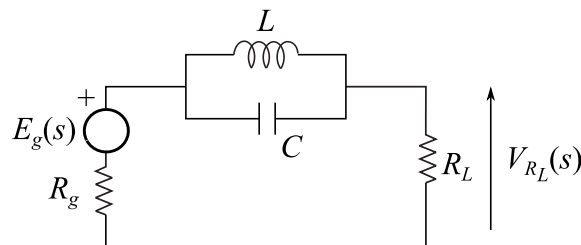

Problem 4.4

For the circuit in Figure 1 we can consider that the initial conditions are zero. Determine:

- The transfer function $H(s) = \frac{V_S(s)}{E_g(s)}$.
- Justify the type of filter provided, as well as its main characteristics (H_0 , cut frequency, ...).
- Draw the zero-pole plot and represent the modulus of the frequency response of the filter..

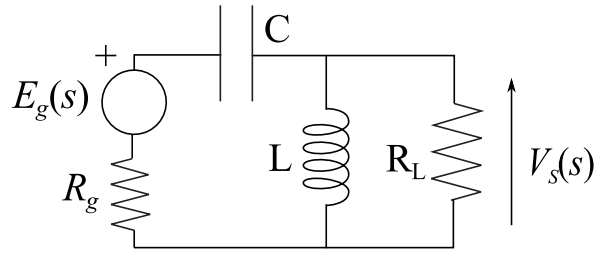


Figure 1


Data: $R_g = R_L = 1 \Omega$, $L = \frac{1}{2} \text{ H}$, $C = \frac{1}{2} \text{ F}$

Result


a) $H(s) = \frac{1}{2} \cdot \frac{s^2}{s^2 + 2s + 2}$

b) High-pass filter, $H_0 = \frac{1}{2}$, $\omega_c = \sqrt{2} \text{ rad/s}$.

c)

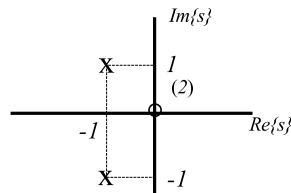

(a)

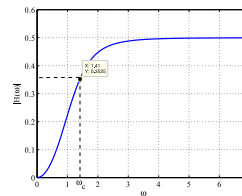

(b)

Problem 4.5

Given the circuit of Figure 1:

- Obtain the literal expression of the transfer function $H(s) = \frac{V_S(s)}{E_g(s)}$ as a function of R_L , C and L .
- Determine the value of C in order to get the minimum value of the modulus of the frequency response for $\omega_1 = 100 \text{ rad/s}$.
- Draw the zero-pole diagram and plot the modulus of the frequency response. Justify the type of filter obtained.

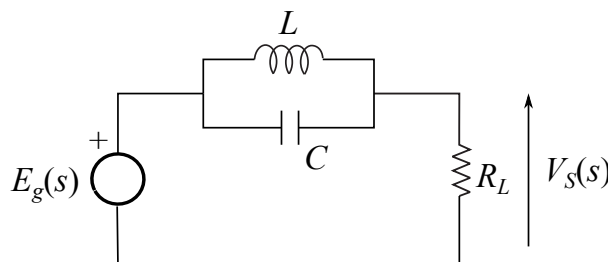


Figure 1

Data: $R_L = 2 \Omega$; $L = 10 \text{ mH}$

Result

a)
$$H(s) = \frac{s^2 + \frac{1}{LC}}{s^2 + \frac{1}{R_L C}s + \frac{1}{LC}}$$

b) $C = 10 \text{ mF}$

c) Stop-band filter.

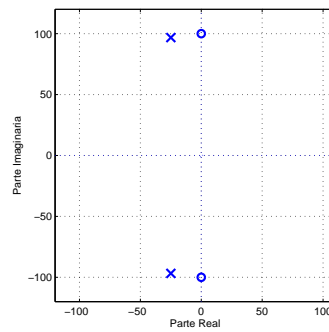


Figure 2

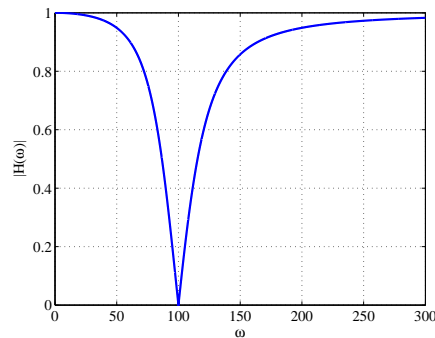


Figure 3

Problem 4.6

For the circuit in Figure 1:

- Obtain the literal expression of the transfer function $H(s) = \frac{V_S(s)}{E_g(s)}$. Justify the type of filter provided.
- Obtain the value of R_L in order to get a bandwidth of $B = 1 \text{ Krad/s}$.
- Plot the zero-pole diagram, and draw the modulus of the frequency response.

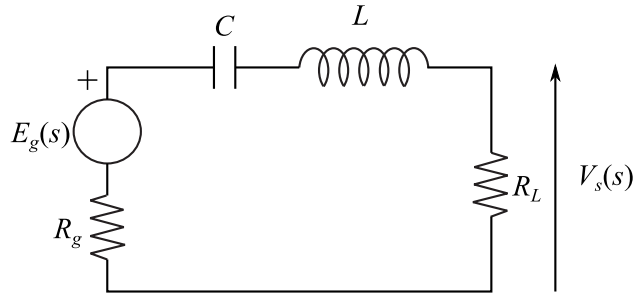


Figure 1

Data: $R_g = 50 \Omega$; $L = 100 \text{ mH}$; $C = 100 \text{ nF}$

Result

a) Band-pass filter.
$$H(s) = \frac{\frac{R_L}{L}s}{s^2 + \frac{R_g + R_L}{L}s + \frac{1}{LC}}$$

b) $R_L = 50 \Omega$

c) Zero-pole plot $|H(\omega)|$:

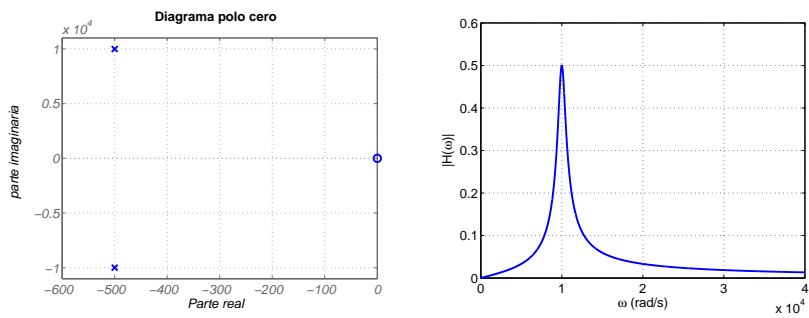


Figure 2

Problem 4.7

Given the circuit of Figure 1,

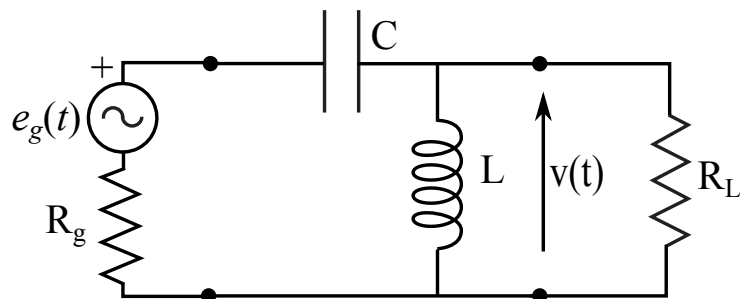


Figure 1

- a) Obtain the literal expression of the transfer function $H(s) = \frac{V(s)}{E_g(s)}$. Compare this transfer function with the general form of transfer functions for second-order filters $H(s) = \frac{a_2s^2 + a_1s + a_0}{s^2 + b_1s + b_0}$ and determine a_2, a_1, a_0, b_1, b_0 .
- b) Justify the type of filter provided considering the modulus of its frequency response.
- c) If $e_g(t) = 8 + 3 \cdot \cos(20t)V$, determine $v(t)$.

Data:

$$R_g = R_L = 1\Omega; \quad C = 10mF; \quad L = 10mH$$

Result

$$a) H(s) = \frac{V(s)}{E_g(s)} = \frac{R_L}{R_g + R_L} \cdot \frac{s^2}{s^2 + \frac{R_L}{R_g + R_L} \cdot \left(\frac{R_g}{L} + \frac{1}{R_L C} \right) s + \frac{R_L}{R_g + R_L} \cdot \frac{1}{LC}}$$

- b) High-pass filter.
- c) $v(t) = 0.12 \cdot \cos(20t + 2.7315) V$

Problem 4.8

Given the circuit of Figure 1,

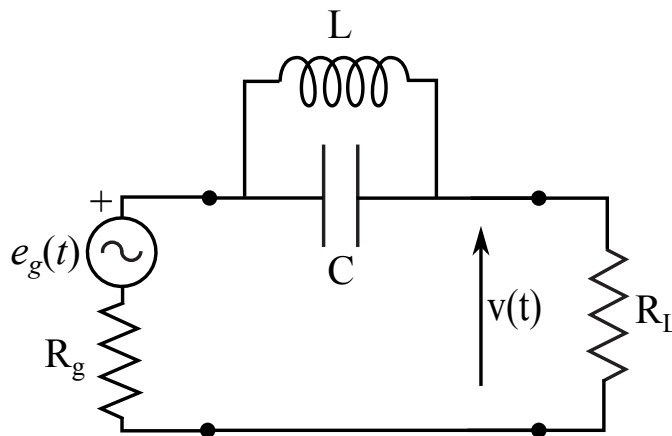


Figure 1

- a) Obtain the literal expression of the transfer function $H(s) = \frac{V(s)}{E_g(s)}$. Compare this transfer function with the general form of transfer functions for second-order filters $H(s) = \frac{a_2s^2 + a_1s + a_0}{s^2 + b_1s + b_0}$ and determine a_2, a_1, a_0, b_1, b_0 .
- b) Justify the type of filter provided considering the modulus of its frequency response.
- c) Compute the value of C in order to eliminate the frequency $\omega = 100 \text{ rad/s}$.
- d) If $e_g(t) = 8 \cdot \sin(100t) + 3 \cdot \cos(20t)V$, determine $v(t)$.

Data:

$$R_g = R_L = 2 \Omega; \quad L = 10mH$$

Result

a)

$$H(s) = \frac{V(s)}{E_g(s)} = \frac{\frac{R_L}{R_g + R_L} \cdot \left(s^2 + \frac{1}{LC} \right)}{s^2 + \frac{1}{(R_g + R_L)C}s + \frac{1}{LC}}$$

$$\begin{cases} a_2 = \frac{R_L}{R_g + R_L} \\ a_1 = 0 \\ a_0 = \frac{R_L}{R_g + R_L} \cdot \frac{1}{LC} \\ b_1 = \frac{1}{(R_g + R_L)C} \\ b_0 = \frac{1}{LC} \end{cases}$$

b) Band-stop filter.

c) $C = 10 \text{ mF}$.

d) $v(t) = 1.498 \cdot \cos(20t - 0.052)$ V

Problem 4.9

For the circuit in Figure 1, determine:

a) The literal expression of the transfer function $H(s) = \frac{V_s(s)}{E_g(s)}$.

b) Values of L and C to get a zero-pole plot of $H(s)$ like the one shown in Figure 2, considering a bandwidth of $B = 10^3 \text{ rad/s}$.

c) $v_s(t)$ when the signal provided by the source is $e_g(t) = 4 + 3 \cdot \text{sen} \left(10^3 t + \frac{\pi}{4} \right)$

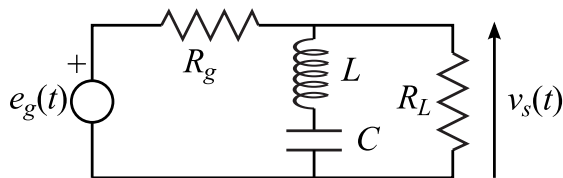


Figure 1

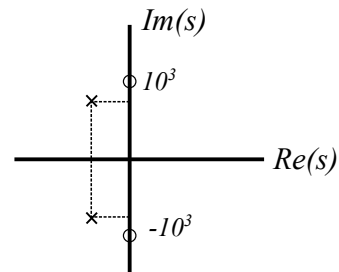


Figure 2

Data: $R_g = R_L = 1 \Omega$

Result

$$a) H(s) = \frac{V(s)}{E_g(s)} = \frac{R_L}{R_L + R_g} \cdot \frac{s^2 + \frac{1}{LC}}{s^2 + \frac{R_g R_L}{(R_L + R_g)L} \cdot s + \frac{1}{LC}}$$

$$b) L = \frac{1}{2} \text{ mH}, C = 2 \text{ mF}.$$

$$c) v_s(t) = 2 \text{ V}$$

Problem 4.10

For the circuit in Figure 1:

- Obtain the literal expression of the transfer function $H(s) = \frac{V_s(s)}{E_g(s)}$ and its zero-pole plot.
- Represent the modulus of the frequency response of the filter, indicating the most representative values (maximum value and its frequency, bandwidth). Justify the type of filter provided.
- Obtain the signal $v_s(t)$ when $e_g(t) = 3 \cdot \cos(10^4 t) + 3 \cdot \text{sen}(2 \cdot 10^4 t) \text{ V}$.

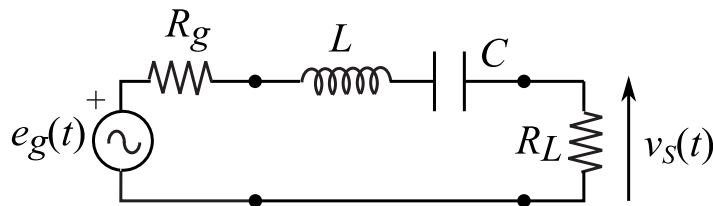


Figure 1
Data: $R_g = 0,5 \Omega$; $L = 1 \text{ mH}$; $C = 10 \mu\text{F}$; $R_L = 1,5 \Omega$

Result

$$a) H(s) = \frac{R_L}{R_g + R_L} \cdot \frac{\frac{R_g + R_L}{L} s}{s^2 + \frac{R_g + R_L}{L} s + \frac{1}{LC}}$$

$$s_{p1,2} = (-1 \pm j\sqrt{99}) \cdot 10^3 \quad ; \quad s_{C1} = 0 \quad ; \quad s_{C2} \rightarrow \infty$$

$$b) \text{ Pass-badn filter. } \omega_0 = 10^4 \text{ rad/s}, H(\omega = 10^4) = \frac{3}{4}, B = 2 \cdot 10^3 \text{ rad/s}.$$

$$c) v_s(t) = \frac{9}{4} \cdot \cos(10^4 t) + \frac{9}{2\sqrt{229}} \cdot \text{sen}(2 \cdot 10^4 t - 1.4382) \text{ V}$$