

PROBLEMS OF CHAPTER 5: RESONANT CIRCUITS.

Roberto Jiménez Martínez

May 3, 2018

PROBLEM 5.1

By varying the frequency of the source in the resonant circuit of Figura 1, we observe that for $\omega_0 = 10^3$ rad/s the current $i(t)$ is maximum. Obtain:

- Values for L and C in order to satisfy the conditions described.
- Time-domain expression for current $i(t)$ at the resonance frequency.
- Time-domain expressions for the current $i(t)$ when the frequency of the source is displaced 1% over, and 5% under the resonance frequency.

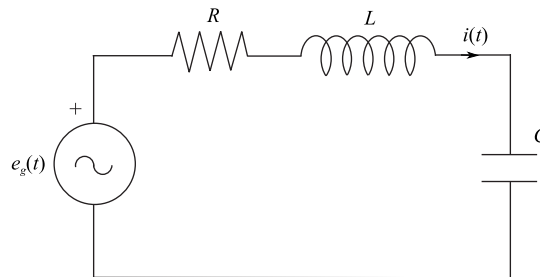


Figure 1

$$\text{Data : } e_g(t) = 20\sqrt{2} \text{ sen}(\omega t) \text{ V; } Q = 5; R = 2 \Omega$$

Result

- $L = 10$ mH, $C = 100$ μ F.
- $i(t) = 10\sqrt{2} \text{ sen}(10^3 t)$ A
- $i_{\delta_1}(t) = 9.95\sqrt{2} \text{ sen}(1.01 \cdot 10^3 t - 0.0997)$ A; $i_{\delta_2}(t) = 8.944\sqrt{2} \text{ sen}(0.95 \cdot 10^3 t + 0.464)$ A

PROBLEMA 5.2

$Q_b = 50$ for the inductor of the circuit shown in Figure 1 at the resonance frequency, $\omega_0 = 1$ Mrad/s. We also know that the anti-resonance circuit receives the maximum power at the resonance frequency. Obtain:

- Values of r , L and C .

- b) Time-domain expression of the current through the inductor, when the frequency of the source increases a 2% with respect to the resonance frequency.
- c) To triplicate the bandwidth of the circuit, we can use a resistor R . Indicate how to connect this resistor in the circuit, and determine its value.

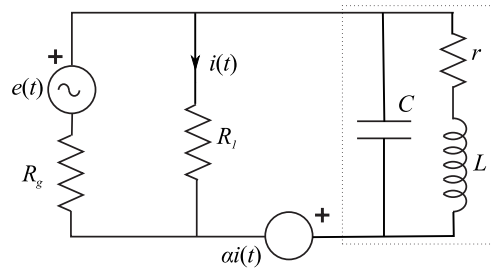


Figure 1

$$DATA: e(t) = 10 \text{ sen}(\omega t) \text{ V} \quad ; \quad R_g = 2 \text{ k}\Omega \quad ; \quad R_1 = 3 \text{ k}\Omega \quad ; \quad \alpha = \frac{1}{2} \text{ k}\Omega$$

Result

- a) $r = 0.4 \text{ }\Omega$; $L = 20 \text{ }\mu\text{H}$, $C = 50 \text{ nF}$.
- b) $i_L(t) = 86.6 \cdot \text{sen}(1.02 \cdot 10^6 t - 2.337) \text{ mA}$
- c) Resistencia en paralelo de valor $R = 250 \text{ }\Omega$

PROBLEM 5.3

For the resonant circuit of Figure 1, it is known that changing the frequency of the source E_g the following voltages are obtained::

$\omega = 101000 \text{ rad/s}$	$v(t) = \frac{1}{\sqrt{2}} \text{sen}(101000t - \frac{\pi}{4})$
$\omega = 99000 \text{ rad/s}$	$v(t) = \frac{1}{\sqrt{2}} \text{sen}(99000t + \frac{\pi}{4})$

Determine:

- a) Values of L and C .
- b) Value of the resistor to be connected in parallel with R_L in order to duplicate the bandwidth of the given circuit.

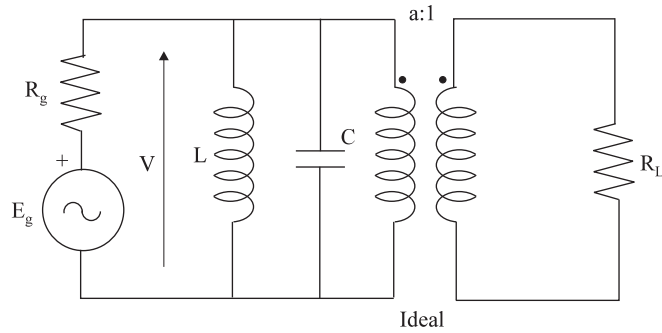


Figure 1

Data : $e_g(t) = 2\text{sen}(\omega t)$; $R_g = 10\text{k}\Omega$; $R_L = 2,5\text{k}\Omega$; $a = 2$

Result

- a) $L = 1\text{ mH}$; $C = 100\text{ nF}$.
- b) $R_P = 1250\ \Omega$.

PROBLEM 5.4

For the circuit in Figure 1, where we have a perfect transformer:

- a) Obtain the value of C_2 in order to get the maximum current I_L for the frequency $\omega = 10^7\text{ rad/s}$.
- b) Determine the value of R_L so as to receive the maximum power in the load, at the frequency of the previous section.
- c) Find the maximum and minimum frequencies for which the attenuation of the current I_L is under 6 dBs .

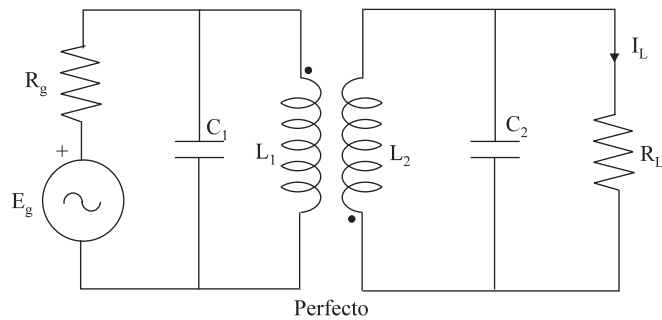


Figure 1

Data : $E_g = 40\text{ V}$; $R_g = 10\text{ k}\Omega$; $L_1 = 4\ \mu\text{H}$; $L_2 = 1\ \mu\text{H}$; $C_1 = 1.5\text{ nF}$

Result

- a) $C_2 = 4 \text{ nF}$.
- b) $R_L = \frac{5}{2} \text{ k}\Omega$.
- c) $\omega_i = 9.93 \cdot \text{Mrad/s}$; $\omega_s = 10.07 \cdot \text{Mrad/s}$

PROBLEM 5.5

In order to build the resonant circuit shown in Figure 1, we have the components shown in Figure 2. We also know that $R_g = 40 \Omega$ and $R_L = 80 \Omega$.

- a) Build a RLC series or a RLC parallel circuit to tune a signal whose frequency is in the interval defined by frequencies $\omega_1 = 975 \text{ rad/s}$ and $\omega_2 = 1025 \text{ rad/s}$.
- b) Justify how to duplicate the bandwidth of the circuit using some of the components NOT used in the previous section, and considering the same value of ω_0 .

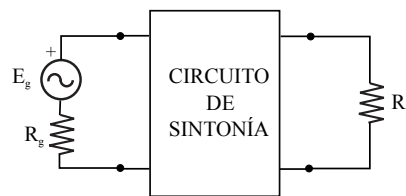


Figure 1

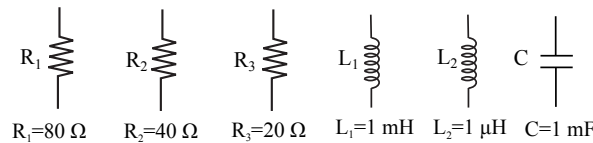


Figure 2

Result

- a) RLC parallel with L_1 , C and R_1 .
- b) Connect the resistor R_3 in parallel with the resonant circuit.

PROBLEM 5.6

We want to tune a signal of 10 Krad/s with a bandwidth at 3 dB of 100 rad/s . We use an antenna and the resonant circuit shown in Figure 1. The equivalent circuit corresponding to the antenna is the current source connected to terminals $A - B$, while the resonant circuit is the rest of the circuit from terminals $A - B$ towards the right.

- a) Determine the value of a and the resistor R in order to be able to tune the proposed signal.
- b) If we can change the values of R and C , justify if we have to increase, decrease or fix the values of R and/or C in order to tune a different signal with frequency 20 Krad/s , but maintaining the bandwidth at 3 dB of 100 rad/s .

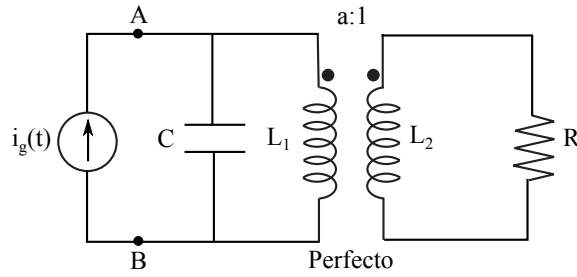


Figure 1

Data : $e_g(t) = 20 \text{ sen}(\omega t) \text{ V}$; $L_2 = 10 \text{ mH}$; $C = 16 \text{ }\mu\text{F}$.

Result

- a) $a = \frac{1}{4}$; $R = 10 \text{ k}\Omega$
- b) Decrease C . Increase R .

PROBLEM 5.7

For the circuit in Figure 1 we want to tune a signal provided by an antenna whose equivalent circuit is shown in Figure 1. At the resonance frequency it is known that the antenna delivers the maximum power.

- a) Obtain the quality factor and bandwidth at 3 dB of the resonant circuit.
- b) Determine the time-domain expressions for the voltage in the capacitor at the maximum and minimum frequencies that define the bandwidth.

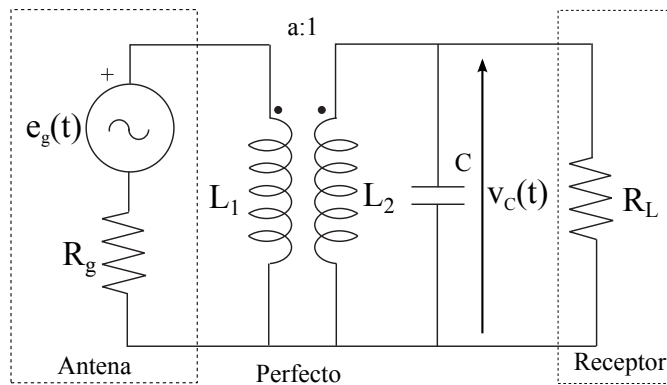


Figure 1

Data : $e_g(t) = 20 \text{ sen}(\omega t) \text{ V}$; $R_g = 200 \text{ k}\Omega$; $L_1 = 1 \text{ mH}$; $C = 4 \text{ nF}$; $R_L = 50 \text{ k}\Omega$.

Result

a) $Q = 100$; $B = 10$ krad/s.

b) $v_{C_1}(t) = \frac{5\sqrt{2}}{2} \cdot \text{sen} \left(995 \cdot 10^3 t + \frac{\pi}{4} \right)$ A; $v_{C_2}(t) = \frac{5\sqrt{2}}{2} \cdot \text{sen} \left(1005 \cdot 10^3 t - \frac{\pi}{4} \right)$ A

PROBLEM 5.8

For the circuit in Figure 1, we have analyzed its frequency response for the following situations:

- Situation 1: Load R_L is not connected.
- Situation 2: Load R_L is connected.

For these two situations, we obtained the plots (a and b), shown in Figure 2, which represent the normalized amplitude of voltage $v(t)$ ($|V|/|V|_{max}$), containing the bandwidths at 3 dB, whose values are shown in the figure.

- Justify what graph corresponds to each of the situations described (1 and 2).
- Obtain the values for L_1 and C .
- Determine the value of R_L .

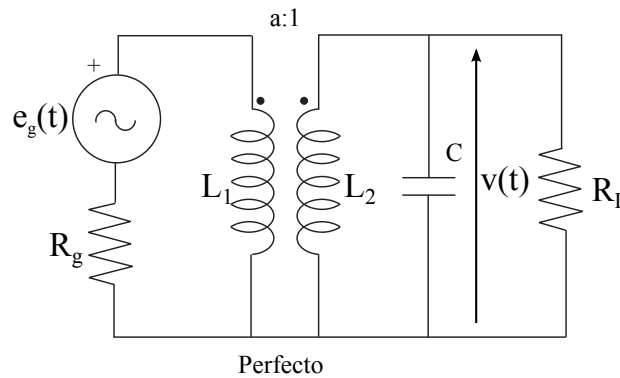


Figure 1

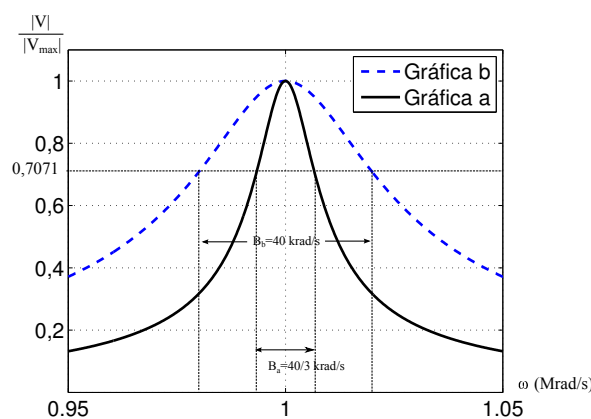


Figure 2

Data : $R_g = 675 \text{ k}\Omega$; $L_2 = 1 \text{ mH}$.

Result

- a) Situation 2: figure *b*. Situation 1: figure *a*.
- b) $L_1 = 9 \text{ mH}$; $C = 1 \text{ nF}$.
- c) $R_L = 37.5 \text{ k}\Omega$.

PROBLEM 5.9

When we change the value of capacitor C of the circuit shown in Figure 1, we observe that for the value of 2.5 nF voltage $V_1 = 48 \text{ V}$ is maximum, while $I_1 = 3 \text{ mA}$.

- a) Determine the value of L_1 and the quality factor for the circuit.
- b) Find the time-domain expression of the current passing through the load R_L , if we increase the frequency of the source by a 3.125 %
- c) Obtain the value of the resistor to be connected between points A and B in the circuit, in order to guarantee that the source ($e_g(t)$, R_g) delivers the maximum power at the resonance frequency.
- d) Determine the relation of the two bandwidths, before and after the connection of this new resistor between A and B .

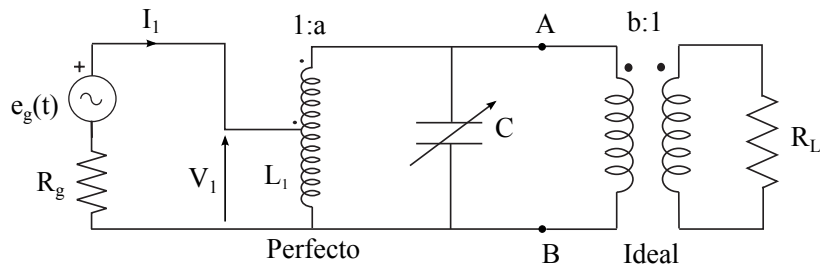


Figure 1

$$\text{Data : } e_g(t) = E_g \text{ sen}(10^6 t) \text{ V} \quad ; \quad R_g = 4 \text{ k}\Omega \quad ; \quad R_L = 16 \text{ k}\Omega \quad ; \quad b = 2$$

Result

- a) $L_1 = 100 \text{ }\mu\text{H}$; $Q = 32$.
- b) $i_{R_L}(t) = \frac{3}{\sqrt{5}} \cdot \text{sen}(1.03125 \cdot 10^6 t - \text{atan}(2)) \text{ mA}$.
- c) $R_p = \frac{64}{3} \text{ k}\Omega$
- d) $\frac{B'}{B} = \frac{5}{8}$

PROBLEM 5.10

In the circuit of Figure 1 we observe that the voltage $v(t)$ reaches a maximum for $\omega_0 = 500$ Krad/s, being the bandwidth defined at 3 dB, $B_{3dB} = 12.5$ Krad/s.

- Determine the values of C and R_L .
- Compute the time-domain expression of $v(t)$ when the source works at $\omega_1 = 505$ Krad/s.

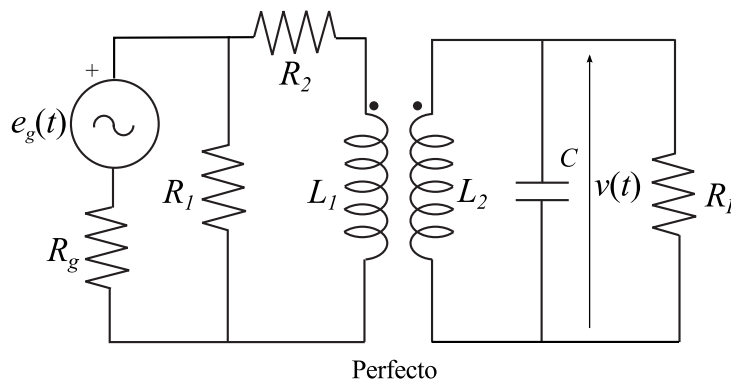


Figure 1

Data : $e_g(t) = 10 \text{ sen}(\omega t)$ V, $R_1 = R_g = 320 \text{ K}\Omega$, $R_2 = 200 \text{ K}\Omega$, $L_1 = 9 \text{ mH}$, $L_2 = 1 \text{ mH}$.

Result

- $C = 4 \text{ nF}$, $R_L = 40 \text{ K}\Omega$.
- $v(t) = 0.6507 \text{ sen}(505 \cdot 10^3 t - 06747)$ V.

PROBLEM 5.11

For the circuit of Figure 1, we know that for the frequency $\omega_0 = 1000$ rad/s the amplitude of the voltage of the capacitor $v_C(t)$ reaches a maximum value of 7.5 V. If we augment 10 rad/s that frequency, we observe that the amplitude of $v_C(t)$ decreases to 3.75 V.

- Obtain the quality factor of the circuit and the bandwidth defined at 3 dB.
- Determine the values for R , L and C .

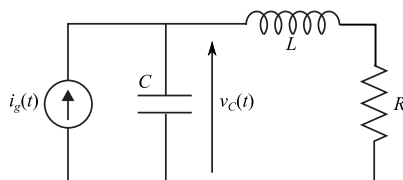


Figure 1

Data : $i_g(t) = \text{sen}(\omega t)$ mA

Result

- a) $Q = 50\sqrt{3}$, $B_{3\text{ dB}} = \frac{20\sqrt{3}}{3}$ rad/s.
- b) $L = 50\sqrt{3}$ mH, $C = \frac{20\sqrt{3}}{3}$ μF y $R = 1$ Ω .

PROBLEM 5.12

In the circuit of Figure 1, for $\omega_0 = 10$ Krad/s the modulus of the voltage of the resistor R , $|V_R|$ is 0. Knowing that for that frequency the value of the modulus of the voltage of the capacitor is $|V_C| = 5$ V:

- a) Obtain L , C and Q (the quality factor of the circuit).
- b) Determine the value of the modulus of the voltage of the resistor R , $|V_R|$ if we increase the frequency of the source a 1% with respect to the resonance frequency.

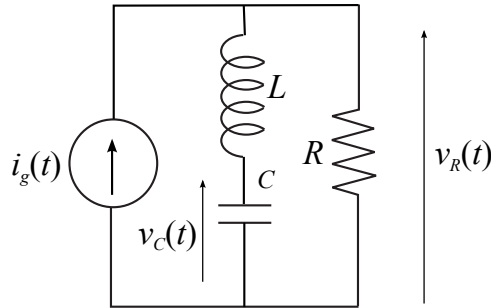


Figure 1

Data : $i_g(t) = \text{sen}(\omega t)$ mA; $R = 100$ Ω .

Result

- a) $C = 20$ nF, $L = \frac{1}{2}$ H, $Q = 50$.
- b) $v_R(t) = 50\sqrt{2} \text{sen}\left(1.01 \cdot 10^4 t + \frac{\pi}{2}\right)$ mV.
- c) $\alpha_2 = 48.5194$ dB.

PROBLEM 5.13

Using the resonant circuit in Figure 1, we want to tune a signal whose spectrum is defined by the frequencies $\omega_1 = 497500$ rad/s and $\omega_2 = 502500$ rad/s.

- a) Determine the values of L_1 and L_2 .
- b) Find the time-domain expression of current $i(t)$ if we increase the frequency a 0.5% with respect to the resonance frequency.

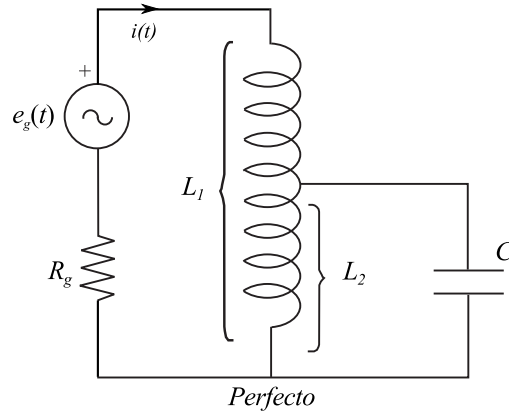


Figure 1

Data : $e_g(t) = \text{sen}(\omega t)$ V; $R_g = 100 \Omega$; $C = 8 \mu\text{F}$.

Result

- a) $L_1 = 2 \mu\text{H}$ y $L_2 = \frac{1}{2} \mu\text{H}$.
- b) $i(t) = 5\sqrt{2} \cdot \text{sen}\left(5.025 \cdot 10^5 t + \frac{\pi}{4}\right)$ mA

PROBLEM 5.14

For the circuit in Figure 1, it is known that for the frequency $\omega = 10^3 \text{ rad/s}$ the current $i(t)$ is maximum. Moreover, for that frequency, the source ($e_g(t), R_g$) delivers the maximum power.

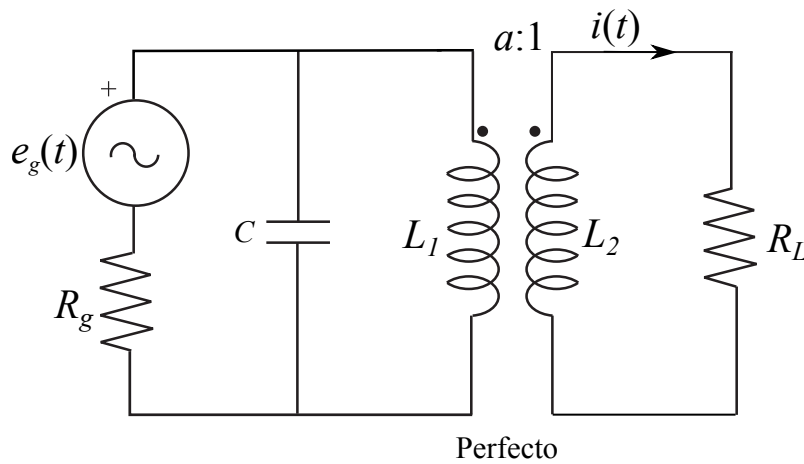


Figure 1

- a) Determine the values of L_1 and C .
- b) Find the quality factor and the bandwidth of the resonant circuit.

- c) Obtain the time-domain expression for $i(t)$ when the frequency of the source is increased a 1% with respect to the resonance frequency.

Data:

$$e_g(t) = 20 \cdot \text{sen}(\omega t) \text{ V}; \quad R_g = 100 \, \Omega; \quad R_L = 25 \, \Omega; \quad L_2 = 250 \mu\text{H}$$

Result

a) $L_1 = 1 \text{ mH}$ y $C = 1 \text{ mF}$.

b) $Q = 50$ and $B_{3 \text{ dB}} = 20 \text{ rad/s}$.

c) $i(t) = \frac{\sqrt{2}}{10} \cdot \text{sen} \left(1.01 \cdot 10^3 t - \frac{\pi}{4} \right) \text{ A}$

PROBLEM 5.15

With the circuit in Figure 1, we want to tune a set of frequencies centered at $\omega_0 = 10^6 \text{ rad/s}$.

- a) Determine the value of L_1 .
- b) Bandwidth of the circuit and the maximum and minimum frequencies.
- c) Voltage V (modulus and phase) if we increase the frequency a 2% with respect to ω_0 .
- d) We would like to double the bandwidth. What component should we include in the circuit? Where should we include it? What should be its value?

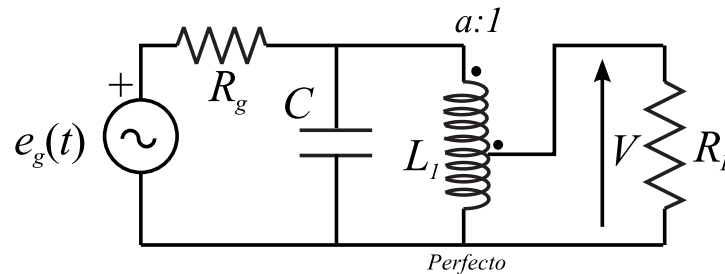


Figure 1

Data : $e_g(t) = 10 \text{ sen}(\omega t) \text{ V}; \quad C = 4 \text{ nF}; \quad R_g = 50 \text{ k}\Omega; \quad a = 5; \quad R_L = 2 \text{ k}\Omega$

Result

a) $L = \frac{1}{4} \text{ mH}$

b) $B|_{3\text{dB}} = 10^4 \text{ rad/s}$.

$$\begin{cases} \omega_{c_i} = 950 \text{ krad/s} \\ \omega_{c_s} = 1050 \text{ krad/s} \end{cases}$$

c) $V \simeq \frac{1}{\sqrt{17}} \cdot e^{-j3.258} \text{ V}$

d) $R_x = R_T = 25 \text{ k}\Omega$