



UNIVERSIDAD DE ALCALÁ

Escuela Politécnica Superior
Departamento de Teoría de la Señal y Comunicaciones
Grados TIC
Subject: Circuit Analysis - P.E.I. 1
Course: 1st. Group: E Grupo Pequeño: -
Surnames:
Name:
D.N.I.:
Date: 1 – March – 2017

--	--	--	--

Instructions

- **Fill in all the data required in the first page.**
- The exam consists on 3 problems. Check that you have all of them.
- The duration of the exam is 1 hours 30 minutes.
- Books or notes are not allowed.
- Read carefully each problem before starting to answer.
- It is compulsory to write your name on each sheet. Any sheet without a name will be **immediately** removed.
- Start a new page for each problem. Before delivering the exam sort the pages.
- **SWITCH OFF AND KEEP AWAY THE MOBILE PHONE.**
- The grading of the exam will take into account the following aspects:
 1. Clean and ordered responses.
 2. **Explanation and reasoning in accordance to the studied theory.**
 3. **Explanations of each performed step in a resolution.**
 4. Simplicity and efficiency of the adopted solution.
 5. The obtained results.

PROBLEM 1 (2.5 points)

Perform the association between the circuits shown in figure 1 and the respective transient responses of the voltage $v_{AB}(t)$ shown in figure 2. **REASON** why do you do these associations.

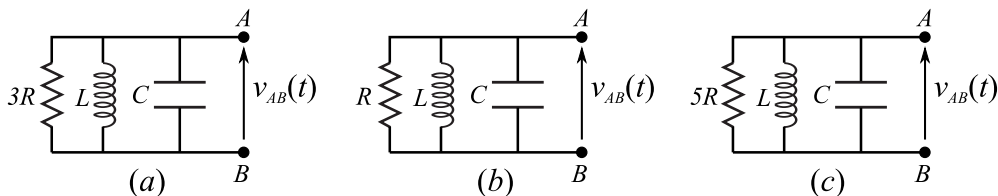


Figura 1

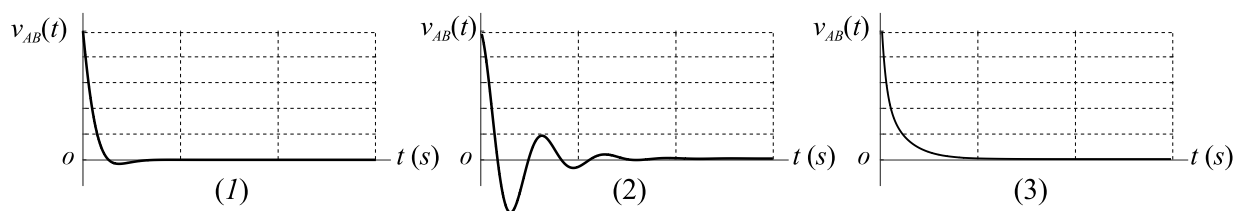


Figura 2

PROBLEM 2 (2.5 points)

In the circuit of the figure 1, the switcher is in position (1) since $t = -\infty$. At $t = 0$ s, it switches to position (2) staying in this position for the rest of the time. It is known that the circuit is a RC -circuit made of only one R and one C , and that the voltage at the circuits terminals for $t > 0$ is:

$$v(t) = 5 \left(1 - e^{-\frac{t}{2}} \right)$$

Determine the internal structure of the RC -circuit and the values of their elements.

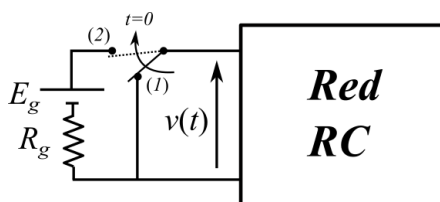


Figura 1

DATA:

$$E_g = 10\text{V} \quad ; \quad R_g = 5 \Omega$$

PROBLEM 3 (5 points)

In the circuit of the figure 1, the switcher is in position (1) since $t = -\infty$. At $t = 0$ s, it switches to position (2) staying in this position for the rest of the time. Calculate:

- Initial conditions at the switching time.
- Obtain the time evolution of the current $i_L(t)$ for $t > 0$ s.
- Calculate the value of \mathbf{R} so that the circuit has a critical transient response.

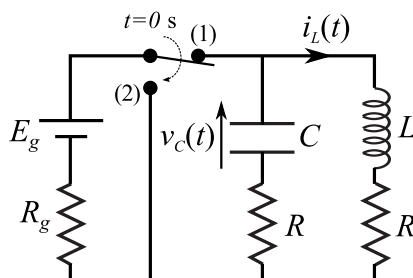


Figura 1

DATA:

$$E_g = 4V \ ; \ R_g = R = 2 \ \Omega \ ; \ L = 2 \text{ H} \ ; \ C = \frac{1}{8} \text{ F}$$