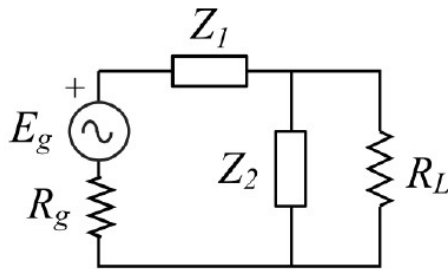


EXAMPLE OF TEST OF THE UNITS 2 AND 3

Grading criteria:

- For correct answer: 2 points
- For wrong answer: -2/3 points
- No answer: 0 points.

1. Value of Z_1 that makes the real generator (E_g, R_g) deliver the maximum power in the following circuit




Datos: $\begin{cases} R_g = 100 \Omega \\ Z_2 = 200j \Omega \\ R_L = 200 \Omega \end{cases}$

Figura 1


- (a) $Z_1 = 100j \Omega$
- (b) $Z_1 = 200j \Omega$
- (c) $Z_1 = -200j \Omega$
- (d) $Z_1 = -100j \Omega$

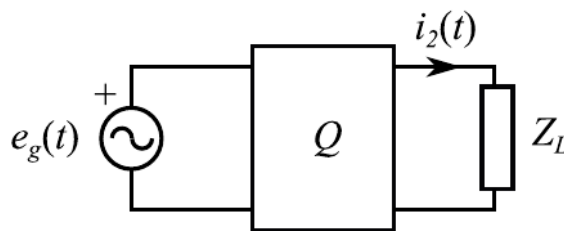2. Knowing two of the parameters “y” ($y_{22} = 0$ and $y_{21} = 1\Omega^{-1}$) of the quadripole, Q, of the figure, and knowing that $e_g(t) = 2 \sin(\omega t)$ V, then the current $i_2(t)$ is




- (a) $i_2(t) = 2 \cdot \text{sen}(\omega t)$ A.....
- (b) $i_2(t) = 2 \cdot \text{sen}(\omega t + \pi)$ A.....
- (c) $i_2(t) = 0$ A.....
- (d) Can not be obtained without knowing y_{11} and y_{12} .

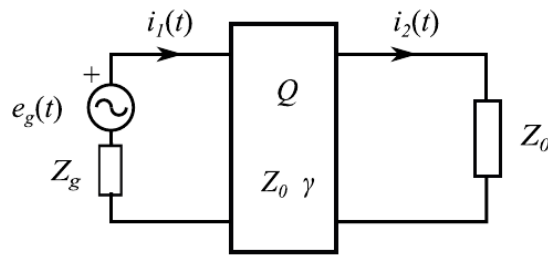3. In the circuit of the figure $i_1(t) = 6 \cos(\omega t + \frac{\pi}{4})$ A and $i_2(t) = 3 \cos(\omega t - \frac{\pi}{4})$ A, then the image parameters are




- (a) $\gamma = \text{Ln}(2) + j\frac{\pi}{2}$
- (b) $\gamma = \text{Ln}(2) + j\frac{\pi}{4}$
- (c) $\gamma = \text{Ln}(2) - j\frac{\pi}{2}$
- (d) $\gamma = \text{Ln}(2)$

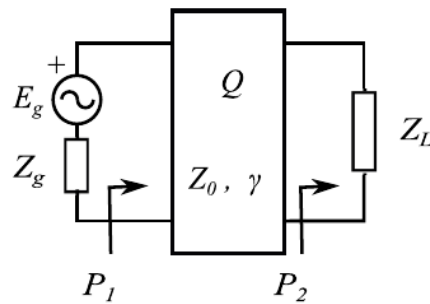4. In the circuit of the figure, where the quadripole, Q, is reciprocal and symmetric, with image parameters $Z_0(\Re\{Z_0\} \neq 0)$ and $\gamma = \alpha + j\beta(\beta \neq 0)$, we can say that



- (a) Independently of the value of Z_g , if $Z_L = Z_0$, then $P_1 = P_2 \cdot e^{2\gamma}$.
- (b) Independently of the value of Z_L , if $Z_g = Z_0$, then $P_1 = P_2 \cdot e^{2\gamma}$.
- (c) Independently of the value of Z_g , if $Z_L = Z_0$, then $P_1 = P_2 \cdot e^{2\alpha}$.
- (d) Independently of the value of Z_L , if $Z_g = Z_0$, then $P_1 = P_2 \cdot e^{2\alpha}$.

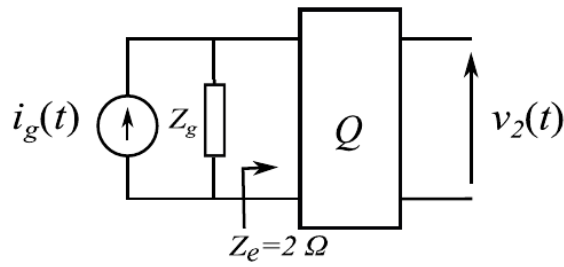5. For the circuit of the figure the quadripole, Q , is reciprocal and symmetrical quadripole, and the following values are known: $Z_e = 2\Omega$, $v_2(t) = \sin(\omega t - \pi)\text{V}$, $i_g(t) = 3 \sin(\omega t)$ and $Z_g = 1\Omega$. The “g” parameters of the quadripole are:



- (a) $g_{11} = \frac{1}{2} \Omega^{-1}$, $g_{12} = \frac{1}{2}$, $g_{21} = -\frac{1}{2}$, $g_{22} = \frac{3}{2} \Omega$
- (b) $g_{11} = 2 \Omega^{-1}$, $g_{12} = \frac{1}{2}$, $g_{21} = -\frac{1}{2}$, $g_{22} = \frac{1}{2} \Omega$
- (c) $g_{11} = \frac{1}{2} \Omega^{-1}$, $g_{12} = -\frac{1}{2}$, $g_{21} = \frac{1}{2}$, $g_{22} = \frac{3}{2} \Omega$
- (d) None of the previous one.

Answers:

1. (d)

2. (b)

3. (a)

4. (c)

5. (a)

(do not memorize the answers to the solutions, try do understand and if you have questions please ask your teacher !!)