 UNIVERSIDAD DE ALCALÁ	Escuela Politécnica Superior
	Departamento de Teoría de la Señal y Comunicaciones
	Grados TIC
	Asignatura: Análisis de Circuitos (PEI-1)
	Curso: 1º. Grupo: E
	Name:
	Surname:
D.N.I.:	
Fecha: 07 of March of 2018	

Exame type: A

PEI-1. Test (5 points)

Instructions


- The five questions of the test are graded as follows:
 - Correct answer: 1 point.
 - Incorrect answer: $-\frac{1}{3}$ of a point.
 - No answer: 0 points.
- The answers to the questions have to be marked in the following table. Mark with a cross the right answers and draw a circle on the cross to cancel it. The answers not marked on the table will not be considered.

ANSWERS TO THE TEST

Question	Answer			
	a	b	c	d
Question 1				
Question 2				
Question 3				
Question 4				
Question 5				

Questions

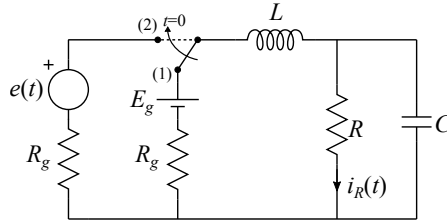
1. In the circuit of the figure, the switcher is in position (1) since $t = -\infty$. At $t = 0$ it changes to position (2), remaining on this position.



DATA: $E_g = 10 \text{ V}$; $e(t) = 10 \cdot e^{-2t} \cdot \cos(3t) \text{ V}$; $R_g = R = 5 \Omega$; $L = 1 \text{ H}$; $C = 2 \text{ F}$.
 The value of the current through the resistance R at $t = 0^+$ [$i_R(t = 0^+)$] is:

- (a) $i_R(t = 0^+) = 0 \text{ A}$
- (b) $i_R(t = 0^+) = 1 \text{ A}$
- (c) $i_R(t = 0^+) = 2 \text{ A}$
- (d) Can not be calculate with the given data.....

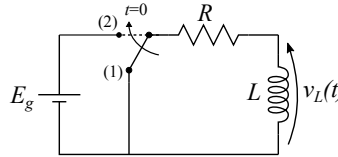
2. In the circuit of the figure, the switcher is in position (1) since $t = -\infty$. At $t = 0$ it changes to position (2), remaining on this position.



The value of the voltage at the coil at $t = 0^+$ is:

- (a) $v_L(t = 0^+) = 0 \text{ V}$, since the value of the voltage at the coil does not change abruptly.
- (b) $v_L(t = 0^+) = 0 \text{ V}$, sinc the value of the current through the coil at $t = 0^+$ is zero.
- (c) $v_L(t = 0^+) = E_g$
- (d) $v_L(t = 0^+) = \frac{E_g}{R}$

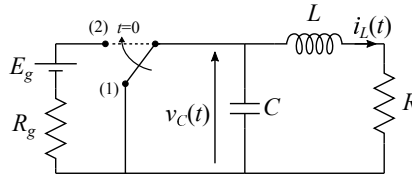
3. In the circuit of the figure, the switcher is in position (1) since $t = -\infty$. At $t = 0$ it changes to position (2), remaining on this position.



which of the following affirmations is the correct one?

- (a) The voltage at the capacitor, $v_C(t)$, is zero at $t = 0$ and $\frac{E_g \cdot R}{R_g + R}$ for $t \rightarrow \infty$
- (b) The initial conditions of the two elements that store energy are different than zero.
- (c) The current trough the coil, $i_L(t)$, is zero for $t = 0$ and also for $t \rightarrow \infty$
- (d) The voltage at the capacitor, $v_C(t)$, is zero for $t = 0$ and also for $t \rightarrow \infty$

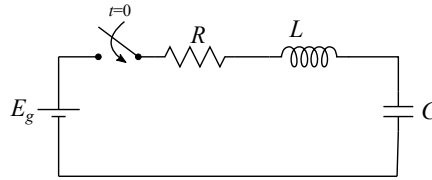
4. In the circuit of the figure, where $R_g = R$, there is no energy stored before the switcher is closed. It is known that $L = 10^{-1}$ H and $C = 10^{-3}$ F.



Which value should have R so that the circuit becomes critically damped?

- (a) $R = 0 \Omega$
- (b) $R = 5 \Omega$
- (c) $R = 20 \Omega$
- (d) $R = 10 \Omega$

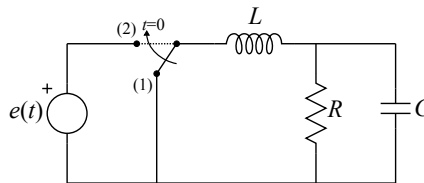5. In the circuit of the figure, the switcher is in position (1) since $t = -\infty$. At $t = 0$ it changes to position (2), remaining in this position. Under these conditions the damping ratio of the circuit is $\xi = 1$.



If the value of the resistance R is doubled:

- (a) The damping coefficient will not changed ($\xi = 1$).....
- (b) The damping coefficient will increase ($\xi > 1$).....
- (c) The damping coefficient will decrease ($\xi < 1$).....
- (d) The damping coefficient can not be predicted without knowing $e(t)$

Answer Key for Exam A

1. (b)
2. (c)
3. (a)
4. (d)
5. (c)