

# U1. Transient circuits response

Circuit Analysis, Grado en Ingeniería de Comunicaciones  
Curso 2016-2017

Philip Siegmann ([philip.siegmann@uah.es](mailto:philip.siegmann@uah.es))  
Departamento de Teoría de la Señal y Comunicaciones





# Index

- Recall
- Goals and motivation
- Linear differential equation (Recall)
- The homogeneous solution
- 1st and 2nd order linear differential equations
- Examples of 2nd order circuits
- Initial conditions
- Transient responses (example on 2<sup>nd</sup> order circuit)
- Cause of the transient responses
- Analysis using Laplace transform

$$\left( v(t) = \frac{dW(t)}{dq}, i(t) = \frac{dq(t)}{dt} \right)$$



# Recall

- Relation between  $i(t)$  and  $v(t)$  for the passive elements  $R, L, C$

- For  $R$ :  $v(t) = Ri(t)$

- For  $C$ :  $q(t) = Cv_C(t) \Rightarrow i_C(t) = C \frac{dv_C(t)}{dt}$




- For  $L$ :  $v_L(t) = L \frac{di_L(t)}{dt}$

- Energy in these elements:

- Dissipated in  $R$ :  $W_R(t) = R \int i_R^2(t) dt$

- Stored in  $C$  and  $L$ :
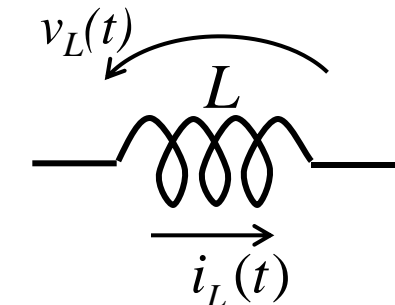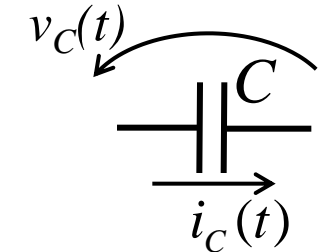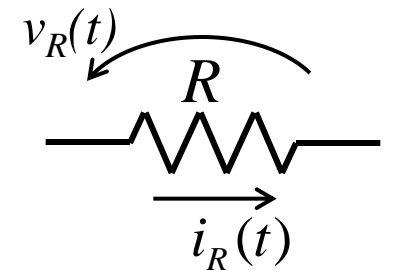
$$W_C(t) = \frac{1}{2} C (v_C(t))^2 \quad W_L(t) = \frac{1}{2} L (i_L(t))^2$$






# Goals

- We want to solve circuits for whatever applied source (not only DC and Sinusoidal Steady State)
  - Direct resolution in the time domain
  - Resolution using Laplace transforms
- In particular we want to understand what happens when an abrupt change takes place in the circuit, which will produce the transient response.



# Motivation

- Signal transmission

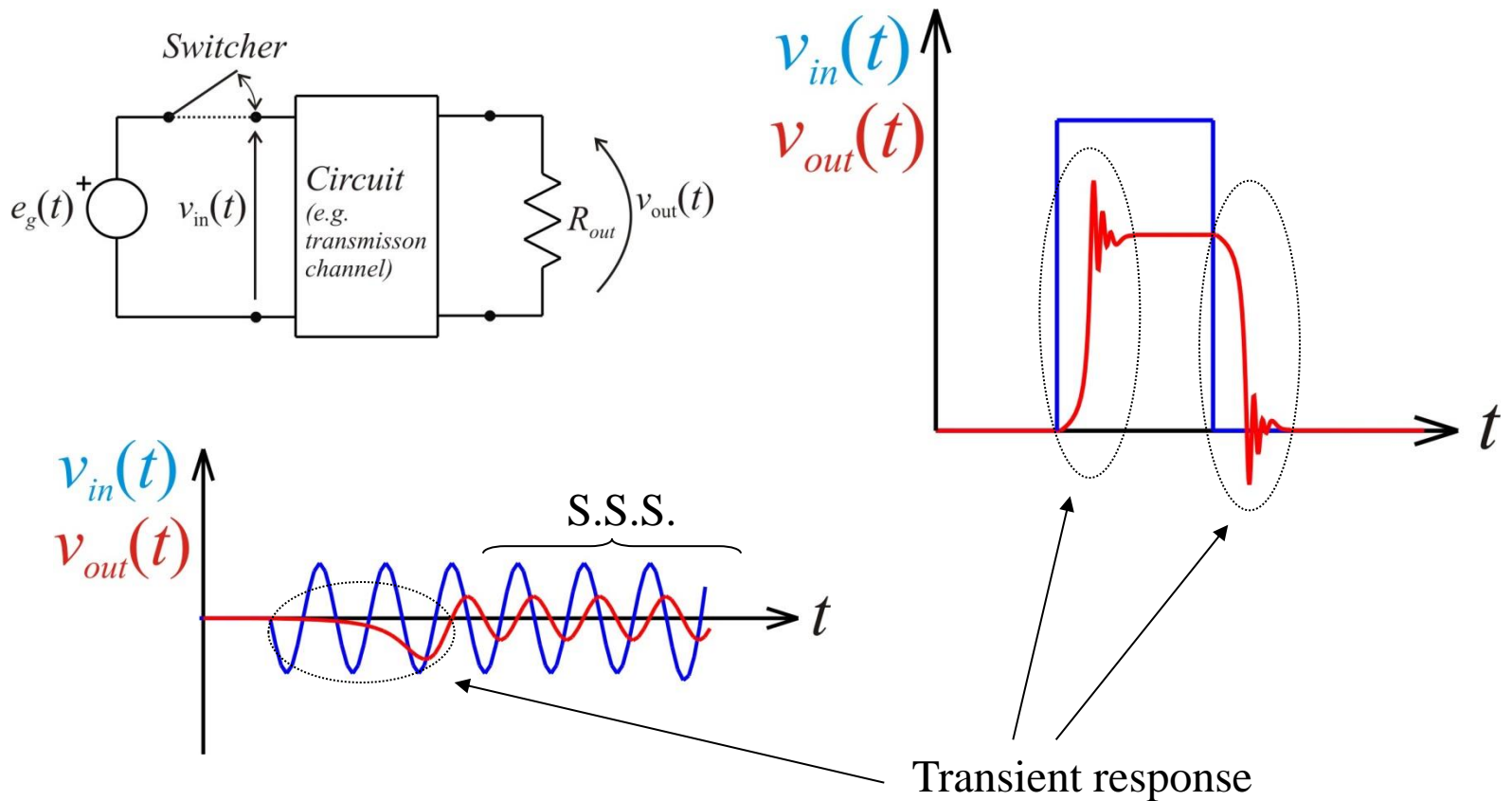



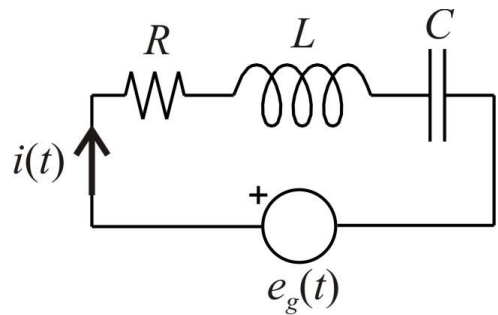
# Examples of 2nd order circuits

- RLC-serial

([http://en.wikipedia.org/wiki/RLC\\_circuit](http://en.wikipedia.org/wiki/RLC_circuit))




$$v_R(t) + v_L(t) + v_C(t) = e_g(t) \quad (\text{Energy conservation})$$

$$\Rightarrow Ri(t) + L \frac{di(t)}{dt} + \frac{1}{C} q(t) = e_g(t)$$

$$\Rightarrow \frac{d^2 i(t)}{dt^2} + \frac{R}{L} \frac{di(t)}{dt} + \frac{1}{LC} i(t) = \frac{1}{L} \frac{de_g(t)}{dt}$$

- RLC-parallel

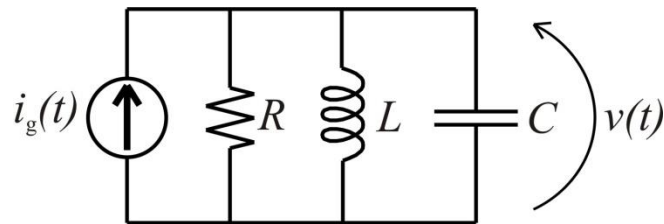

$$\frac{d}{dt} \{i_R(t) + i_L(t) + i_C(t) = i_g(t)\} \quad (\text{Charge conservation})$$

$$\Rightarrow \frac{1}{R} \frac{dv(t)}{dt} + \frac{1}{L} v(t) + C \frac{d^2 v(t)}{dt^2} = \frac{di_g(t)}{dt}$$

$$\Rightarrow \frac{d^2 v(t)}{dt^2} + \frac{1}{RC} \frac{dv(t)}{dt} + \frac{1}{LC} v(t) = \frac{1}{C} \frac{di_g(t)}{dt}$$



# Transient response

- Response of a circuit (voltage or current) when an abrupt change happens (e.g. switching)
- Time evolution until achieving a new equilibrium
- The transition function follows exponential variations (decreasing or increasing, fluctuating or no fluctuating)
- They are solutions of linear differential equations



# General solution

Linear differential equation of order  $n$ :

$$\frac{d^n y(t)}{dt^n} + a_{n-1} \frac{d^{n-1} y(t)}{dt^{n-1}} + \dots + a_0 y(t) = g(t),$$
$$y(t) = y_h(t) + y_p(t),$$

$y_h(t)$  is the solution for  $g(t)=0$ : the Complementary, natural or homogeneous solution. Gives the *transient behavior* of the circuit due to the passive elements. It is dependent of the initial conditions.

$y_p(t)$  is a particular solution for the given source or forcing function  $g(t)$ . The particular solution looks like the forcing function, e.g.:

- If  $g(t)$  is constant, then  $y_p(t)$  is constant
- If  $g(t)$  is sinusoidal, then  $y_p(t)$  is sinusoidal (i.e. the S.S.S.)

The homogeneous solution decreases exponentially so that

$$y(t \rightarrow \infty) \rightarrow y_p(t)$$





# The homogeneous solution

$y_h(t)$  is the solution for  $g(t)=0$  (external energy supply =0)

The solution has the form:  $y_h(t)=A \cdot \exp(st)$  (“Ansatz”)

$$\text{since: } \frac{d^k}{dt^k} (A e^{st}) = A s^k e^{st}$$

$$\Rightarrow s^n + a_{n-1}s^{n-1} + \dots + a_0 = 0, \text{ characteristic polynomial equation}$$

$$\Rightarrow s = \{s_1, s_2, \dots, s_n\} \quad (\text{“Eigenwerte”})$$

$$\Rightarrow y_h(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + \dots + A_n e^{s_n t} = \sum_{k=1}^n A_k e^{s_k t}$$

$A_1, A_2, \dots$  are obtained with the **initial** (and/or boundary) **conditions**



# 1st and 2nd order linear differential equations

## 1st order

$$\frac{dy(t)}{dt} + a_0 y(t) = g(t),$$

$$a_0 = \frac{1}{\tau}$$

For circuits containing one energy storage element ( $C$  or  $L$ )

$\tau$  is a time constant (how fast  $y_h(t)$  decreases)

## 2nd order

$$\frac{d^2 y(t)}{dt^2} + a_1 \frac{dy(t)}{dt} + a_0 y(t) = g(t),$$

$$a_1 = 2\xi\omega_n$$

$$a_0 = \omega_n^2$$

For circuits containing two independent energy storage element

$\xi$  is called the **damping ratio** (accounts for the energy loss)

$\omega_n$  is called the **natural frequency** (maximum energy storage)


(<http://en.wikipedia.org/wiki/Damping>)


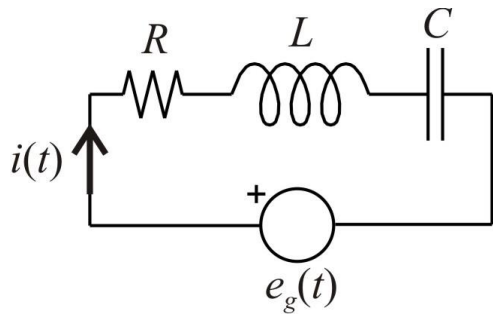
# Example of 2º orden circuits

- RLC-serial


([http://en.wikipedia.org/wiki/RLC\\_circuit](http://en.wikipedia.org/wiki/RLC_circuit))



$$\frac{d^2 i(t)}{dt^2} + \frac{R}{L} \frac{di(t)}{dt} + \frac{1}{LC} i(t) = \frac{1}{L} \frac{de_g(t)}{dt}$$

$$\Rightarrow \omega_n = \frac{1}{\sqrt{LC}}, \xi = \frac{R}{2\omega_n L}$$

- RLC-parallel

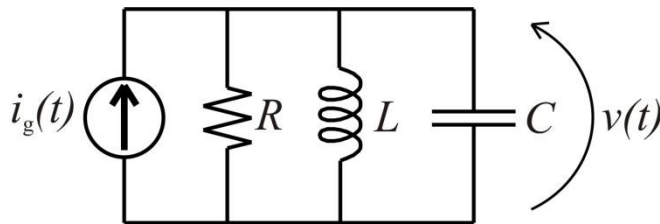


$$\frac{d^2 v(t)}{dt^2} + \frac{1}{RC} \frac{dv(t)}{dt} + \frac{1}{LC} v(t) = \frac{1}{C} \frac{di_g(t)}{dt}$$

$$\Rightarrow \omega_n = \frac{1}{\sqrt{LC}}, \xi = \frac{1}{2R\omega_n C}$$



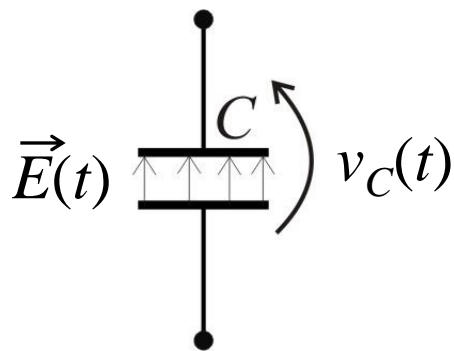
# Initial conditions

- For each energy storage element we need an initial condition (at  $t=t_0$ ):
  - For  $C$ :  $v_C(t=t_0) = V_0$
  - For  $L$ :  $i_L(t=t_0) = I_0$



$$W_L(t) = \frac{1}{2} C (v_C(t))^2$$

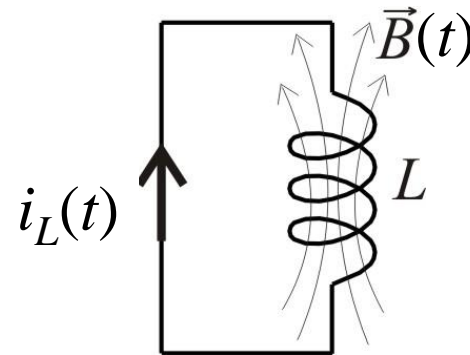

$$W_L(t) = \frac{1}{2} L (i_L(t))^2$$



# Condiciones iniciales

- When an abrupt change happens at  $t=t_0$  in a circuit, there is always continuity in the variation of the energies in  $C$  and  $L \Rightarrow$ 
  - There is continuity in the voltage at  $C$ :

$$v_C(t_0^-) = v_C(t_0^+) \quad (\text{not so for the current } i_C(t))$$

Justo antes de  $t_0$

Justo después de  $t_0$

- There is continuity in the current through  $L$ :

$$i_L(t_0^-) = i_L(t_0^+) \quad (\text{not so for the voltage } v_L(t))$$



# Example of transient response

## Discharge of the capacitor

Initial conditions at  $t = 0$ :

$$\begin{cases} i(0) = 0 \\ v_C(0) = E_g \end{cases}$$

**For  $t \geq 0$**

$$Ri(t) + \frac{1}{C}q(t) + L\frac{di(t)}{dt} = 0,$$

$$\Rightarrow \frac{d^2i(t)}{dt^2} + \frac{R}{L}\frac{di(t)}{dt} + \frac{1}{LC}i(t) = 0,$$


Homogeneous (sourcefree) equation with solutions of the form

$$i(t) = Ae^{st},$$

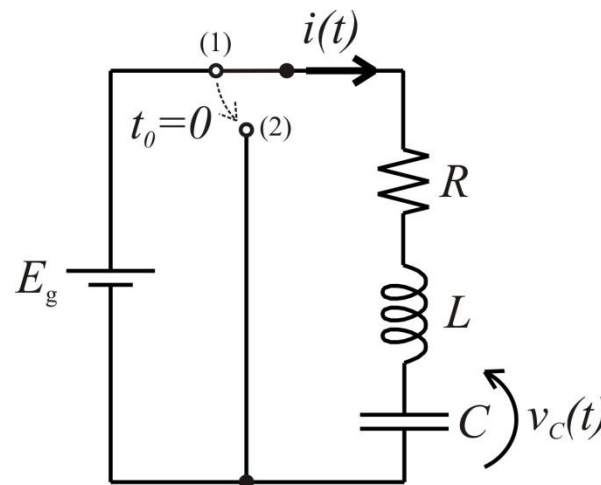**Characteristic equation:**

$$\Rightarrow s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$\left( \begin{array}{l} \text{Once } i(t) \text{ is known we can obtain } v_C(t): \\ v_C(t) = -v_R(t) - v_L(t) = -Ri(t) - L\frac{di(t)}{dt} \end{array} \right)$$





# Type of solutions of the homogeneous equation

$$s^2 + a_1 s + a_0 = 0 \text{ being } a_1 = \frac{R}{L} = 2\xi\omega_n, \quad a_0 = \frac{1}{LC} = \omega_n^2$$



$$s_{1,2} = \frac{-a_1 \pm \sqrt{a_1^2 - 4a_0}}{2} = -\xi\omega_n \pm \omega_n \sqrt{\xi^2 - 1}, \text{ (units : s}^{-1}\text{)}$$

If  $a_1^2 > 4a_0$ , ( $\xi > 1$ )

$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$  : **Overdamped**

$$i(0) = A_1 + A_2 = 0 \Rightarrow i(t) = A_1 (e^{s_1 t} - e^{s_2 t})$$

$$v_C(0) = -Ri(0) - L \left. \frac{di(t)}{dt} \right|_{t=0} = E_g \Rightarrow A_1 = \frac{-E_g}{L(s_1 - s_2)} \Rightarrow i(t) = \frac{-E_g (e^{s_1 t} - e^{s_2 t})}{L(s_1 - s_2)}$$

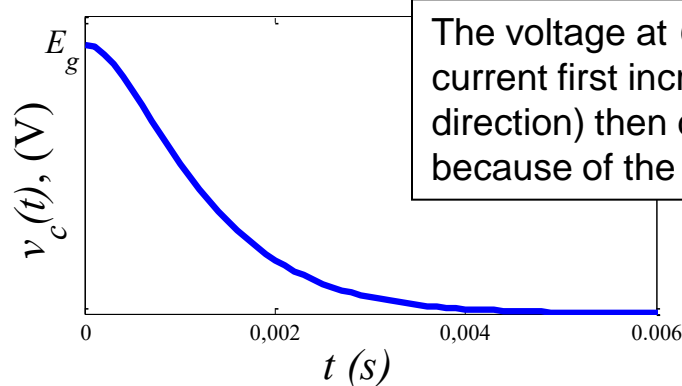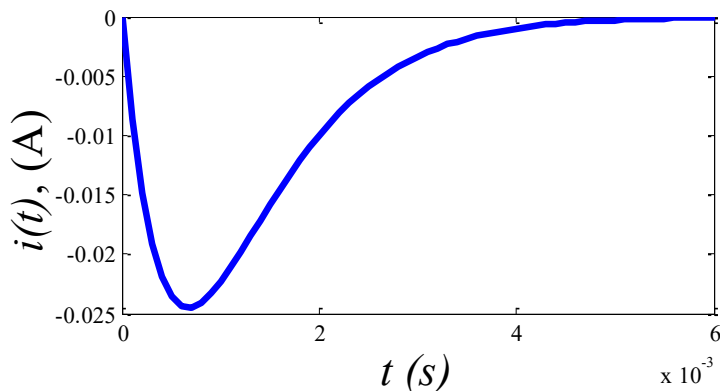

The voltage at C decreases. The current first increases (in opposite direction) then decreases to zero because of the energy dissipated in R.



# Type of solutions of the homogeneous equation


If  $a_1^2 < 4a_0$ , ( $\xi < 1$ )  $\Rightarrow s_1 = s_2^*$

$$i(t) = A_1 e^{-\frac{a_1}{2}t} \sin\left(\frac{\sqrt{4a_0 - a_1^2}}{2}t + \phi\right): \text{Underdamped}$$

here  $\omega_d := \frac{\sqrt{4a_0 - a_1^2}}{2}$  is the **damped natural frequency**

$$i(0) = A_1 \sin \phi = 0 \Rightarrow \phi = 0, \pm\pi, \pm 2\pi, \dots$$

$$v_C(0) = 0 - L \left. \frac{di(t)}{dt} \right|_{t=0} = E_g \Rightarrow A_1 = \frac{-2E_g}{L\sqrt{4a_0 - a_1^2}} \Rightarrow i(t) = \frac{-2E_g}{L\sqrt{4a_0 - a_1^2}} e^{-\frac{a_1}{2}t} \sin\left(\frac{\sqrt{4a_0 - a_1^2}}{2}t\right).$$

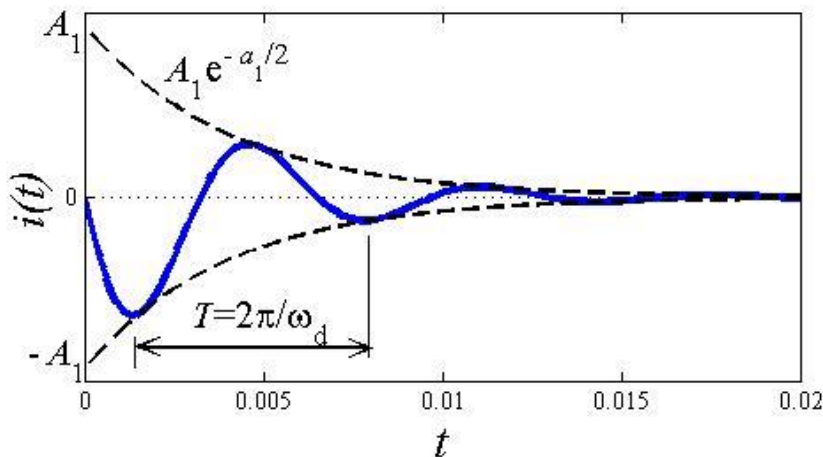

The oscillation is a consequence of the energy exchange between  $C$  and  $L$ . First it moves from  $C$  to  $L$ , on the way some energy is dissipated by  $R$ . Once the remaining energy is stored in  $L$  it moves back to  $C$  dissipating again some energy in  $R$  and so on until all the energy is dissipated by  $R$ .





# Type of solutions of the homogeneous equation

$$\text{If } a_1^2 = 4a_0, (\xi = 1) \Rightarrow s_1 = s_2 = -\frac{a_1}{2} = -\frac{R}{2L} = -\xi\omega_n$$

$$i(t) = (A_1 + A_2 t)e^{s_1 t} : \text{Critically damped}$$

$$i(0) = A_1 = 0 \Rightarrow i(t) = A_2 t e^{s_1 t}$$

$$v_C(0) = 0 - L \left. \frac{di(t)}{dt} \right|_{t=0} = E_g \Rightarrow A_2 = \frac{-E_g}{L} \left. \right\} \Rightarrow i(t) = \frac{-E_g}{L} t e^{-\frac{a_1}{2} t}$$

$$\text{If } a_1 = 0, (\xi = 0)$$

$$i(t) = A_1 \sin(\sqrt{a_0} t + \phi) : \text{Undamped}$$

$$i(0) = A_1 \sin \phi = 0 \Rightarrow \phi = 0, \pm\pi, \pm 2\pi, \dots$$


$$v_C(0) = 0 - L \left. \frac{di(t)}{dt} \right|_{t=0} = E_g \Rightarrow A_1 = \frac{-E_g}{L\sqrt{a_0}} \left. \right\} \Rightarrow i(t) = -E_g \sqrt{\frac{C}{L}} \sin\left(\frac{1}{\sqrt{LC}} t\right)$$

undamped natural frequency



# Type of solutions of the homogeneous equation


Discharge of the capacitor

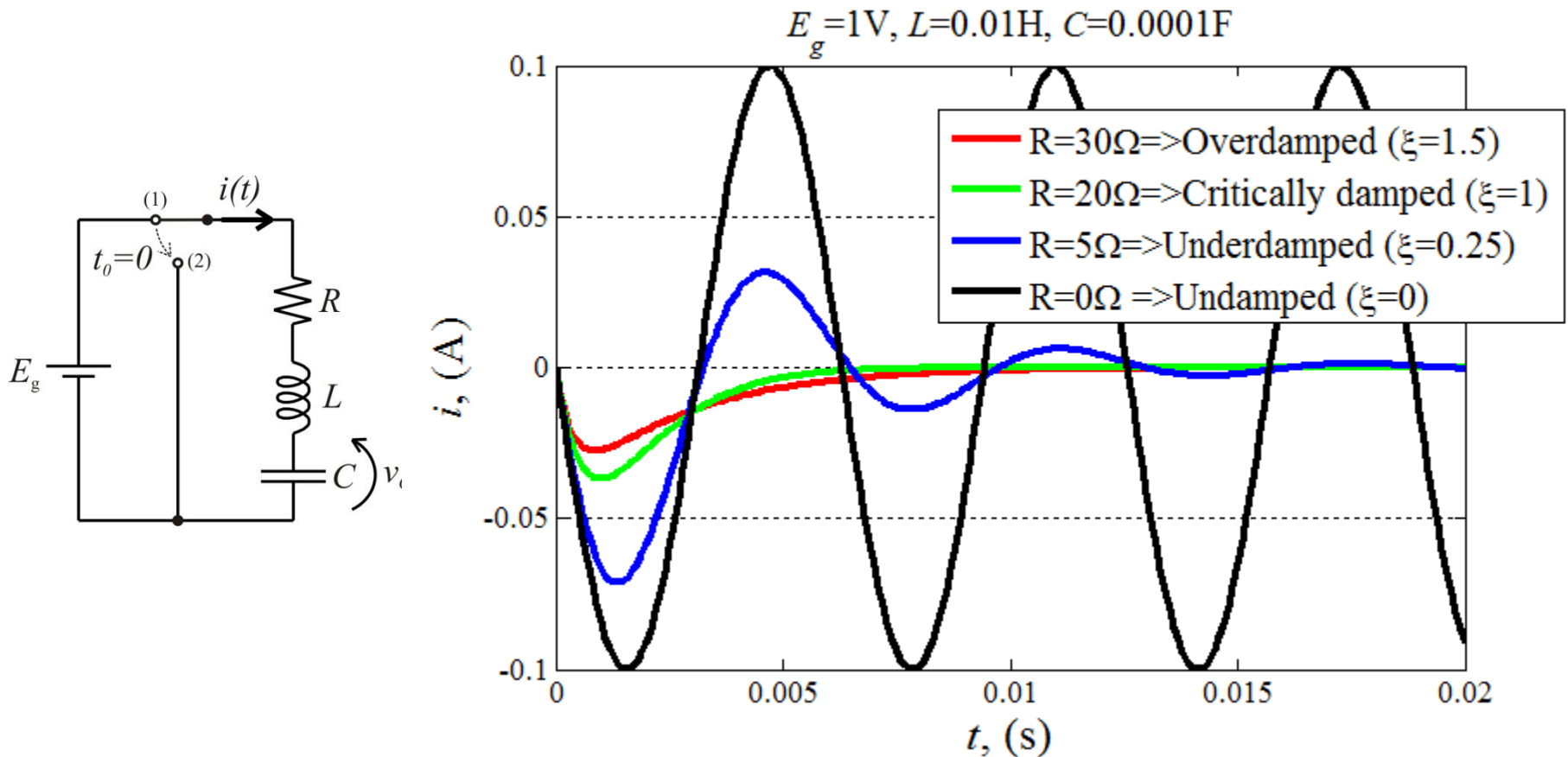


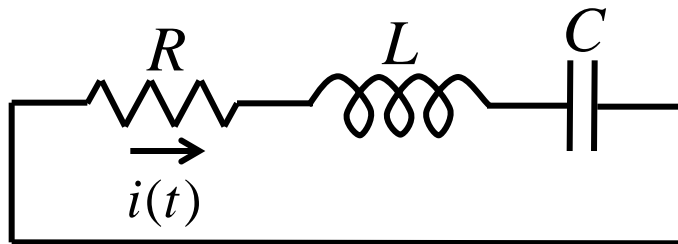
# Cause of the transient response

- RLC-serie. The resulting damping ratio is:




$$\xi = \frac{R}{2\omega_n L}$$

Is proportional to  $R$  because the energy dissipated in  $R$  increases with  $R$ :

$$p_R(t) = Ri^2(t)$$

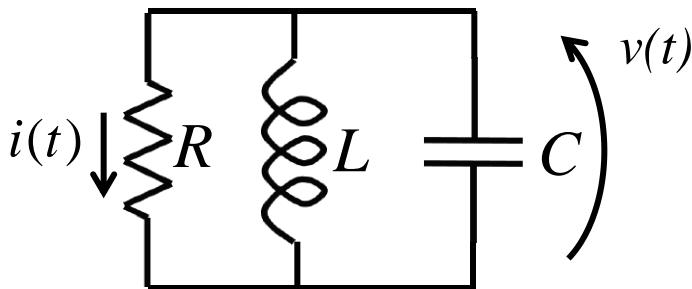- RLC-parallel. The resulting damping ratio is:



$$\xi = \frac{1}{2R\omega_n C}$$

Is inversely proportional to  $R$  since the energy dissipated in  $R$  decreases with  $R$ :

$$p_R(t) = Ri_R^2(t) = \frac{v^2(t)}{R}$$



# Transient circuit's analysis using Laplace transforms

- By using Laplace transforms the circuits can be solved much easily:
  - No differential equation has to be obtained
  - We will solve algebraic instead of differential equations
  - No need to perform the tedious operations to calculate the constants ( $A_1, A_2, \dots$ ) of the solution



# Laplace transform ( $\mathcal{L}$ )

- The solutions are superposition's of exponential decreasing functions starting from the initial instant ( $t=0$ )

$$y(t) = \sum_n A_n e^{s_n t}$$

- The Laplace transform ( $\mathcal{L}$ ) allows to transform the differential equation into an algebraic equation with coefficients  $A(s)$

$$A(s) = \mathcal{L}[y(t)] = \int_0^{\infty} y(t) e^{-st} dt$$



# Some properties of $\mathcal{L}$

- $\mathcal{L}$  is lineal,  $F(s) = \mathcal{L}[f(t)]$

$$f_3(t) = af_1(t) + bf_2(t) \Leftrightarrow F_3(s) = aF_1(s) + bF_2(s)$$

Ohm's and Kirchhoff law's  
are still valid in  $\mathcal{L}$ -domain

- $\mathcal{L}$  of a derivation

$$\mathcal{L}[f^{(n)}(t)] = s^n \mathcal{L}[f(t)] - s^{n-1} f(0) - s^{n-2} f'(0) - \dots - f^{(n-1)}(0)$$

- Time translation

$$\mathcal{L}[f(t-t_0)] = e^{-st_0} \mathcal{L}[f(t)], \quad \text{if } f(t < t_0) = 0$$

Differential equation are transformed into algebraic equations

- Translation *in*  $s$  domain

$$F(s-a) = \mathcal{L}[e^{ta} f(t)]$$

- Theorem of the final and initial value


$$\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} (sF(s)),$$

$$\lim_{t \rightarrow 0} f(t) = \lim_{s \rightarrow \infty} (sF(s)).$$




# $\mathcal{L}$ of some functions

- Step function displaced in time

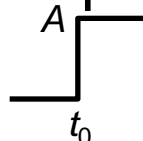


$$\mathcal{L}[Au(t-t_0)] = Ae^{-t_0s} \mathcal{L}[u(t)] = \frac{A}{s} e^{-t_0s}$$

- Slope

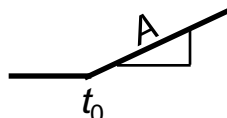


$$\mathcal{L}[A(t-t_0)u(t-t_0)] = Ae^{-t_0s} \mathcal{L}[tu(t)] = \frac{A}{s^2} e^{-t_0s}$$

- Rec function

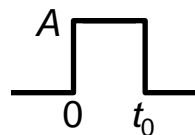

$$\mathcal{L}[A(u(t) - u(t-t_0))] = \frac{A}{s} - Ae^{-t_0s} \mathcal{L}[u(t)] = \frac{A}{s} (1 - e^{-t_0s})$$

- Dirac delta function

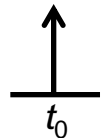

$$\mathcal{L}[\delta(t-t_0)] = e^{-t_0s} \mathcal{L}[\delta(t)] = 1e^{-t_0s}$$

- Periodic functions** with period  $T$

$$f(t) = \sum g(t-nT), \quad g(t) = f(t)(u(t) - u(t-T))$$

$$\mathcal{L}[f(t)] = \sum_n \mathcal{L}[g(t)]e^{nTs} = \frac{\mathcal{L}[g(t)]}{1 - e^{Ts}}$$



# $\mathcal{L}$ of some functions

- Exponential

$$\mathcal{L}[e^{-at}] = \frac{1}{s + a}$$

- Sine

$$\mathcal{L}[\sin at] = \frac{a}{s^2 + a^2}$$

- Cosine

$$\mathcal{L}[\cos at] = \frac{s}{s^2 + a^2}$$

- In practice we will use a table with the most common inverse Laplace transforms ( $\mathcal{L}^{-1}$ ) used for the resolution of the proposed problems





# Resolution using Laplace


- The circuits will be solved in the Laplace domain:
  - Draw the circuit in the transformed domain, for this the initial conditions are deduced:  $i_L(0)$ ,  $v_C(0)$ .
  - The transformed circuit is then solved using the known methods, thus, by applying the Kirchhoff laws to the transformed currents and voltages:  $I(s)$ ,  $V(s)$ .(\*)
  - Once you know the Laplace transformed voltage or current, the inverse Laplace transform is applied to get the currents and voltages in the time domain

$$i(t) = \mathcal{L}^{-1}[I(s)], \quad v(t) = \mathcal{L}^{-1}[V(s)]$$

(\*): Convention: Laplace transformed variables in capital letters


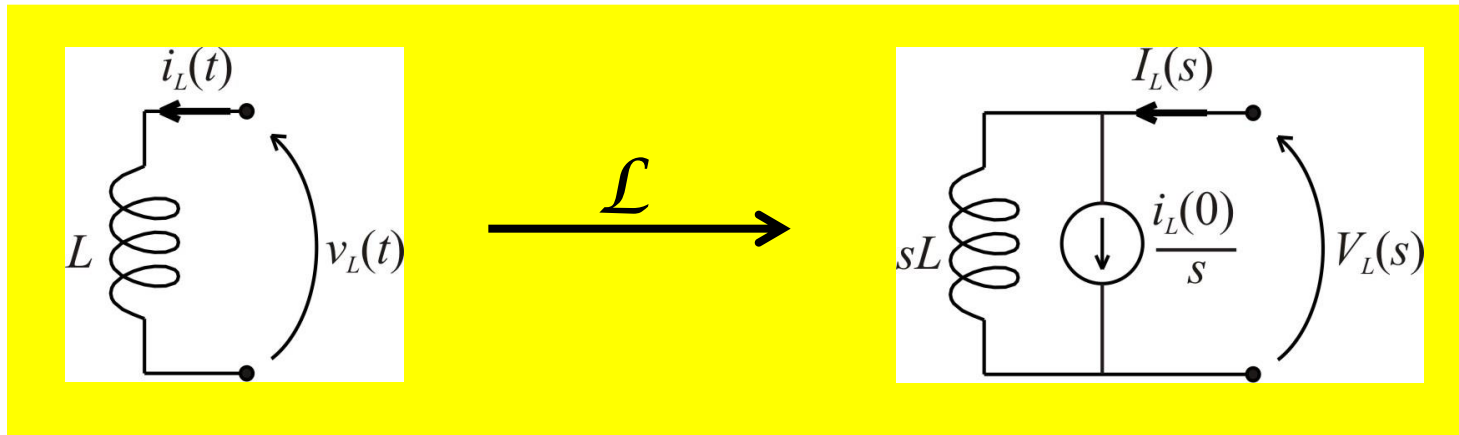
# $\mathcal{L}$ transform of the inductor




$$I_L(s) = \mathcal{L}[i_L(t)],$$

$$V_L(s) = \mathcal{L}[v_L(t)],$$

$$V_L(s) = \int_0^{\infty} v_L(t) e^{-st} dt = L \int_0^{\infty} \frac{di_L(t)}{dt} e^{-st} dt = Ls \left( I_L(s) - \frac{i_L(0)}{s} \right).$$


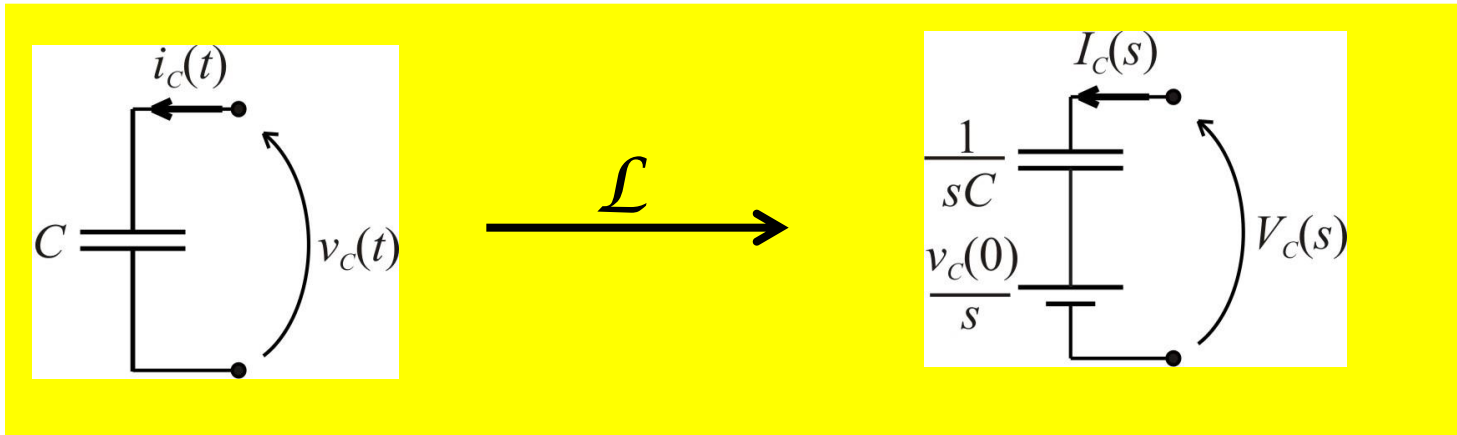
# $\mathcal{L}$ transform of the capacitor



$$I_C(s) = \mathcal{L}[i_C(t)],$$

$$V_C(s) = \mathcal{L}[v_C(t)],$$


$$V_C(s) = \int_0^{\infty} v_C(t) e^{-st} dt = \frac{1}{C} \int_0^{\infty} q(t) e^{-st} dt = \frac{1}{C} \left( \frac{q(0)}{s} + \frac{1}{s} I_C(s) \right)$$

$$= \frac{1}{sC} I_C(s) + \frac{v_C(0)}{s}.$$



# $\mathcal{L}$ transform of the generator

- After the switching:

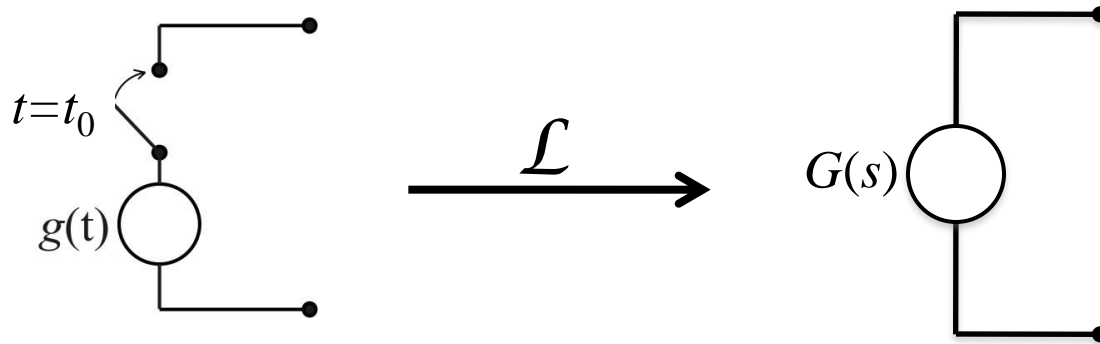

For example:  $\mathcal{L}[E] = \frac{E}{s}$ ,  $\mathcal{L}[\sin at] = \frac{a}{s^2 + a^2}$ ,  $\mathcal{L}[\cos at] = \frac{s}{s^2 + a^2}$

- If the switching happens at  $t_0 \neq 0$ , perform a time translation by defining:  $t' = t - t_0$ . This has to be taken into account by performing the inverse transform.



# Initial conditions

- The initial condition we need are:
  - The currents through each of the coils just after the switching takes place:  $i_L(t_0^+)$
  - The voltages at the terminals of the capacitors after the switching takes place:  $v_C(t_0^+)$
- If they are not known, then they have to be calculated by a previous (before the switching) resolution of the circuit,
  - Remember:  $i_L(t_0^+) = i_L(t_0^-)$ ,  $v_C(t_0^+) = v_C(t_0^-)$



# Resolution in the $\mathcal{L}$ -domain

- The transformed circuit is solved by applying the mesh or nod methods of the transformed voltages or the currents which depend on the variable  $s$ .
- The following expression for the voltage or current has to be obtained:

$$Y(s) \propto \frac{f(s)}{s^2 + a_1s + a_0}$$

where the denominator is the characteristic equation:

$$s^2 + a_1s + a_0 = 0 \Rightarrow s_{1,2} = \frac{1}{2} \left( -a_1 \pm \sqrt{a_1^2 - 4a_0} \right)$$

From which the roots ( $s_1$  and  $s_2$ ) are obtained, these allows:

- Predict the kind of solution
- Find the inverse in the Laplace transform table



# Predicting of the kind of solution

- If the roots are **real and different**

$$Y(s) \propto \frac{f(s)}{s^2 + a_1s + a_0} = \frac{f(s)}{(s - s_1)(s - s_2)} \xrightarrow{\mathcal{L}^{-1}} y(t) \propto A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

- For **equal and real** roots

$$Y(s) \propto \frac{f(s)}{s^2 + a_1s + a_0} = \frac{f(s)}{(s - s_1)^2} \xrightarrow{\mathcal{L}^{-1}} y(t) \propto (A_1 + A_2 t) e^{s_1 t}$$

- For complex conjugated roots:  **$s_{1,2} = p \pm jq$**

$$Y(s) \propto \frac{f(s)}{s^2 + a_1s + a_0} = \frac{f(s)}{(s - p)^2 + q^2} \xrightarrow{\mathcal{L}^{-1}} y(t) \propto A e^{pt} \sin(qt + \phi)$$

- Imaginary roots:  **$s_{1,2} = \pm jq$**

$$Y(s) \propto \frac{f(s)}{s^2 + a_1s + a_0} = \frac{f(s)}{s^2 + q^2} \xrightarrow{\mathcal{L}^{-1}} y(t) \propto A \sin(qt + \phi)$$



# Inverse Laplace transform ( $\mathcal{L}^{-1}$ )


- The roots of the characteristic equation allows:
  - To know beforehand the kind of solution
  - It makes easier to find the inverse Laplace transform in the inverse Laplace transform table.
- Do not forget: if there was a time shifting, substitute  $t'$  by  $t-t_0$  in the inverse transform.
- The obtained solution is defined for a time interval after the switching.
- **Check the initial condition.**




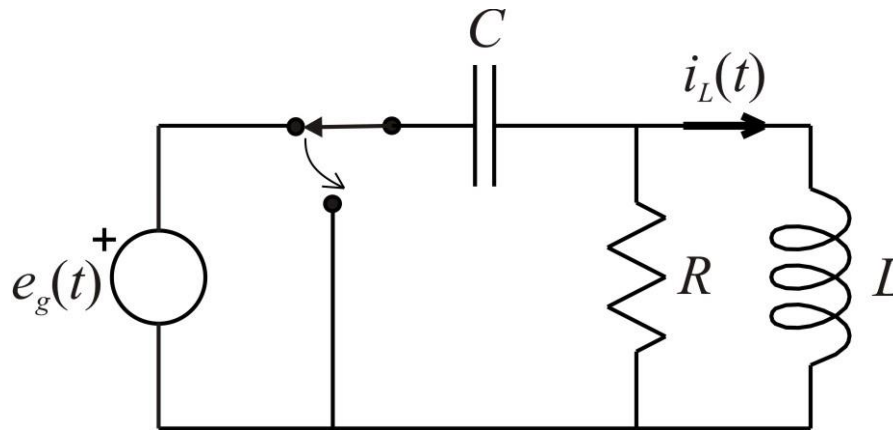
# Example 1

- In the circuit of the figure, the switcher is in position (1) since  $t = -\infty$ . At  $t = \pi/2$  the switcher changes to position (2). Obtain the temporal evolution of  $i_L(t)$ .




Data:  $e_g(t) = 2\cos 2t$  V,  $R = 2\Omega$ ,  $L = 1$ H,  $C = 0.5$ F.


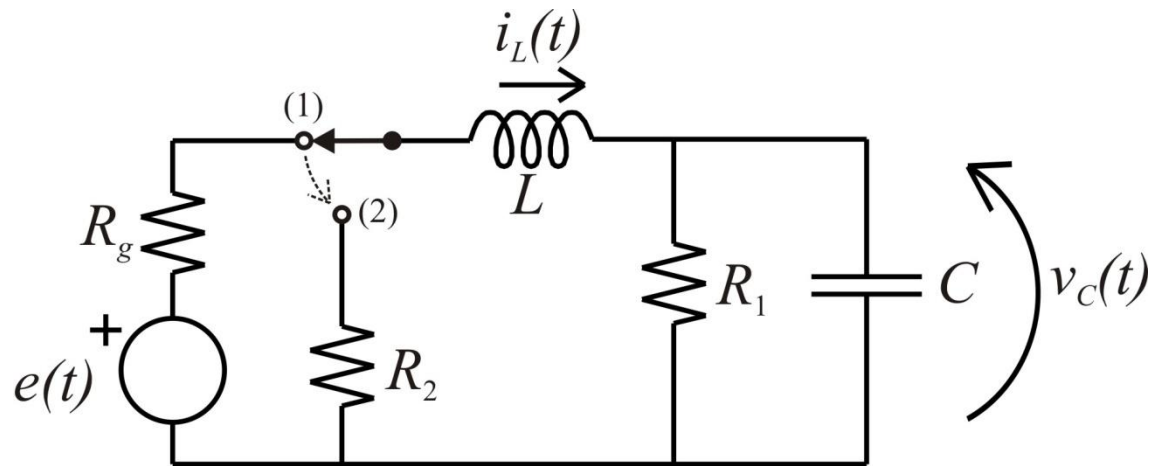
## Example 2


- In the circuit of the figure, the switcher is in position (1) since  $t = -\infty$ . At  $t = 0$  the switcher switches to position (2). Obtain the temporal evolution of  $v_C(t)$ .



Data:  $e(t) = 10\text{V}$ ,  $R_g = R_1 = 1\Omega$ ,  $R_2 = 2\Omega$ ,  $L = 1\text{H}$ ,  $C = 2\text{F}$ .



# Simulation with 5Spice

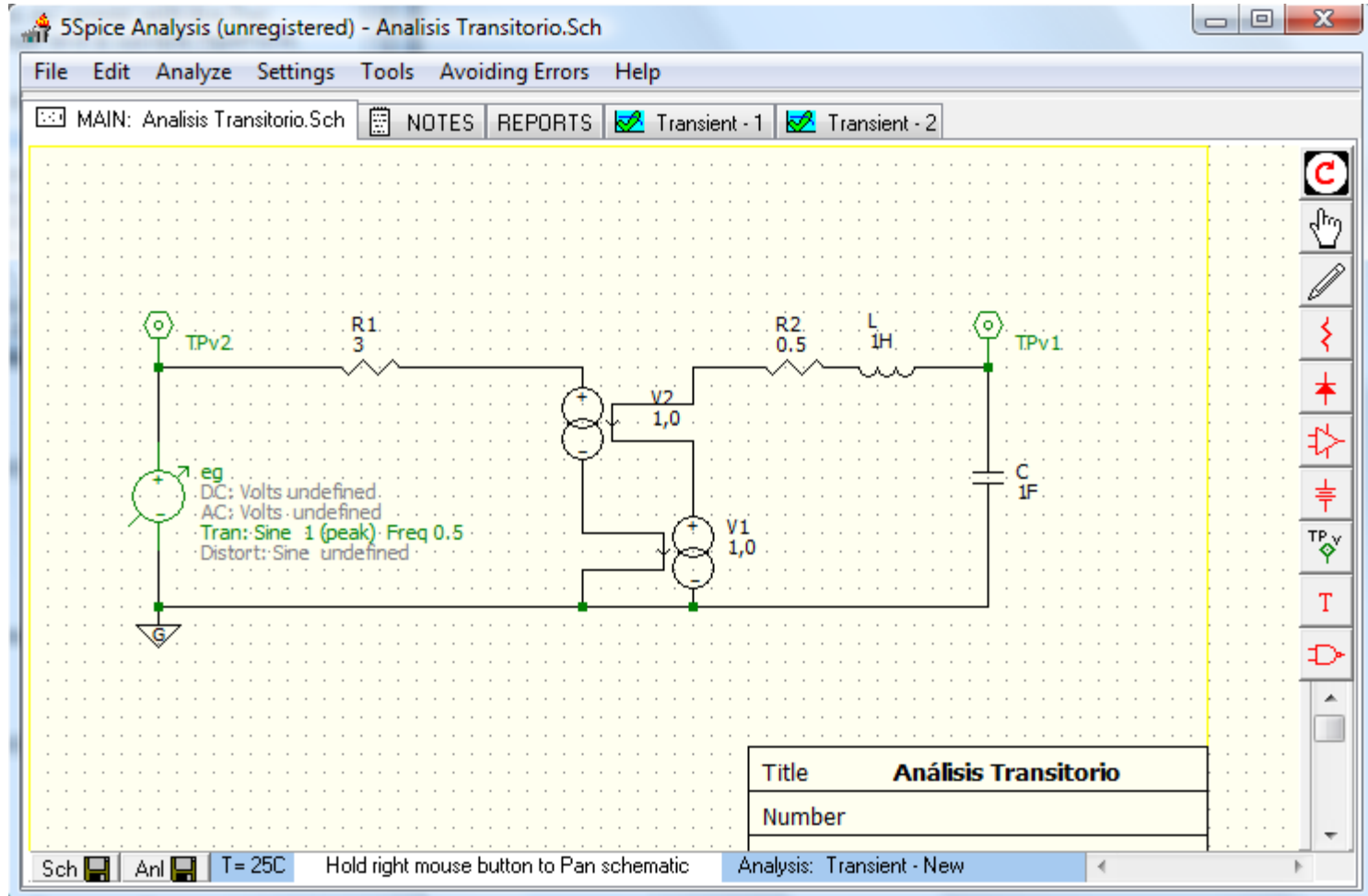



# Simulación con 5Spice

