

U2. Two-port Networks or Quadripoles

Circuit Analysis, Grado TIC

Philip Siegmann

Departamento de Teoría de la Señal y Comunicaciones

philip.siegmann@uah.es


Curso 2017-2018

Index

- Introduction
- Definition
- Motivation
- Reciprocal and symmetrical quadripoles (Q)
- y-parameters
- z-parameters
- h-parameters
- g-parameters
- Transmission parameters (T or ABCD)
- Parameters for reciprocal and symmetrical Q
- Relationship between parameters (table)
- Association (p-p, s-s, s-p, p-s, and cascaded)


Two-port network or quadripole (Q)

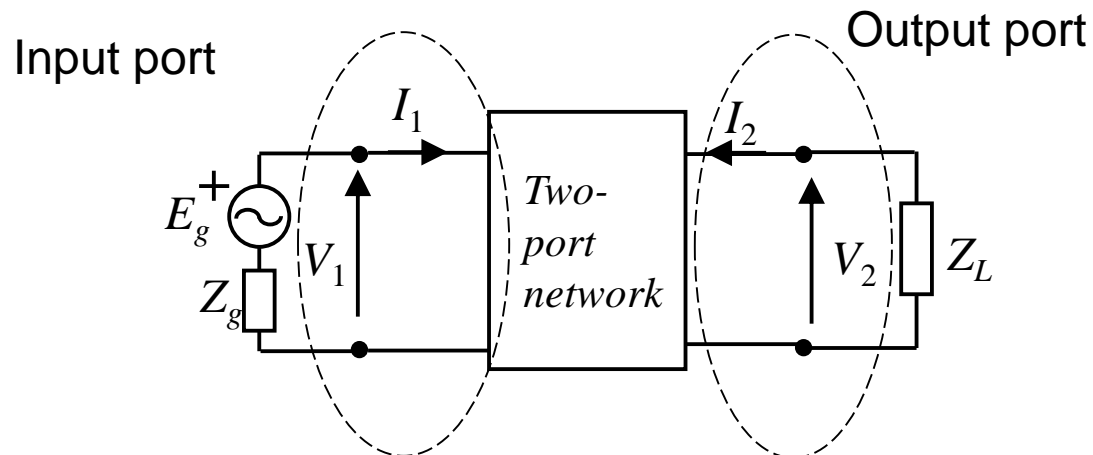- It is an external characterization of a *linear* and *passive* circuit that allows to know how it will interact with other elements
- It has two ports to be connected to other elements: the input and the output port
- It is then a “black box” that is usually connected between a generator (E_g, Z_g) and a load element (Z_L)




Two-port network or quadripole (Q)

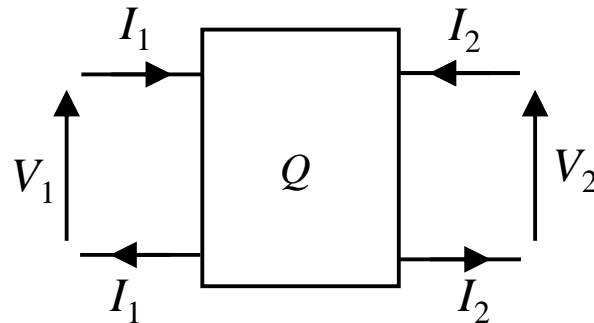- **Q is characterized with 4 parameters** that will allow us to directly relate I_1 , I_2 , V_1 and V_2
- Q's are characterized by:
 - Initial conditions are zero (when analyzing in Laplace domain no energy is stored before any connection)
 - It is **passive** (it does not have independent sources)
 - At **each port** the current that enters is the same as the current that exits (port condition)



Two-port network or quadripoles (Q)

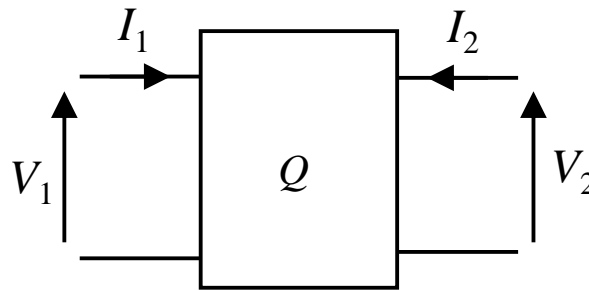- The voltages and currents at the input and output ports can be related each other with different family of parameters: “z”, “y”, “h”, ...



$$\text{"z":} \begin{cases} V_1 = z_{11}I_1 + z_{12}I_2 \\ V_2 = z_{21}I_1 + z_{22}I_2 \end{cases}, \text{"y":} \begin{cases} I_1 = y_{11}V_1 + y_{12}V_2 \\ I_2 = y_{21}V_1 + y_{22}V_2 \end{cases}, \text{"h":} \begin{cases} V_1 = h_{11}I_1 + h_{12}V_2 \\ I_2 = h_{21}I_1 + h_{22}V_2 \end{cases} \dots$$

You don't need to know the internal structure of the network, it suffices with the parameters to study the behavior of Q

Reciprocal and Symmetrical Two-port networks

- Q is **reciprocal** when Q is “flipped over”(*) and the relationship between the voltage (or current) applied at one port and the current (or voltage) measured at the other port does not change
- Q is **symmetrical** when Q is flipped over and there is no change in any current and voltage at the input and output gate

(*): the input port is changed with the output port


Reciprocal and Symmetrical Two-port networks

- Any symmetrical Q is also reciprocal
- A special case of reciprocal Q 's are the one made of linear elements only (L, R, C), also known as bilateral Q .
- For symmetrical Q the input- and output impedances will be the same if Q is connected to the same load (at the output- and input port respectively).

Objectives


- Definition and determination of the Q parameters of the different families from measurements at their port's
- Analyze circuits with Q's whose parameters are known.
- The Q parameters are in general defined in the Laplace transformed domain, but we will consider SSS regimen (where $s = j\omega$)

Admittance parameters “y”

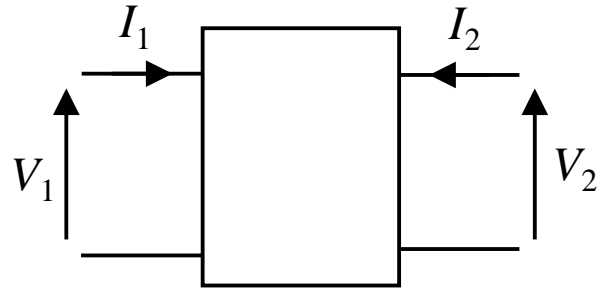

$$\begin{cases} I_1 = y_{11}V_1 + y_{12}V_2 \\ I_2 = y_{21}V_1 + y_{22}V_2 \end{cases}$$


Short-circuit at the output port:

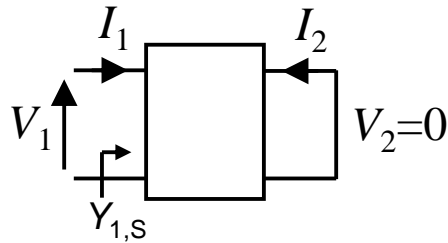

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = Y_{1,S} [=] \Omega^{-1}$$

$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} \quad \text{Short-circuit transfer admittance } i \rightarrow o$$

Short-circuit at the input port:

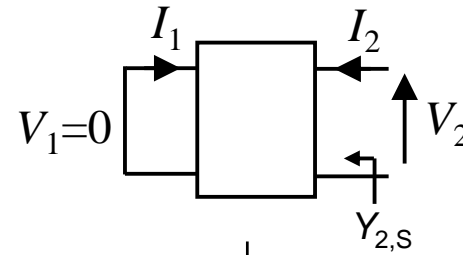


$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \quad \text{S.c. transfer admittance } o \rightarrow i$$

$$y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = Y_{2,S}$$

Admittance parameters “y”

- Equivalent circuit

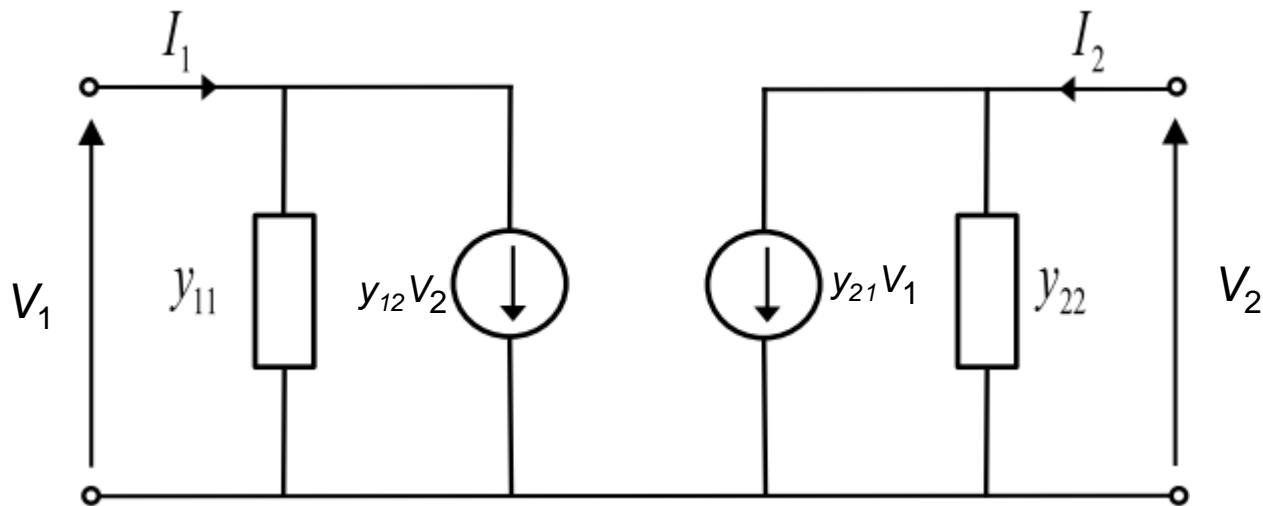


$$\begin{cases} I_1 = y_{11}V_1 + y_{12}V_2 \\ I_2 = y_{21}V_1 + y_{22}V_2 \end{cases}$$

Q is reciprocal $\Rightarrow y_{12}=y_{21}$


Q is symmetrical $\Rightarrow y_{11}=y_{22}$ & $y_{12}=y_{21}$

Impedance parameters “z”

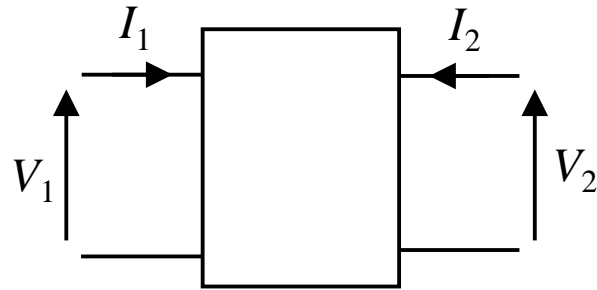

$$\begin{cases} V_1 = z_{11}I_1 + z_{12}I_2 \\ V_2 = z_{21}I_1 + z_{22}I_2 \end{cases}$$


Open-circuit at the output port:

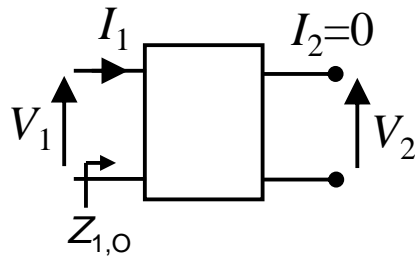

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = Z_{1,0} [=] \Omega$$

$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} \quad \text{O.c. transfer impedance } i \rightarrow o$$

Open-circuit at the input port:

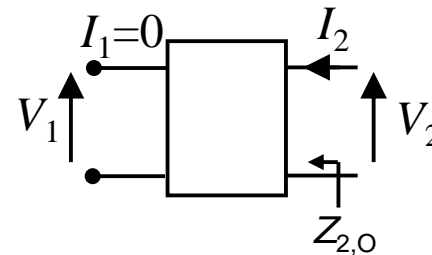


$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad \text{O.c. transfer impedance } o \rightarrow i$$

$$z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = Z_{2,0}$$

Impedance parameters “z”

- Equivalent circuit

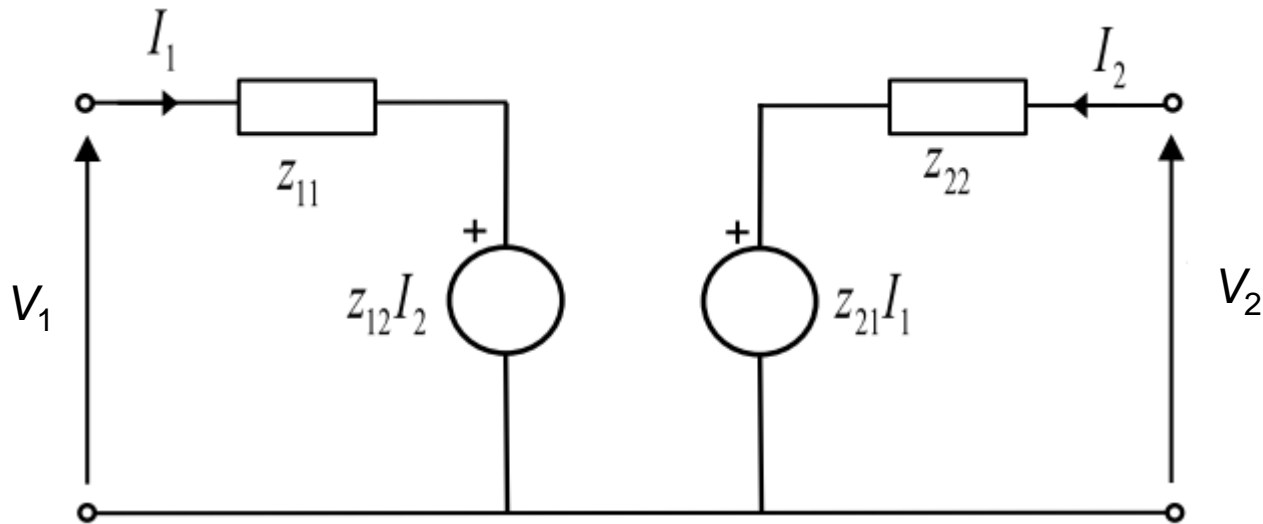



$$\begin{cases} V_1 = z_{11}I_1 + z_{12}I_2 \\ V_2 = z_{21}I_1 + z_{22}I_2 \end{cases}$$

Q is reciprocal $\Rightarrow z_{12} = z_{21}$

Q is symmetrical $\Rightarrow z_{11} = z_{22}$ & $z_{12} = z_{21}$


Bilateral and symmetrical quadripoles

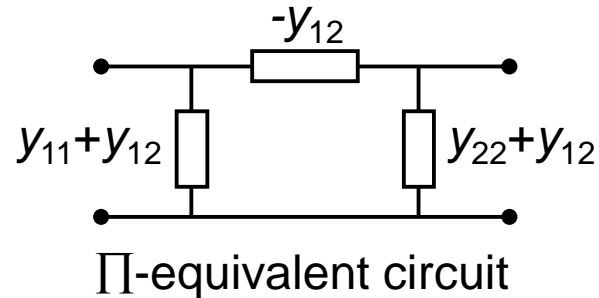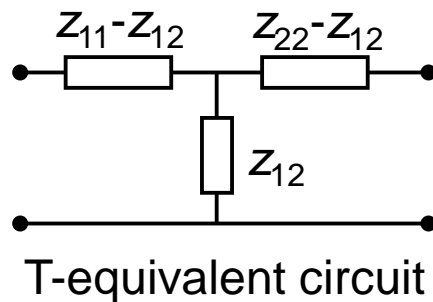- Example of quadripoles characterized with z and y-parameters




- Some application of z- and y-parameters
 - Impedance matching (optimize the power transference from source to load impedance)
 - Power distribution networks
 - Filter design (unit 4)

Hybrid parameters “h”

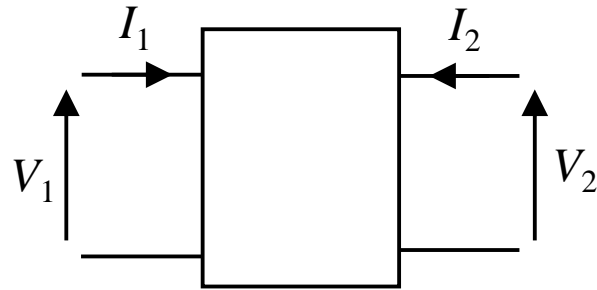

$$\begin{cases} V_1 = h_{11}I_1 + h_{12}V_2 \\ I_2 = h_{21}I_1 + h_{22}V_2 \end{cases}$$


Short-circuit at the output port:

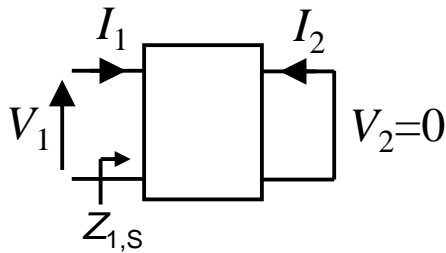

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = Z_{1,s} [=] \Omega$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} \quad \text{S.c. forward (i} \rightarrow \text{o) current gain}$$

Open-circuit at the input port:

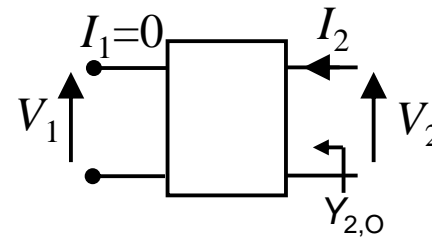


$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} \quad \text{O.c. reverse (o} \rightarrow \text{i) voltage gain}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = Y_{2,o} [=] \Omega^{-1}$$

Hybrid parameters “h”

- Equivalent circuit

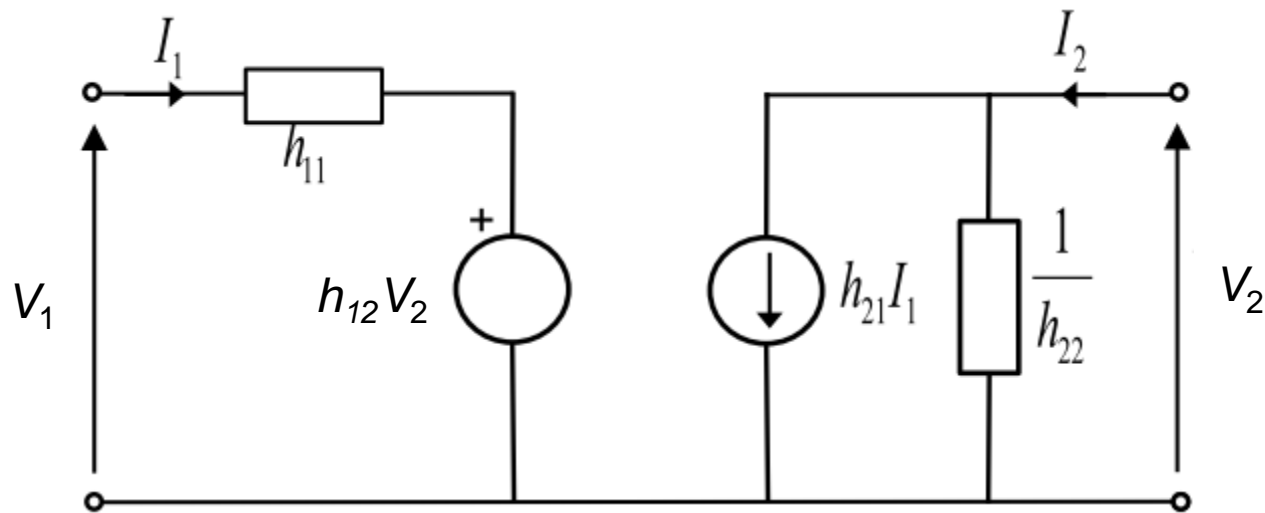


$$\begin{cases} V_1 = h_{11}I_1 + h_{12}V_2 \\ I_2 = h_{21}I_1 + h_{22}V_2 \end{cases}$$

Q is reciprocal $\Rightarrow h_{12} = -h_{21}$


Q is symmetrical $\Rightarrow \det(\mathbf{h}) = h_{11}h_{22} - h_{12}h_{21} = 1$ & $h_{12} = -h_{21}$

Inverse hybrid parameters “g”

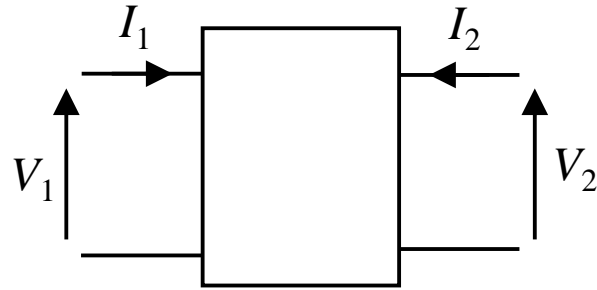

$$\begin{cases} I_1 = g_{11}V_1 + g_{12}I_2 \\ V_2 = g_{21}V_1 + g_{22}I_2 \end{cases}$$


Open-circuit at the output port:

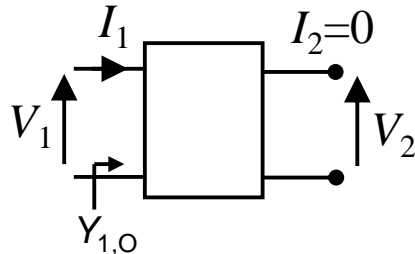

$$g_{11} = \left. \frac{I_1}{V_1} \right|_{I_2=0} = Y_{1,o} [=] \Omega^{-1}$$

$$g_{21} = \left. \frac{V_2}{V_1} \right|_{I_2=0} \quad \text{O.c. forward (i} \rightarrow \text{o) voltage gain}$$

Short-circuit at the input port:

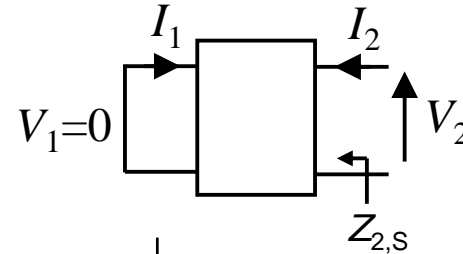


$$g_{12} = \left. \frac{I_1}{I_2} \right|_{V_1=0} \quad \text{S.c. reverse (o} \rightarrow \text{i) current gain}$$

$$g_{22} = \left. \frac{V_2}{I_2} \right|_{V_1=0} = Z_{2,s} [=] \Omega$$

Inverse hybrid parameters “g”

- Equivalent circuit

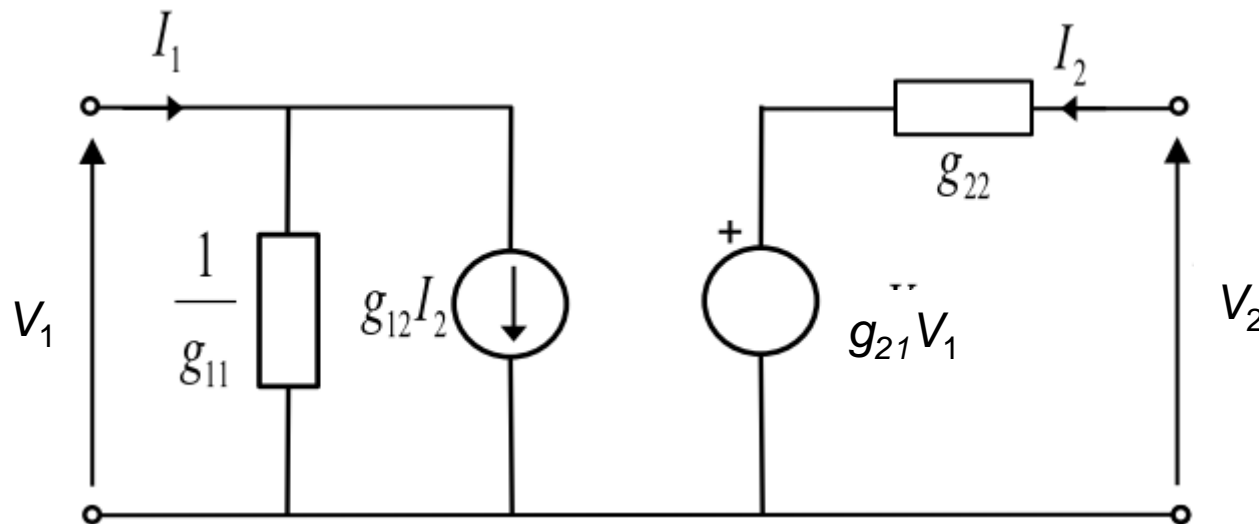


$$\begin{cases} I_1 = g_{11}V_1 + g_{12}I_2 \\ V_2 = g_{21}V_1 + g_{22}I_2 \end{cases}$$

Q is reciprocal $\Rightarrow g_{12} = -g_{21}$,

Q is symmetrical $\Rightarrow \det(\mathbf{g}) = g_{11}g_{22} - g_{12}g_{21} = 1$ & $g_{12} = -g_{21}$

g- and h-parameters are used for modeling transformers and transistors

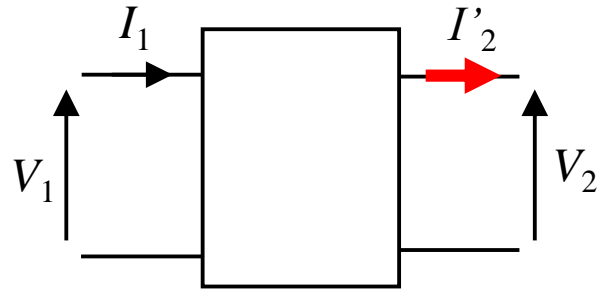
Transmission parameters “**T**” (o “*ABCD*”)



$$\begin{cases} V_1 = AV_2 + BI'_2 \\ I_1 = CV_2 + DI'_2 \end{cases}, \quad \mathbf{T} = \begin{pmatrix} A & B \\ C & D \end{pmatrix}$$

$$(I'_2 = -I_2)$$


Open-circuit at the output port:

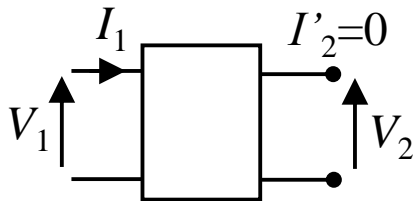

$$A = \left. \frac{V_1}{V_2} \right|_{I'_2=0} \quad \text{O.c. reverse (o} \rightarrow \text{i) voltage gain.}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I'_2=0} \quad \text{O.c. transfer admittance (o} \rightarrow \text{i)}$$


Short-circuit at the output port :

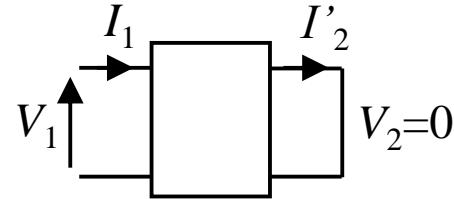


$$B = \left. \frac{V_1}{I'_2} \right|_{V_2=0} \quad \text{S.c. transfer impedance o} \rightarrow \text{i}$$

$$D = \left. \frac{I_1}{I'_2} \right|_{V_2=0} \quad \text{S.c. reverse (o} \rightarrow \text{i) current gain}$$

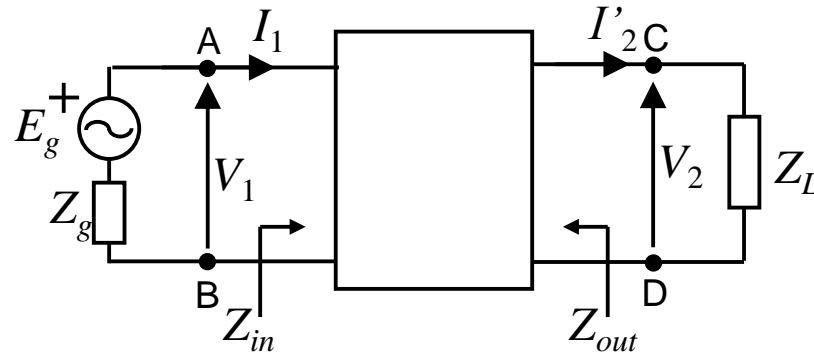
Thevenin and equivalent impedance seen through Q using “T” parameters



Equivalent circuit:

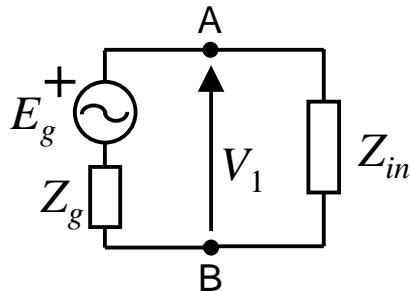


$$Z_{in} = \frac{AZ_L + B}{CZ_L + D}$$

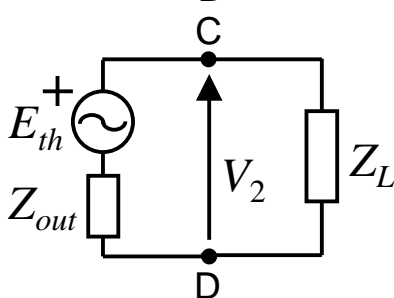

$$Z_{out} = \frac{DZ_g + B}{CZ_g + A}, \quad E_{th} = \frac{E_g}{CZ_g + A}$$

(Note: if $A=D$ and $Z_g=Z_L$ then $Z_{in}=Z_{out}$)

Summary of the Q parameters

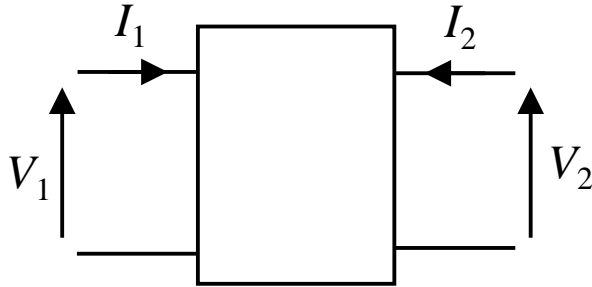

$$\begin{cases} V_1 = AV_2 - BI_2 \\ I_1 = CV_2 - DI_2 \end{cases}$$

$$\begin{cases} V_1 = z_{11}I_1 + z_{12}I_2 \\ V_2 = z_{21}I_1 + z_{22}I_2 \end{cases}$$

$$\begin{cases} I_1 = g_{11}V_1 + g_{12}I_2 \\ V_2 = g_{21}V_1 + g_{22}I_2 \end{cases}$$

$$\begin{cases} I_1 = y_{11}V_1 + y_{12}V_2 \\ I_2 = y_{21}V_1 + y_{22}V_2 \end{cases}$$

$$\begin{cases} V_1 = h_{11}I_1 + h_{12}V_2 \\ I_2 = h_{21}I_1 + h_{22}V_2 \end{cases}$$

There exist two-port network's for which some family of parameters are not defined, for example, ideal transformer.

If Q is reciprocal and symmetrical


Family	Reciprocal only fulfill:	Symmetrical also fulfill
“z”	$z_{12}=z_{21}$	$z_{11}=z_{22}$
“y”	$y_{12}=y_{21}$	$y_{11}=y_{22}$
“h”	$h_{12}=-h_{21}$	$ \mathbf{h} =1$
“g”	$g_{12}=-g_{21}$	$ \mathbf{g} =1$
“T”	$ \mathbf{T} =AD-BC=1$	$A=D$

Relations between the parameters



	“z”	“y”	“h”	“g”	“T”
“z”		$\begin{matrix} y_{22}/ \mathbf{y} & -y_{12}/ \mathbf{y} \\ -y_{21}/ \mathbf{y} & y_{11}/ \mathbf{y} \end{matrix}$	$\begin{matrix} \mathbf{h} /h_{22} & h_{12}/h_{22} \\ -h_{21}/h_{22} & 1/h_{22} \end{matrix}$	$\begin{matrix} 1/g_{11} & -g_{12}/g_{11} \\ g_{21}/g_{11} & \mathbf{g} /g_{11} \end{matrix}$	$\begin{matrix} A/C & \mathbf{T} /C \\ 1/C & D/C \end{matrix}$
“y”	$\begin{matrix} z_{22}/ \mathbf{z} & -z_{12}/ \mathbf{z} \\ -z_{21}/ \mathbf{z} & z_{11}/ \mathbf{z} \end{matrix}$		$\begin{matrix} 1/h_{11} & -h_{12}/h_{11} \\ h_{21}/h_{11} & \mathbf{h} /h_{11} \end{matrix}$	$\begin{matrix} \mathbf{g} /g_{22} & g_{12}/g_{22} \\ -g_{21}/g_{22} & 1/g_{22} \end{matrix}$	$\begin{matrix} D/B & - \mathbf{T} /B \\ -1/B & A/B \end{matrix}$
“h”	$\begin{matrix} \mathbf{z} /z_{22} & z_{12}/z_{22} \\ -z_{21}/z_{22} & 1/z_{22} \end{matrix}$	$\begin{matrix} 1/y_{11} & -y_{12}/y_{11} \\ y_{21}/y_{11} & \mathbf{y} /y_{11} \end{matrix}$		$\begin{matrix} g_{22}/ \mathbf{g} & -g_{12}/ \mathbf{g} \\ -g_{21}/ \mathbf{g} & g_{11}/ \mathbf{g} \end{matrix}$	$\begin{matrix} B/D & \mathbf{T} /D \\ -1/D & C/D \end{matrix}$
“g”	$\begin{matrix} 1/z_{11} & -z_{12}/z_{11} \\ z_{21}/z_{11} & \mathbf{z} /z_{11} \end{matrix}$	$\begin{matrix} \mathbf{y} /y_{22} & y_{12}/y_{22} \\ -y_{21}/y_{22} & 1/y_{22} \end{matrix}$	$\begin{matrix} h_{22}/ \mathbf{h} & -h_{12}/ \mathbf{h} \\ -h_{21}/ \mathbf{h} & h_{11}/ \mathbf{h} \end{matrix}$		$\begin{matrix} C/A & - \mathbf{T} /A \\ -1/A & B/A \end{matrix}$
“T”	$\begin{matrix} z_{11}/z_{21} & \mathbf{z} /z_{21} \\ 1/z_{21} & z_{22}/z_{21} \end{matrix}$	$\begin{matrix} -y_{22}/y_{21} & -1/y_{21} \\ - \mathbf{y} /y_{21} & -y_{11}/y_{21} \end{matrix}$	$\begin{matrix} - \mathbf{h} /h_{21} & -h_{11}/h_{21} \\ -h_{22}/h_{21} & -1/h_{21} \end{matrix}$	$\begin{matrix} 1/g_{21} & g_{22}/g_{21} \\ g_{11}/g_{21} & \mathbf{g} /g_{21} \end{matrix}$	

Association of Q's

Serial-serial

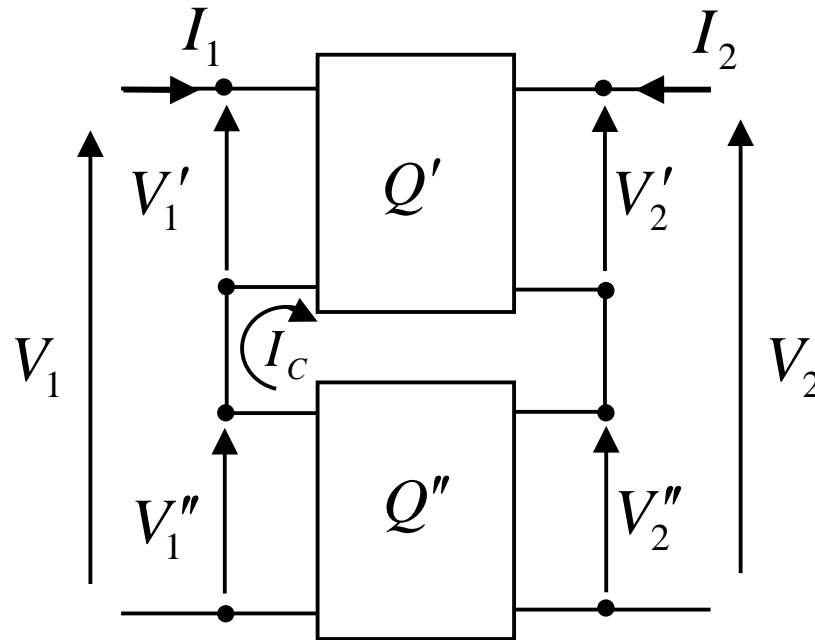

Brune Tests:

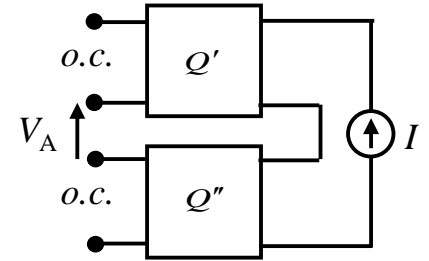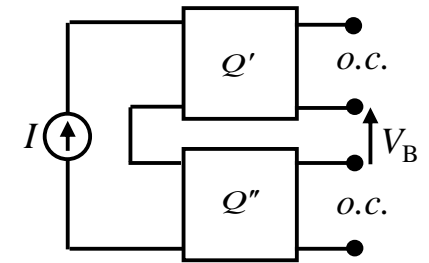


If $V_A=0$ and $V_B=0$
 $\forall I \Rightarrow I_C=0$.


$$\text{If } I_C = 0 \Rightarrow \begin{cases} V_1 = V_1' + V_1'' = (z'_{11} + z''_{11})I_1 + (z'_{12} + z''_{12})I_2 \\ V_2 = V_2' + V_2'' = (z'_{21} + z''_{21})I_1 + (z'_{22} + z''_{22})I_2 \end{cases}$$

Association of Q's

Parallel-parallel

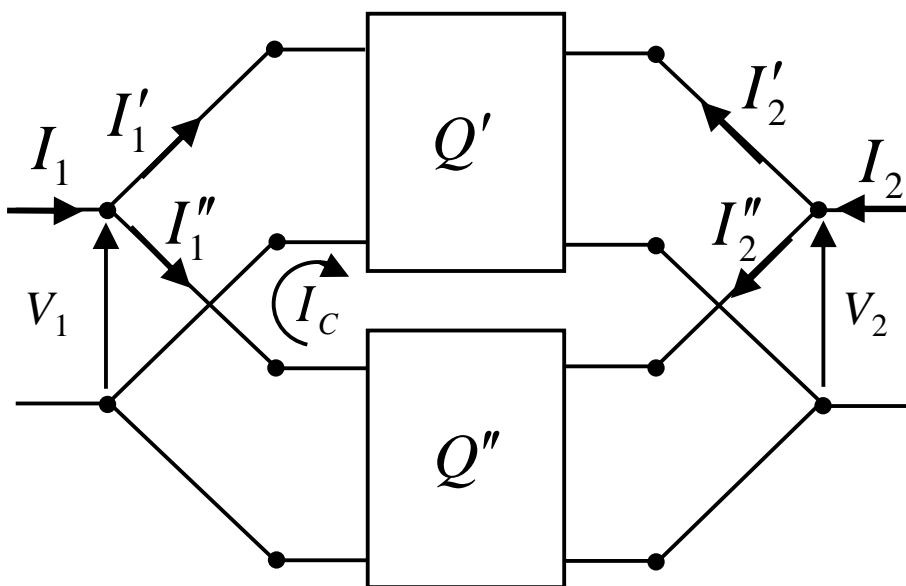

Brune Tests:

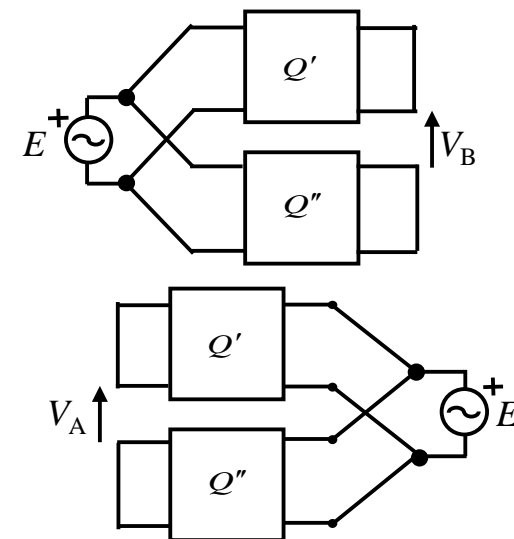


If $V_A=0$ and $V_B=0$
 $\forall E \Rightarrow I_C=0$.



$$\text{if all } I_C = 0 \Rightarrow \begin{cases} I_1 = I_1' + I_1'' = (y'_{11} + y''_{11})V_1 + (y'_{12} + y''_{12})V_2 \\ I_2 = I_2' + I_2'' = (y'_{21} + y''_{21})V_1 + (y'_{22} + y''_{22})V_2 \end{cases}$$

Association of Q's

Serial-parallel

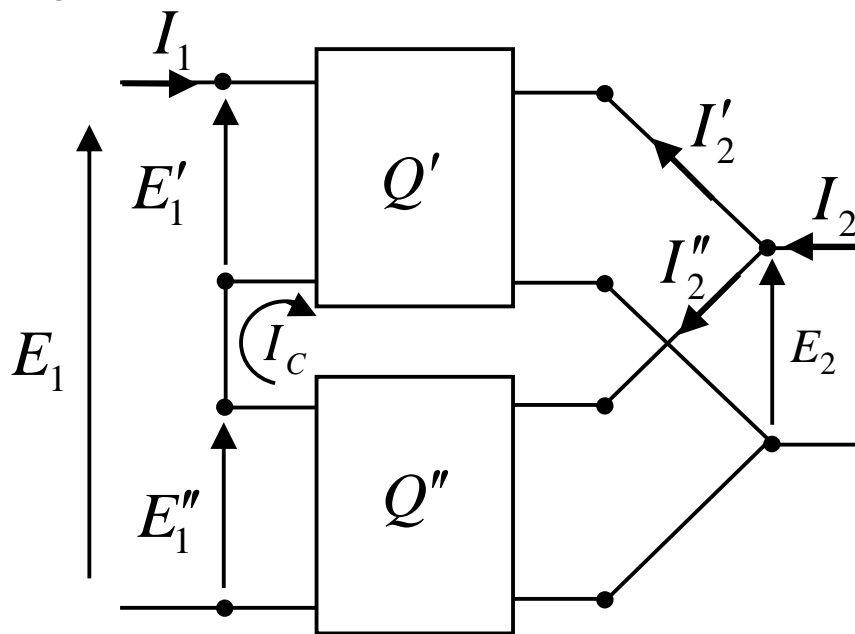

Brune Tests:

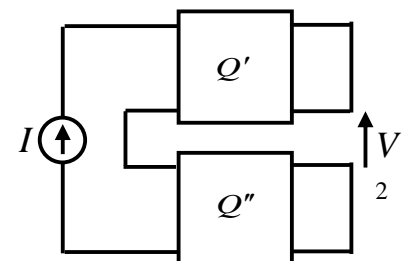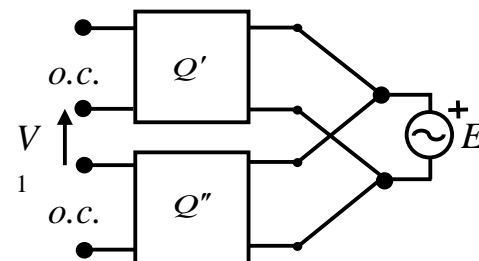


If $V_1=0 \forall E$ and $V_2=0 \forall I \Rightarrow I_C=0$.


$$\text{if all } I_C = 0 \Rightarrow \begin{cases} E_1 = E_1' + E_1'' = (h'_{11} + h''_{11})I_1 + (h'_{12} + h''_{12})E_2 \\ I_2 = I_2' + I_2'' = (h'_{21} + h''_{21})I_1 + (h'_{22} + h''_{22})E_2 \end{cases}$$

Association of Q's

Parallel-serial

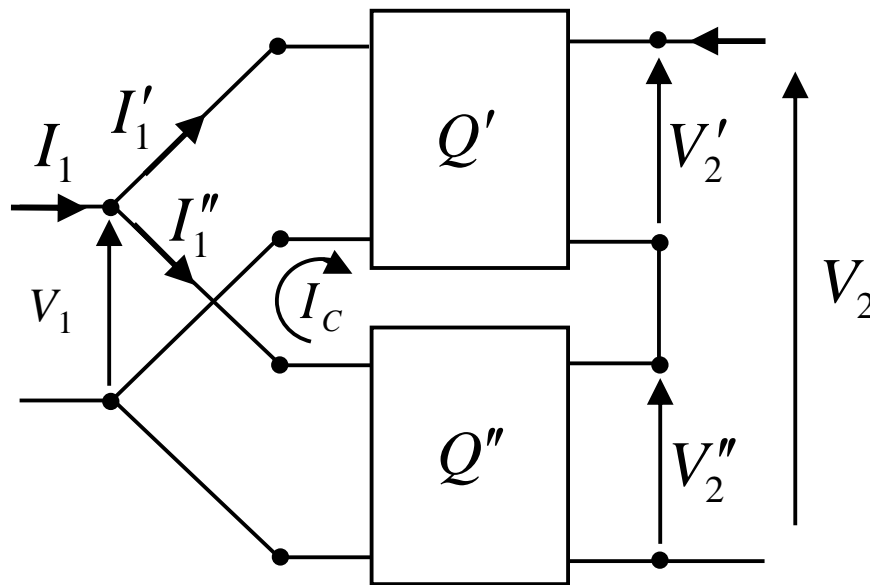

Brune Tests:

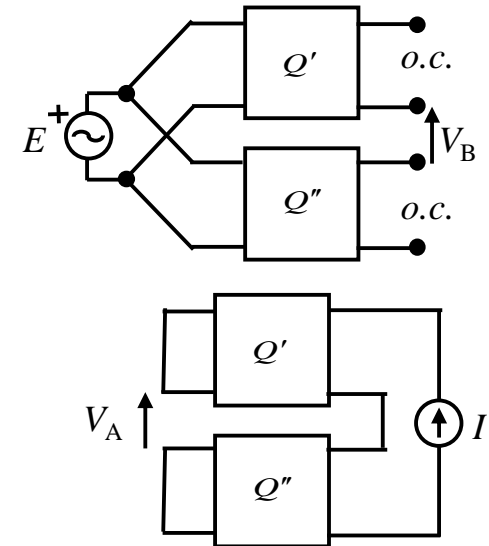


If $V_B=0 \forall E$ and $V_A=0 \forall I \Rightarrow I_C=0$.

$$\text{if all } I_C = 0 \Rightarrow \begin{cases} I_1 = I_1' + I_1'' = (g_{11}' + g_{11}'')V_1 + (g_{12}' + g_{12}'')I_2 \\ V_2 = V_2' + V_2'' = (g_{21}' + g_{21}'')V_1 + (g_{22}' + g_{22}'')I_2 \end{cases}$$

Association of Q's

Cascaded

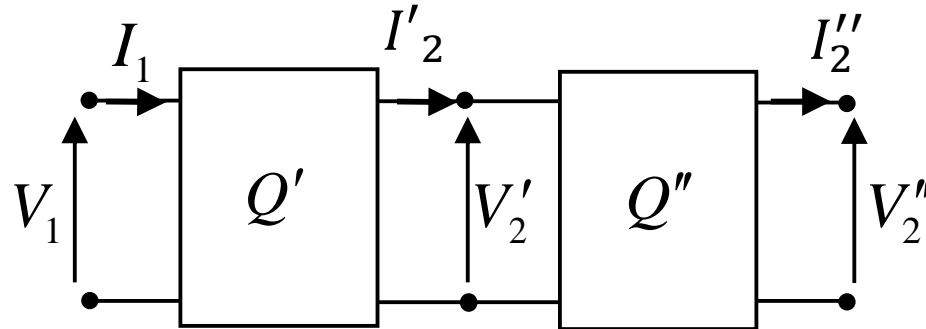

$$\begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \begin{pmatrix} A' & B' \\ C' & D' \end{pmatrix} \begin{pmatrix} V'_2 \\ I'_2 \end{pmatrix} = \begin{pmatrix} A' & B' \\ C' & D' \end{pmatrix} \begin{pmatrix} A'' & B'' \\ C'' & D'' \end{pmatrix} \begin{pmatrix} V''_2 \\ I''_2 \end{pmatrix}$$

For $n=1$ to N Q's connected in cascade: $\begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \prod_{n=1}^N \mathbf{T}_n \begin{pmatrix} V_2 \\ I_2 \end{pmatrix}$