

U3. Power transfer theorems and image parameters

Circuit Analysis, GIT

Philip Siegmann

Departamento de Teoría de la Señal y Comunicaciones

philip.siegmann@uah.es


Curso 2016-2017

Index

- Introduction: Typical circuit configuration
- Recall
 - Equivalent impedance
 - Equivalent Thevenin and Norton
- Maximum power supply. Impedance Matching
- Power transfer. Everitt Theorem.
- Transmission Units
- Image Parameters
- Cascaded association using image param.

Typical circuit configuration

Equivalent Thevenin, (E_{Th}, Z_{Th})

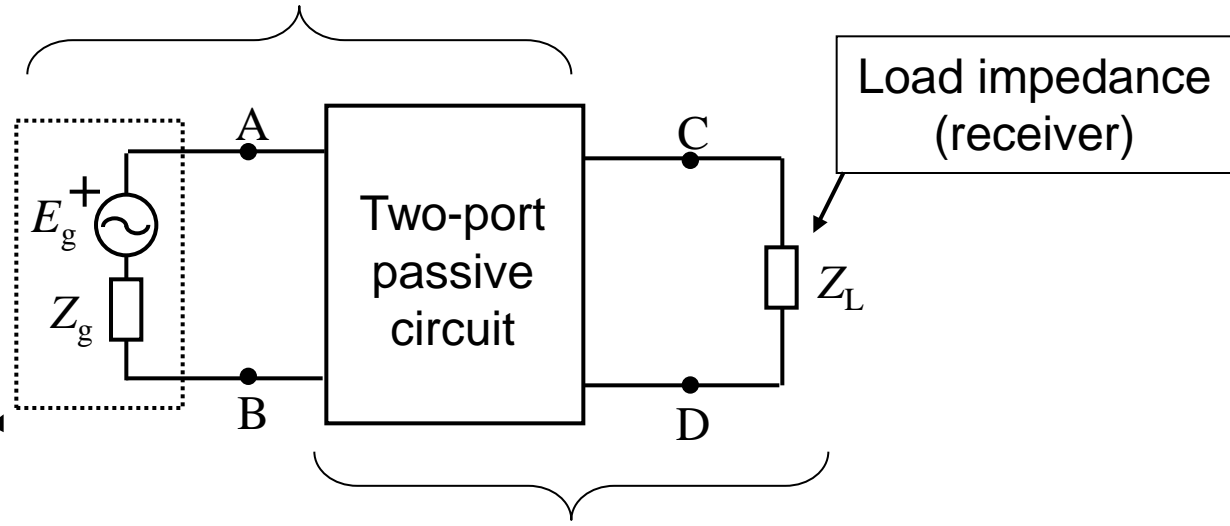


Energy supply (real voltage or current source)

Load impedance (receiver)


Equivalent impedance, Z_{eq}

Equivalent circuits:

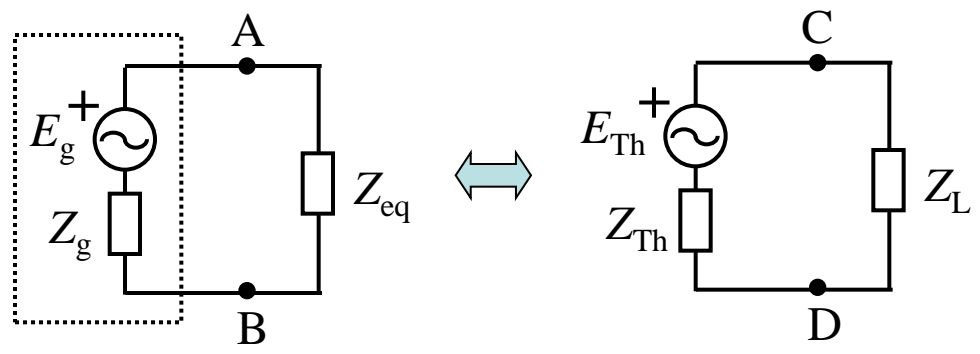


Recall: Equivalent Impedance

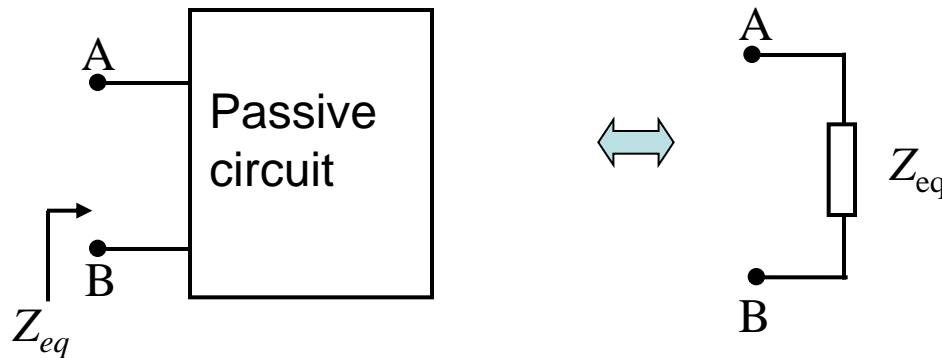- Any passive circuit (i.e. without independent sources) between two terminals (A,B) can be simplified with a equivalent impedance, Z_{eq} :




The equivalent impedance can be obtained by:

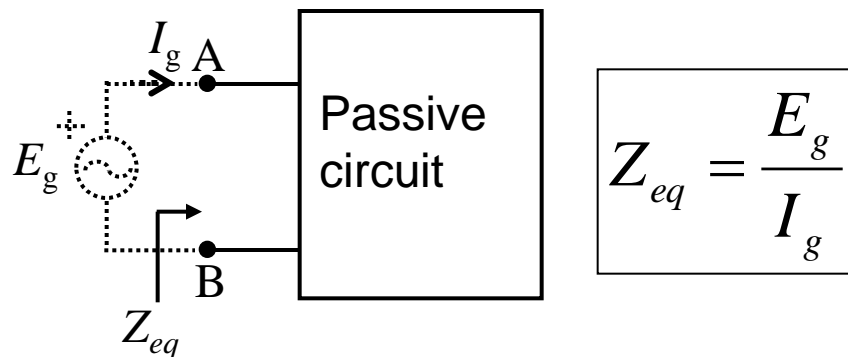- Parallel and/or serial association of the impedances within the passive circuit.
- Applying a test generator E_g :




Recall: Equivalent Thevenin & Norton

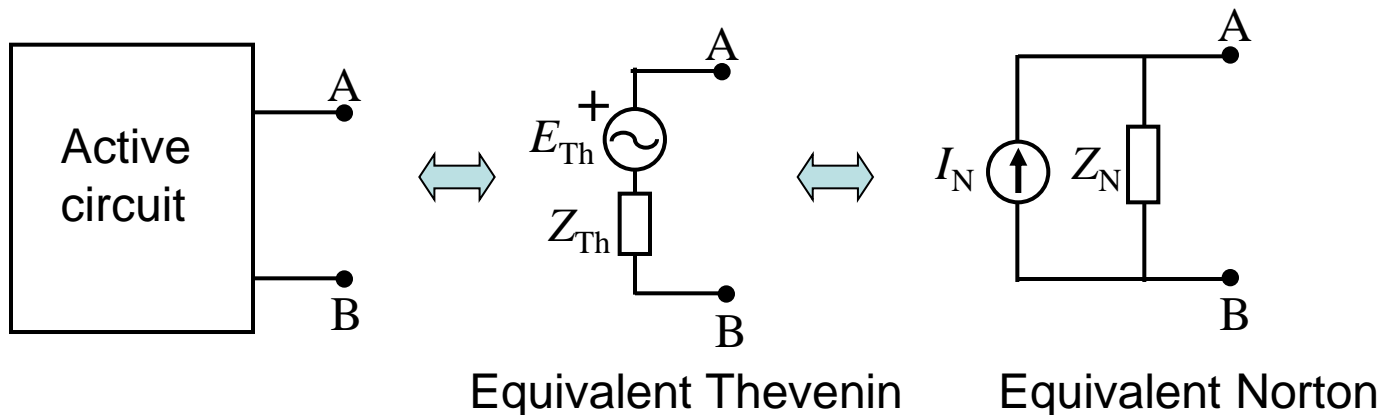- Any linear circuit with independent sources (i.e. active circuit) between two terminals (A,B) can be simplified by a real voltage source (Equiv.Thevenin) or real current source (Equiv. Norton):




Recall: Equivalent Thevenin

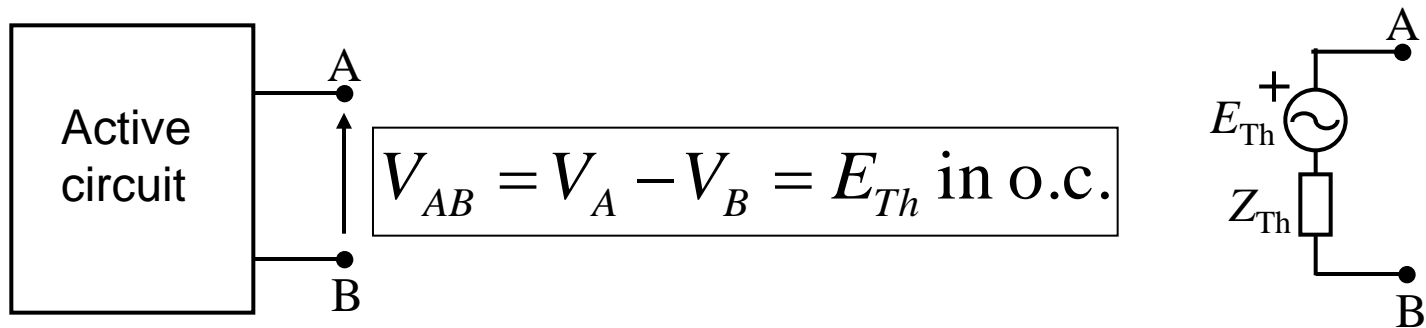- E_{Th} is the voltage between A and B in open circuit:



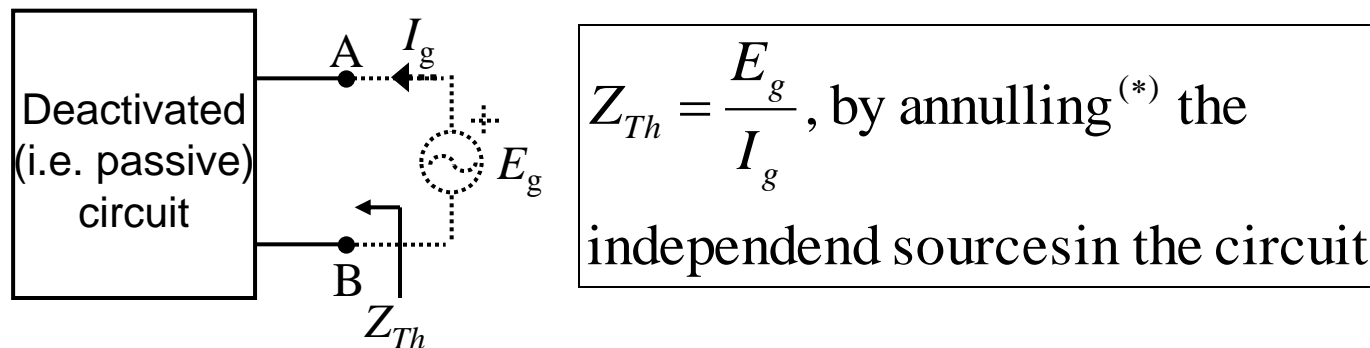
- Z_{th} is the equivalent impedance seen through A-B



(*) see slide 4


Recall: Equivalent Norton

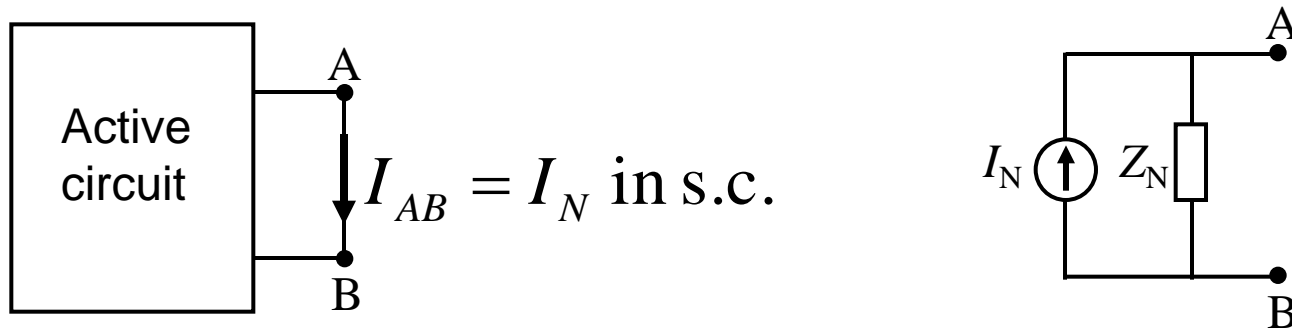- I_N is the current between A and B in short circuit:




- Z_N (as Z_{Th}) is the equivalent impedance seen through A-B
- Equivalencies between the real Thevenin and Norton sources:
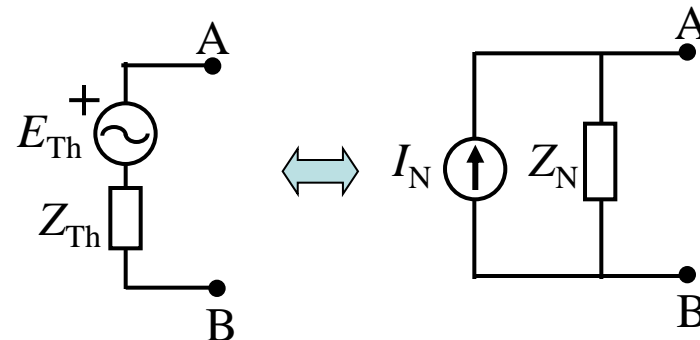
$$\begin{cases} E_{Th} = Z_N I_N \\ Z_{Th} = Z_N \end{cases}$$



Maximum power supply

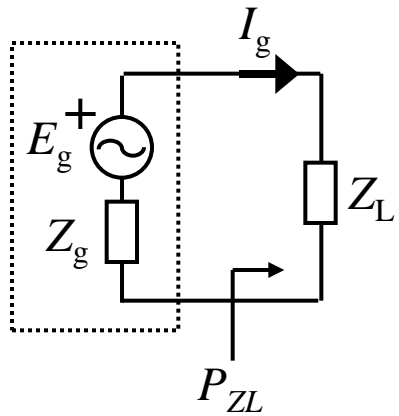- When does a real generator (E_g, Z_g) supply the maximum power to a load impedance Z_L ?




$$\begin{cases} Z_g = a + jb & \text{fixed} \\ Z_L = x + jy & \text{variable} \end{cases}$$

$$P_{ZL} = \frac{1}{2} |I_g|^2 \operatorname{Re}[Z_L] = \frac{|E_g|^2}{2} \frac{x}{|a + x + j(b + y)|^2}$$

$$P_{ZL} = P_{ZL}|_{\max} \Leftrightarrow \begin{cases} x = a \\ y = -b \end{cases} \Leftrightarrow Z_L = Z_g^* \Leftrightarrow \text{Impedance matching and } P_{ZL}|_{\max} = \frac{|E_g|^2}{8a}$$

Everitt theorem

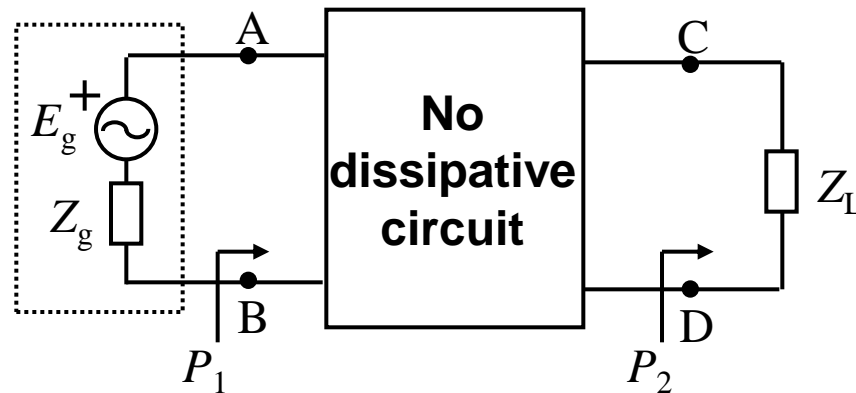- When there is maximum power supply at the input gate (P_1) of a **non-dissipative circuit** (i.e. made of L and C only) then there is also maximum power supply at the output (P_2) of the circuit and vice versa:



$$P_1 = P_1|_{\max} \Leftrightarrow P_2 = P_2|_{\max}$$

Impedance matching at A - B \Leftrightarrow Impedance matching at C - D

Transmission units



- For measuring the signal transmission through a circuit the following magnitudes are usually used:

- Transmission loss:


$$\frac{\text{circuit input signal}}{\text{circuit output signal}}$$

- Insertion loss:
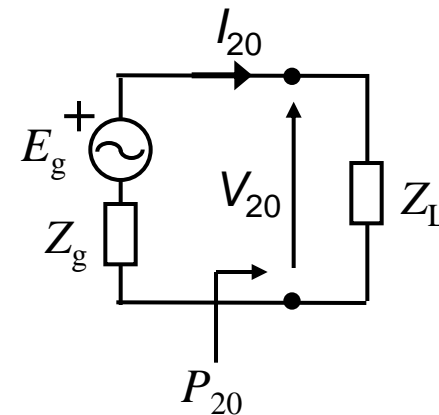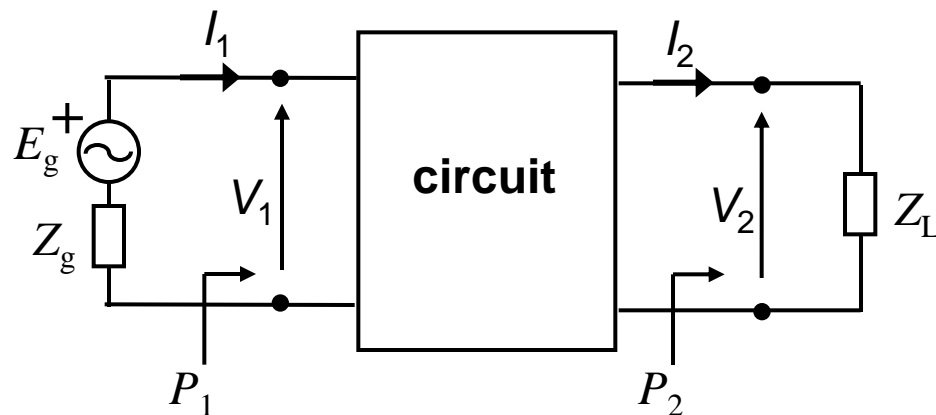
$$\frac{\text{supplied signal without circuit}}{\text{circuit output signal}}$$




Transmission loss

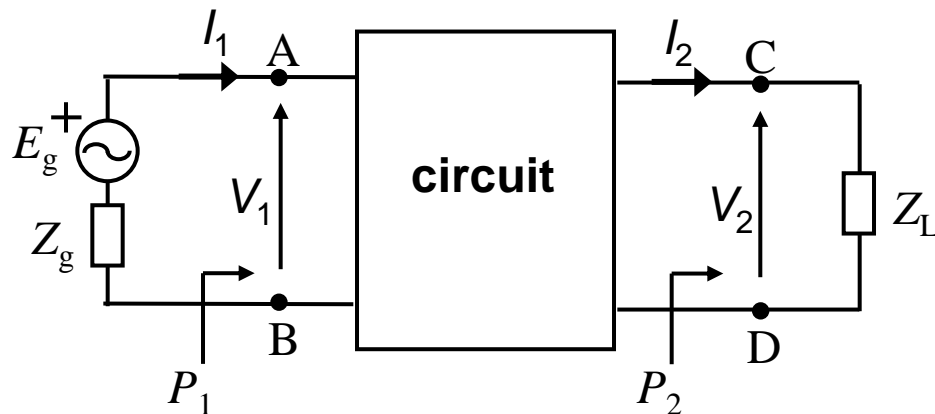

	Corriente	Tensión	Potencia
U. naturales	$l_T = \frac{ I_1 }{ I_2 }$	$l_T = \frac{ V_1 }{ V_2 }$	$l_T = \frac{P_1}{P_2}$
Decibelios	$L_T = 20 \log \frac{ I_1 }{ I_2 } [\text{dB}]$	$L_T = 20 \log \frac{ V_1 }{ V_2 } [\text{dB}]$	$L_T = 10 \log \frac{P_1}{P_2} [\text{dB}]$
Neperios	$L_T = \ln \frac{ I_1 }{ I_2 } [\text{Np}]$	$L_T = \ln \frac{ V_1 }{ V_2 } [\text{Np}]$	$L_T = \frac{1}{2} \ln \frac{P_1}{P_2} [\text{Np}]$

Insertion loss

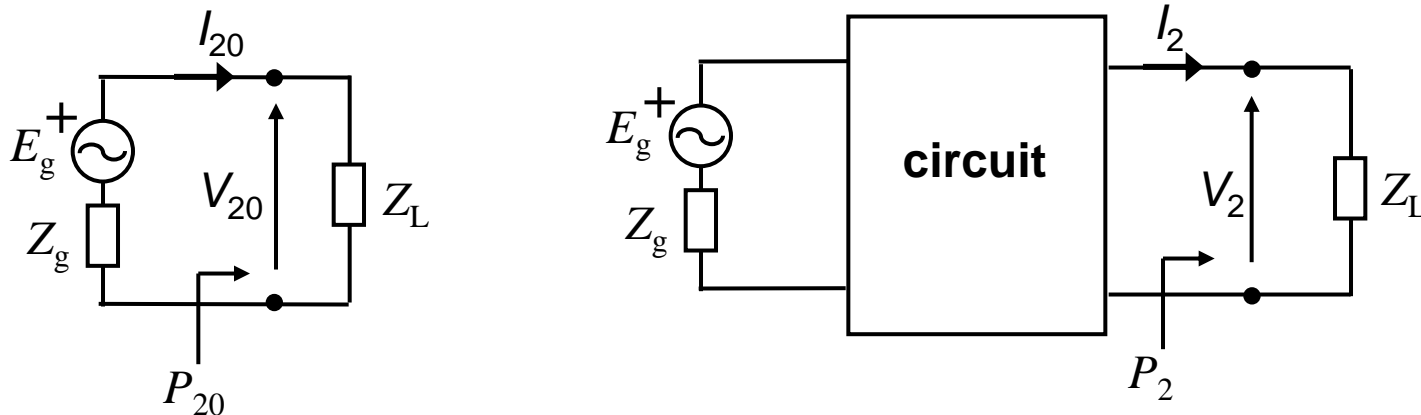

	Corriente	Tensión	Potencia
U. naturales	$l_I = \frac{ I_{20} }{ I_2 }$	$l_I = \frac{ V_{20} }{ V_2 }$	$l_I = \frac{P_{20}}{P_2}$
Decibelios	$L_I = 20 \log \frac{ I_{20} }{ I_2 } [\text{dB}]$	$L_I = 20 \log \frac{ V_{20} }{ V_2 } [\text{dB}]$	$L_I = 10 \log \frac{P_{20}}{P_2} [\text{dB}]$
Neperios	$L_I = \ln \frac{ I_{20} }{ I_2 } [\text{Np}]$	$L_I = \ln \frac{ V_{20} }{ V_2 } [\text{Np}]$	$L_I = \frac{1}{2} \ln \frac{P_{20}}{P_2} [\text{Np}]$

Are the different insertion loss the same if in dB and Np?

Transmission units

- Transmission gain:


	Corriente	Tensión	Potencia
U. naturales ($g=1/l$)	$g_T = \frac{ I_2 }{ I_1 }$	$g_T = \frac{ V_2 }{ V_1 }$	$g_T = \frac{P_2}{P_1}$
Decibelios ($G=-L$)	$G_T = 20 \log \frac{ I_2 }{ I_1 } [\text{dB}]$	$G_T = 20 \log \frac{ V_2 }{ V_1 } [\text{dB}]$	$G_T = 10 \log \frac{P_2}{P_1} [\text{dB}]$
Neperios ($G=-L$)	$G_T = \ln \frac{ I_2 }{ I_1 } [\text{Np}]$	$G_T = \ln \frac{ V_2 }{ V_1 } [\text{Np}]$	$G_T = \frac{1}{2} \ln \frac{P_2}{P_1} [\text{Np}]$

- Insertion gain:

	Corriente	Tensión	Potencia
U. naturales ($g=1/l$)	$g_I = \frac{ I_2 }{ I_{20} }$	$g_I = \frac{ V_2 }{ V_{20} }$	$g_I = \frac{P_2}{P_{20}}$
Decibelios ($G=-L$)	$G_I = 20 \log \frac{ I_2 }{ I_{20} } [\text{dB}]$	$G_I = 20 \log \frac{ V_2 }{ V_{20} } [\text{dB}]$	$G_I = 10 \log \frac{P_2}{P_{20}} [\text{dB}]$
Neperios ($G=-L$)	$G_I = \ln \frac{ I_2 }{ I_{20} } [\text{Np}]$	$G_I = \ln \frac{ V_2 }{ V_{20} } [\text{Np}]$	$G_I = \frac{1}{2} \ln \frac{P_2}{P_{20}} [\text{Np}]$

Image parameters of a bilateral Q

Image impedances Z_{01} y Z_{02}

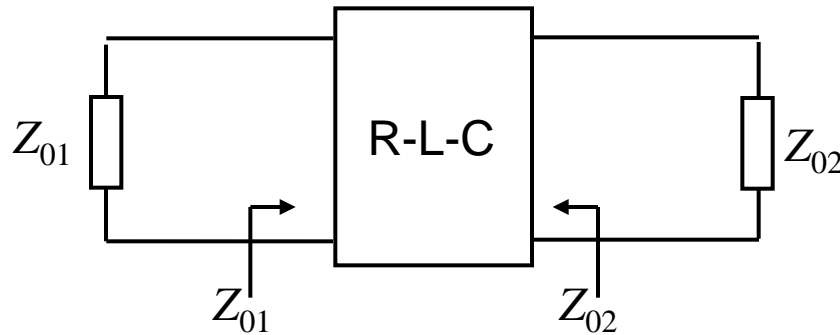

Propagation constant γ

$$\exp(2\gamma) = \frac{V_1 I_1}{V_2 I_2} \Big|_{Z_L = Z_{02}}$$

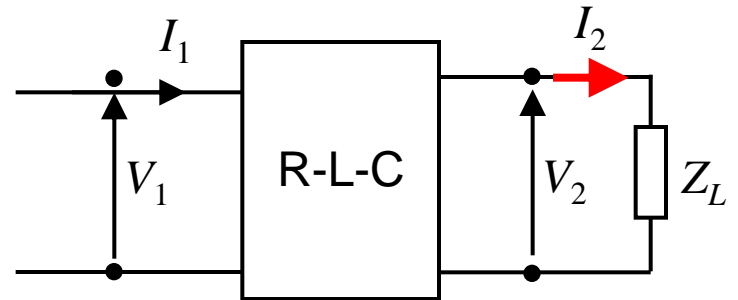


Image parameters for a bilateral and symmetrical Q

Characteristic impedance ($Z_0 = Z_{01} = Z_{02}$) and propagation constant (γ) can be obtained as follows:

$$Z_0 = \sqrt{\frac{B}{C}} = \sqrt{Z_{O.C.} Z_{S.C.}}, \quad \tanh \gamma = \frac{\sqrt{BC}}{A} = \sqrt{\frac{Z_{S.C.}}{Z_{O.C.}}}, \quad \gamma = \frac{1}{2} \ln \frac{1 + \tanh \gamma}{1 - \tanh \gamma}$$

being $Z_{O.C.}$ y $Z_{S.C.}$ impedances seen trough Q when the ports of the opposite side are respectively open- and short-circuit:


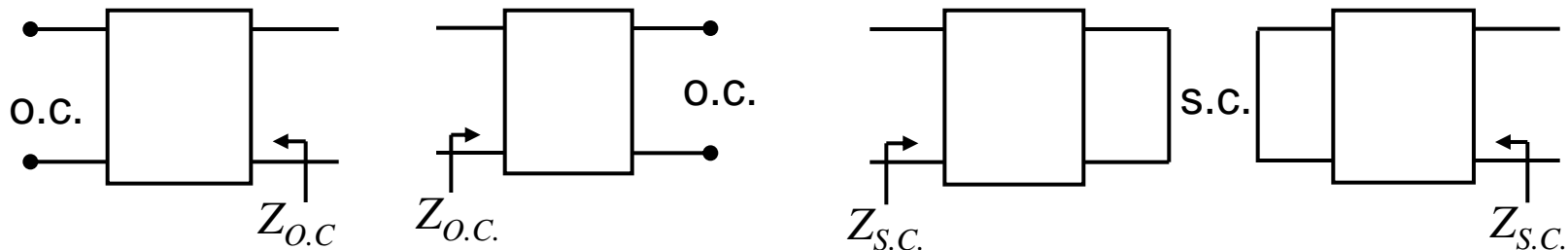


Image parameters for a bilateral and symmetrical Q

Propagation constant γ

$$\exp(\gamma) = \frac{V_1}{V_2} \Big|_{Z_L=Z_0} = \frac{I_1}{I_2} \Big|_{Z_L=Z_0},$$

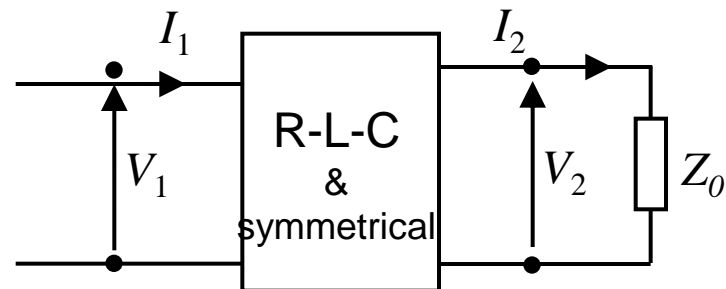

$\gamma = \alpha + j\beta$, β : phase difference, α : **transmission loss** (= insertion loss)


$$\alpha[\text{Np}] = \ln \left| \frac{V_1}{V_2} \right|_{Z_L=Z_0} = \ln \left| \frac{I_1}{I_2} \right|_{Z_L=Z_0} = \frac{1}{2} \ln \frac{P_1}{P_2} \Big|_{Z_L=Z_0}$$

$$\begin{aligned} \alpha[\text{dB}] &= 20 \log_{10} \left| \frac{V_1}{V_2} \right| \\ &= 20 \log_{10} \left| \frac{I_1}{I_2} \right| \\ &= 10 \log_{10} \frac{P_1}{P_2} \end{aligned}$$


“T” as function of Z_0 and γ

$$\begin{pmatrix} A & B \\ C & D \end{pmatrix} = \begin{pmatrix} \cosh \gamma & Z_0 \sinh \gamma \\ \frac{1}{Z_0} \sinh \gamma & \cosh \gamma \end{pmatrix}$$

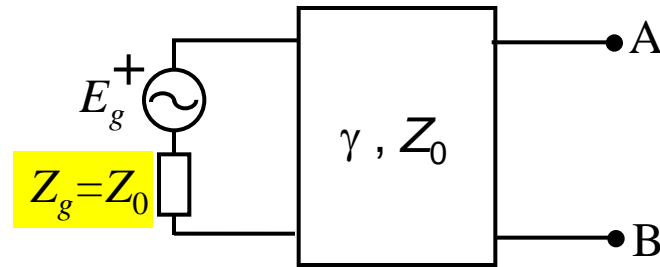Equivalent Thevenin for a bilateral and symmetrical Q when $Z_g = Z_0$




Equivalent Thevenin:

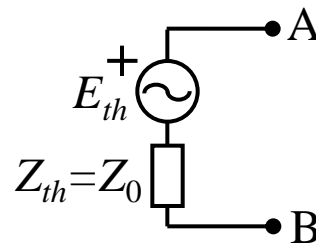


$$E_{th} = \frac{E_g}{CZ_g + A} = \frac{E_g}{\frac{1}{Z_0} \sinh \gamma \cdot Z_0 + \cosh \gamma} = E_g \exp(-\gamma)$$

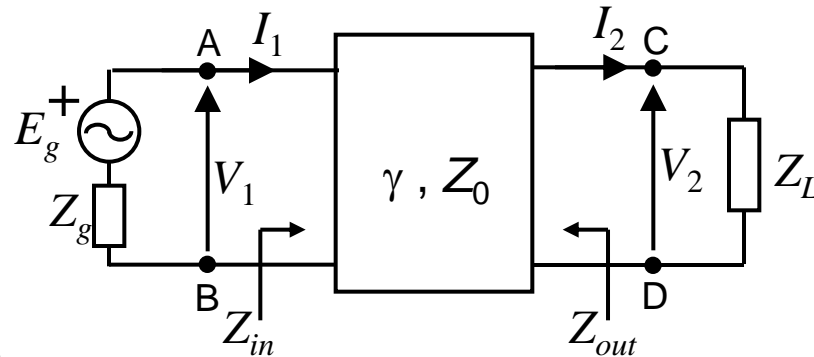Summarizing, for a bilateral and symmetric quadripole




Equivalent circuits:

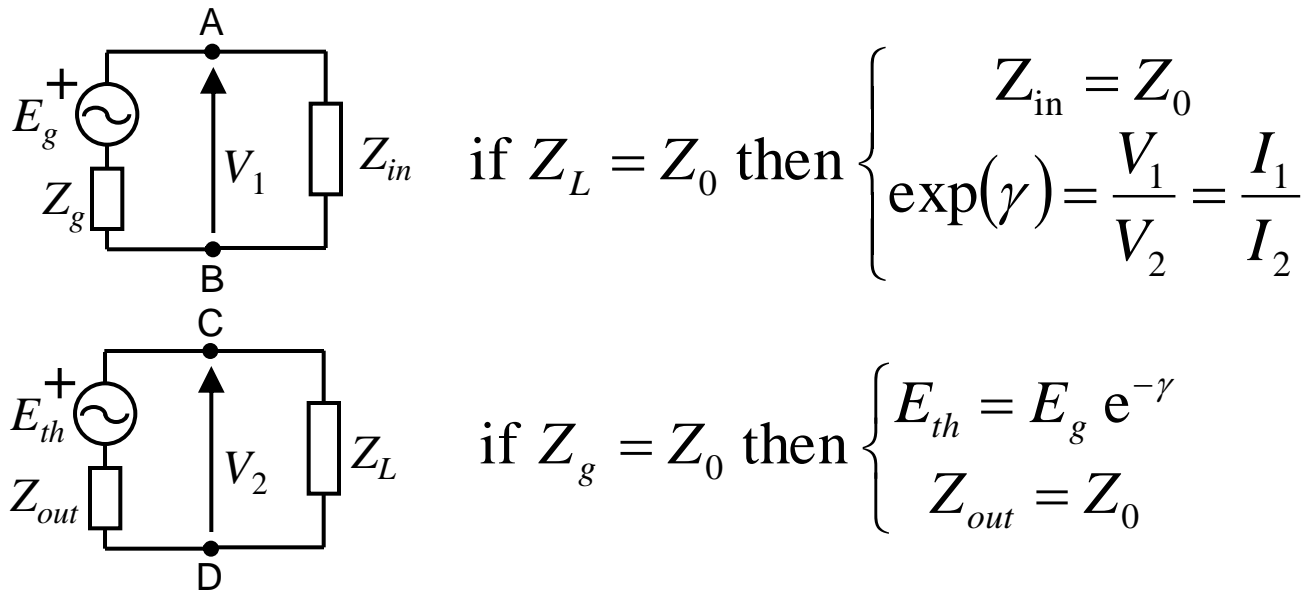

Cascaded association using image parameters

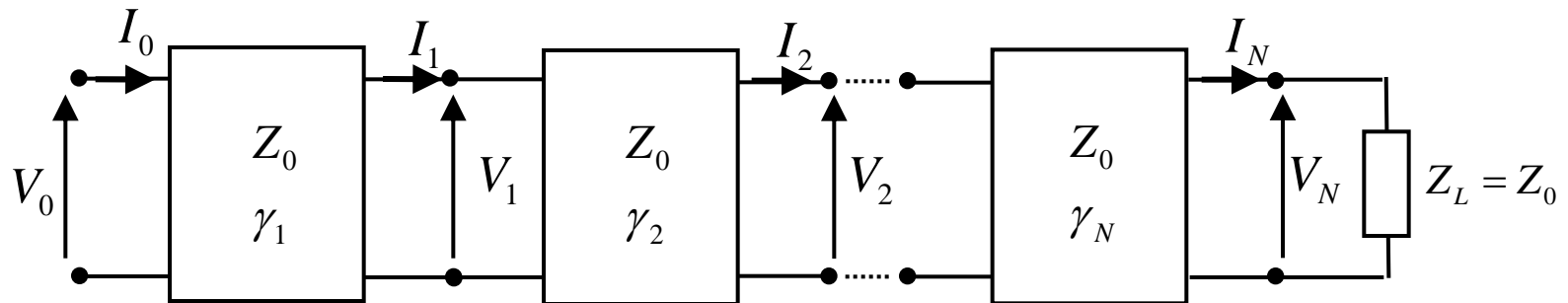N bilateral and symmetric quadripoles (all with the same Z_0) connected in cascade:



$$V_N = V_{N-1} e^{-\gamma_N} = V_{N-2} e^{-\gamma_{N-1}} e^{-\gamma_N} = \dots = V_0 e^{-(\gamma_1 + \gamma_2 + \dots + \gamma_N)}$$

$$I_N = I_0 e^{-(\gamma_1 + \gamma_2 + \dots + \gamma_N)}$$