

U4. Introduction to passive filters

Circuit Analysis, Grado en Ingeniería de Comunicaciones
Curso 2013-2014

Philip Siegmann (philip.siegmann@uah.es)
Departamento de Teoría de la Señal y Comunicaciones






Introduction

- **Definition** of a filter: A device (i.e. quadripole) that selects a interval of frequencies from an input signal, whose amplitudes and phase can be modified.
- **Analogical** filters (signal is no discrete)
 - **Passive**: made only with R,L and C
 - **Active**: have also operational amplifiers, transistors,...
- **Digital** filters (signal is discrete)



Introduction

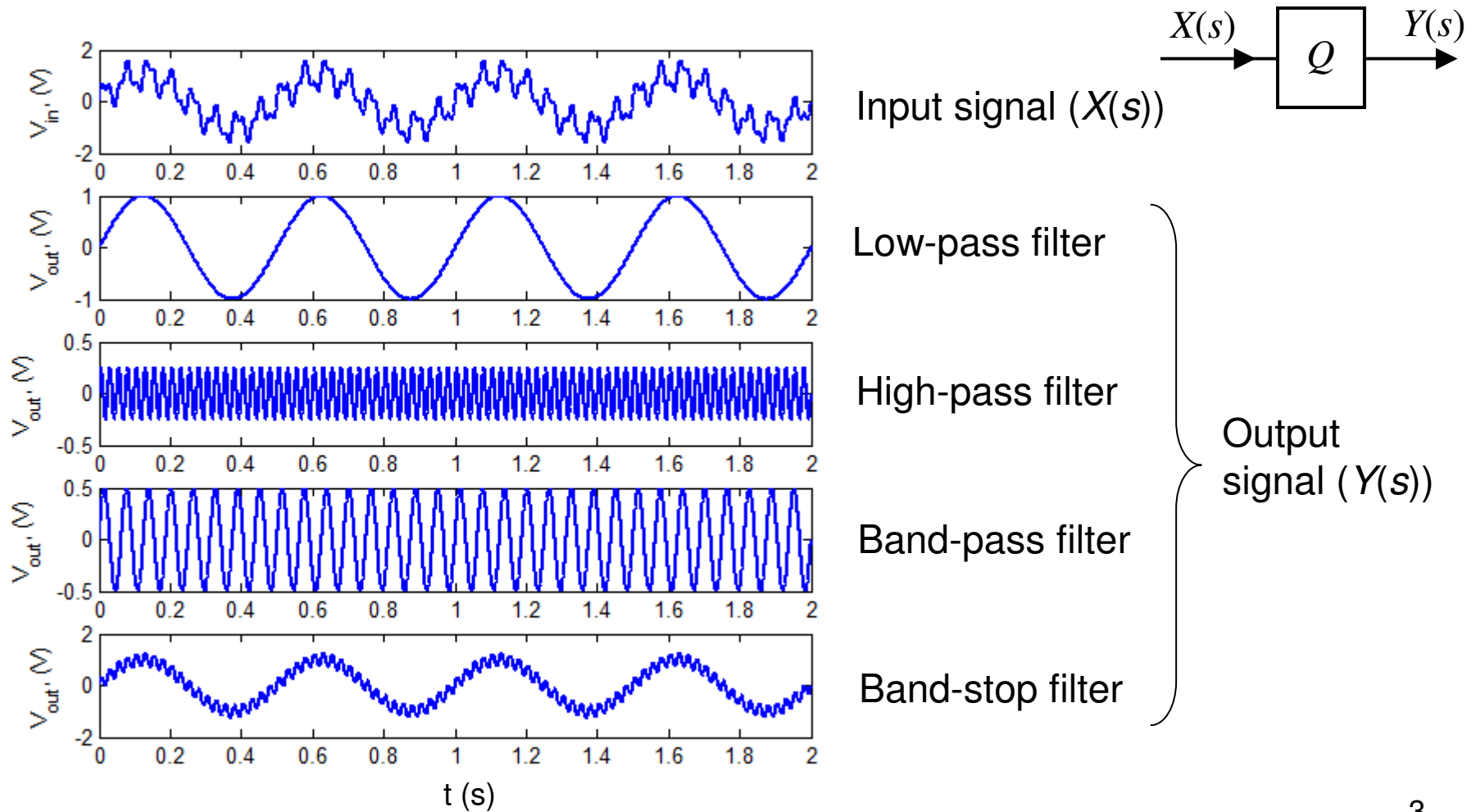Classification according to the selected range of frequencies






Transfer Function $H(s)$

- Definition (Laplace Transform domain (\mathcal{L}))
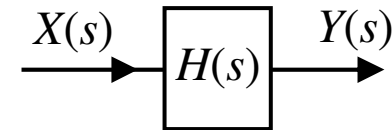
$$H(s) = \frac{Y(s)}{X(s)} = \frac{\mathcal{L}[\text{output signal}]}{\mathcal{L}[\text{input signal}]},$$




with initial conditions equal zero ($v_C(0)=i_L(0)=0$).

$H(s)$ is independent of the applied signal.

Note that $H(s)=Y(s)$ when $x(t)=\delta(t)$, ($h(t)=\mathcal{L}^{-1}[H]$ is the *impulse response*).

- For example

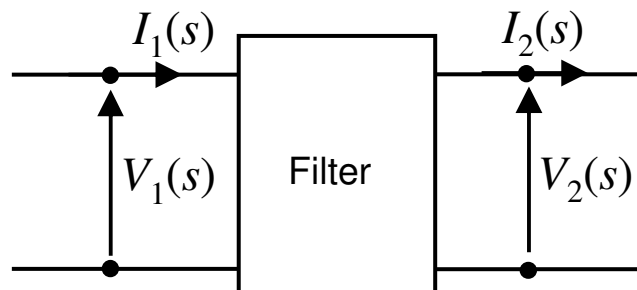

$$G_V(s) = \frac{V_2(s)}{V_1(s)}, \quad Z_T(s) = \frac{V_2(s)}{I_1}$$

$$G_I(s) = \frac{I_2(s)}{I_1(s)}, \quad Y_T(s) = \frac{I_2(s)}{V_1(s)}$$



Transfer Function

- Example 1

$$H_1(s) = \frac{V_2(s)}{V_1(s)} = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} = \frac{1}{RC} \cdot \frac{1}{s + \frac{1}{RC}}$$

- Example 2

$$H_2(s) = \frac{V_2(s)}{V_1(s)} = \frac{R + sL}{sL + 2R + \frac{1}{sC}} = \frac{s^2 + \frac{R}{L}s}{s^2 + \frac{2R}{L}s + \frac{1}{LC}}$$

What kind of filter are they?



Poles and zeros of $H(s)$

- $H(s)$ can be written as a fraction of two polynomials with real-valued and positive coefficients:

$$H(s) = K \frac{s^M + a_{M-1}s^{M-1} + \dots + a_1}{s^N + b_{N-1}s^{N-1} + \dots + b_1} = K \frac{\prod_M (s - c_m)}{\prod_N (s - p_n)}$$

where c_m and p_m are the **zeros** and the **poles** of the transfer function:

$$\lim_{s \rightarrow c_m} \{H(s)\} \rightarrow 0$$

$$\lim_{s \rightarrow p_m} \{H(s)\} \rightarrow \infty$$

zeros and the poles can also be at $s \rightarrow \infty$



Pole-zero plot

- The poles and zeros are usually represented in a complex plane called the **pole-zero plot** to help to convey certain properties of the circuit
- The poles and zeros are either real or complex conjugated
- Poles are represented with “x”
- Zeros are represented with “o”



Frequency response of the Transfer Function: $H(\omega)$

- Frequency response using sinusoidal signals, then $s=j\omega$:

$$H(\omega) = K \frac{\prod_M (j\omega - c_m)}{\prod_N (j\omega - p_n)} = |H(\omega)| \exp(j\phi(\omega))$$

where

$$|H(\omega)| = K \frac{\prod_M |j\omega - c_m|}{\prod_N |j\omega - p_n|}, \text{ is the amplitude response,}$$

$$\phi(\omega) = \arctan \frac{\text{Im}[H(\omega)]}{\text{Re}[H(\omega)]}, \text{ is the phase response.}$$

- $|H(\omega)|$ becomes high for ω close to p_n
- $|H(\omega)|$ becomes low for ω close to c_m



Pole-zero plot and $|H(\omega)|$


- Example 3

$$H(s) \propto \frac{s - c_1}{(s - p_1)(s - p_2)}, \quad \begin{array}{l} \text{Poles at } s = p_1, p_2 \\ \text{Zero at } s = c_1 \end{array}$$

Poles at $s = -1 \pm j5$
Zero at $s = -5$

Poles at $s = -1 \pm j10$
Zero at $s = -5$

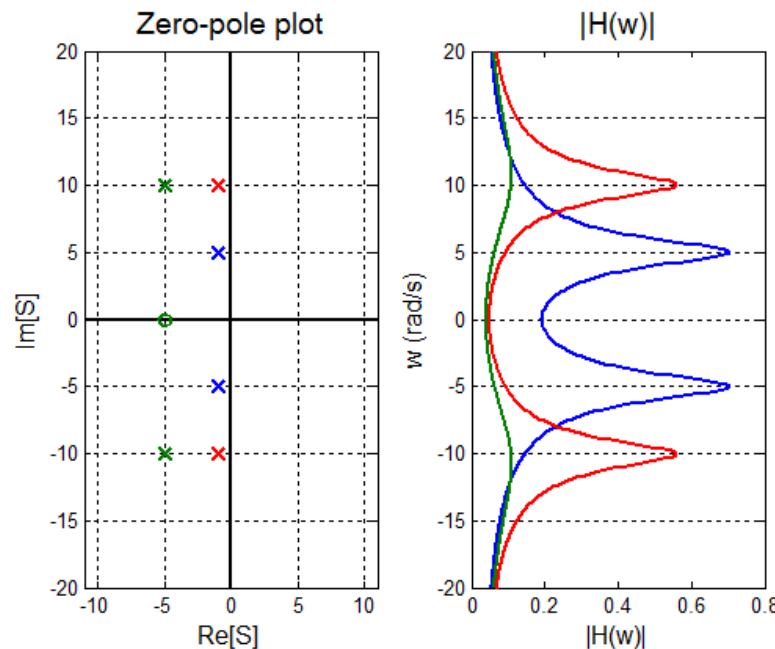Poles at $s = -5 \pm j10$
Zero at $s = -5$




The closer the pole to the imaginary axis, the more pronounced is the maximum



Pole-zero plot and $|H(\omega)|$

- Example 1

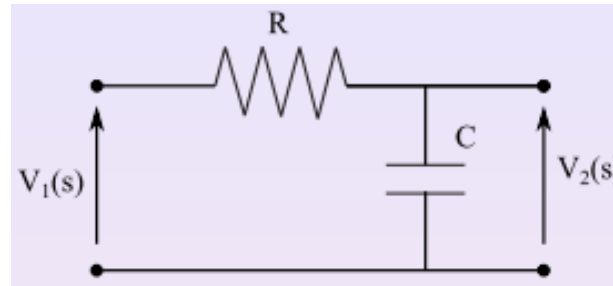



Data: $R=1 \text{ k}\Omega$, $C=100 \text{ }\mu\text{F}$

$$H(s) = \frac{\frac{1}{RC}}{s + \frac{1}{RC}} = \frac{10}{s + 10},$$

Pole at $s = -10$
Zero at $s \rightarrow \infty$

$$H(\omega) = \frac{10}{j\omega + 10} = \frac{10}{\sqrt{100 + \omega^2}} \exp(j\phi)$$


$$\phi = \arctan \frac{-\omega}{10}$$

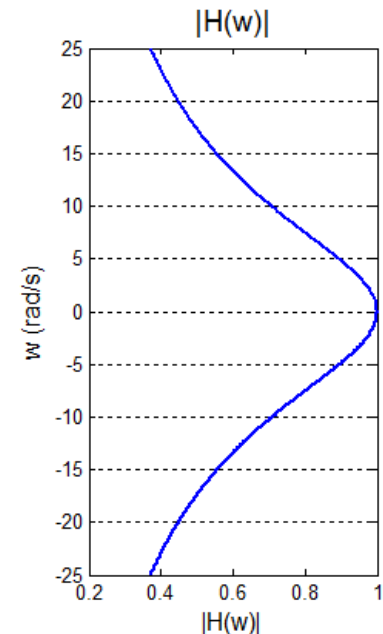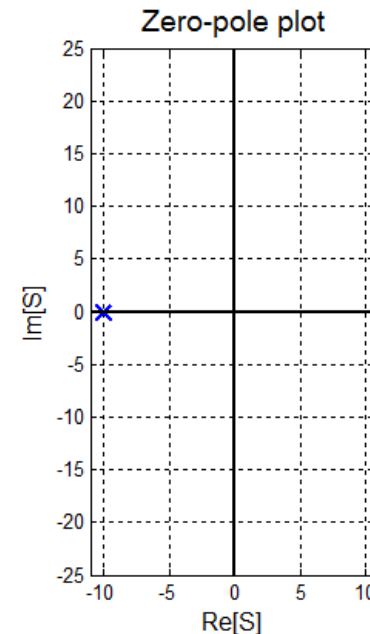



Pole-zero plot and $|H(\omega)|$

- Example 2

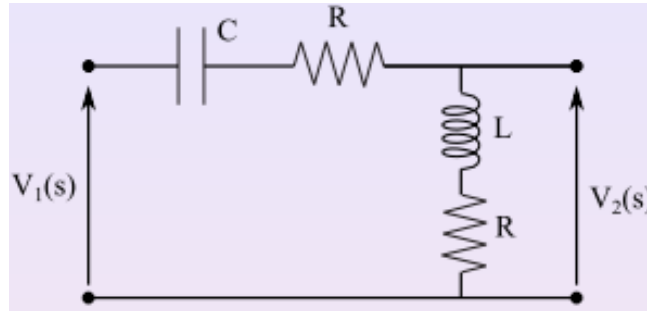



Data: $R=1 \Omega$, $C=1/5 \text{ F}$, $L=1 \text{ H}$

$$H(s) = \frac{s^2 + \frac{R}{L}s}{s^2 + \frac{2R}{L}s + \frac{1}{LC}} = \frac{s(s+1)}{(s+1-j2)(s+1+j2)}$$

Poles at $s = -1 \pm j2$


Zeros at $s = 0, -1$

$$H(\omega) = \frac{-\omega^2 + j\omega}{5 - \omega^2 + j2\omega}, \quad |H(\omega)| = \frac{\omega\sqrt{1+\omega^2}}{\sqrt{(5-\omega^2)^2 + 4\omega^2}}$$

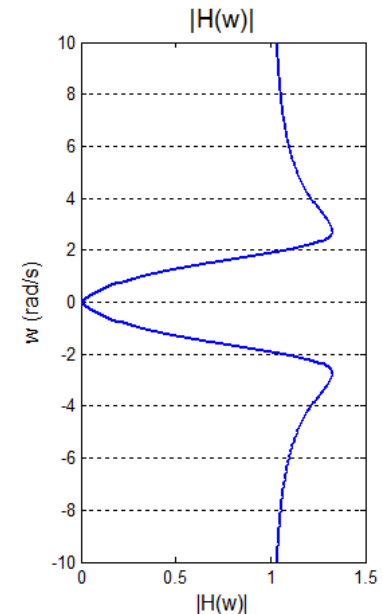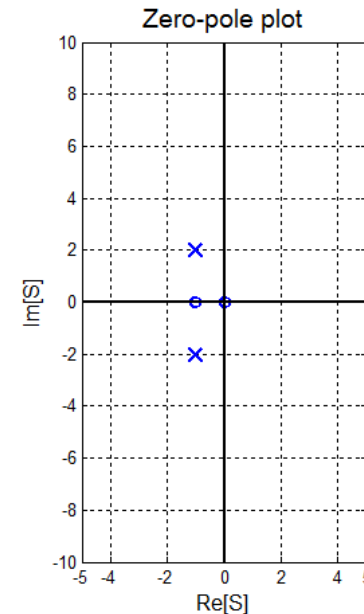




$H(s)$ between (E_g, R_g) and R_L

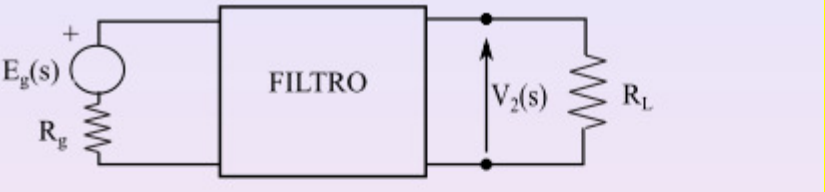

$$H(s) = \frac{V_2(s)}{E_g(s)}$$

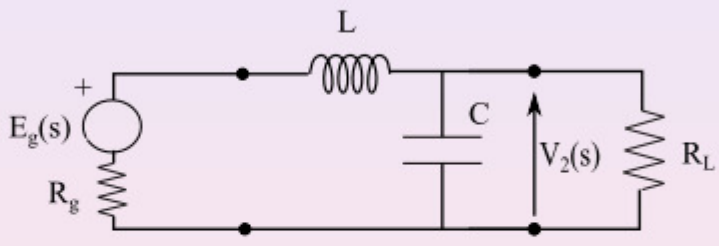

$$\frac{V_2(s) - E_g(s)}{R_g + sL} + sC V_2(s) + \frac{V_2(s)}{R_L} = 0$$

$$H(s) = \frac{V_2(s)}{E_g(s)} = \frac{R_L}{R_g + R_L} \cdot \frac{\frac{R_g + R_L}{LCR_L}}{s^2 + \left(\frac{1}{CR_L} + \frac{R_g}{L}\right)s + \frac{R_g + R_L}{LCR_L}}$$




RLC passive filters

- **Low-pass** filter
 - 1st order
 - 2nd order
- **High-pass** filter
 - 1st order
 - 2nd order
- **Band-pass** filter (2nd order)
- **Band-stop** filter (2nd order)




Example: Low-pass filter

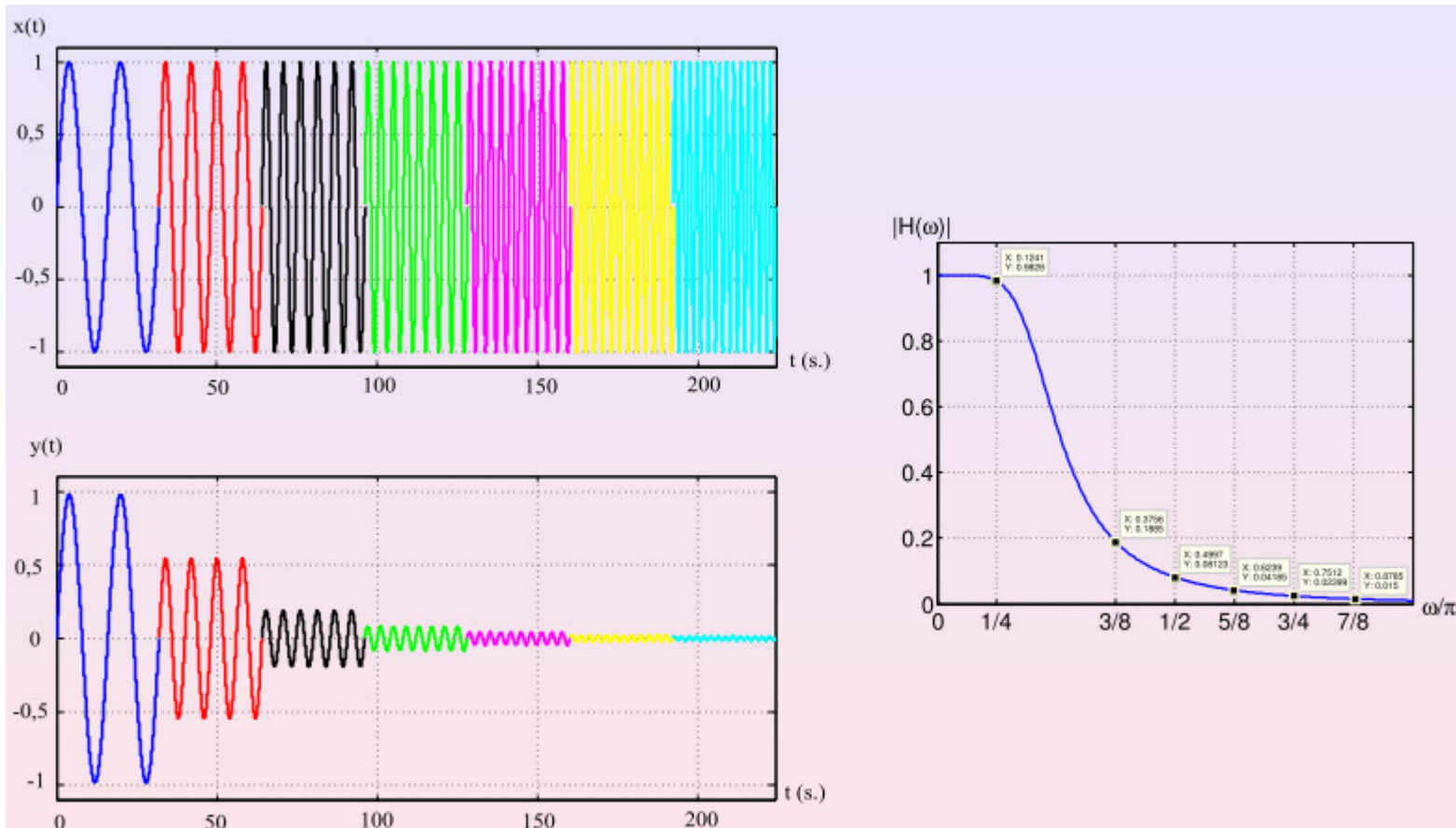




Example: High-pass filter

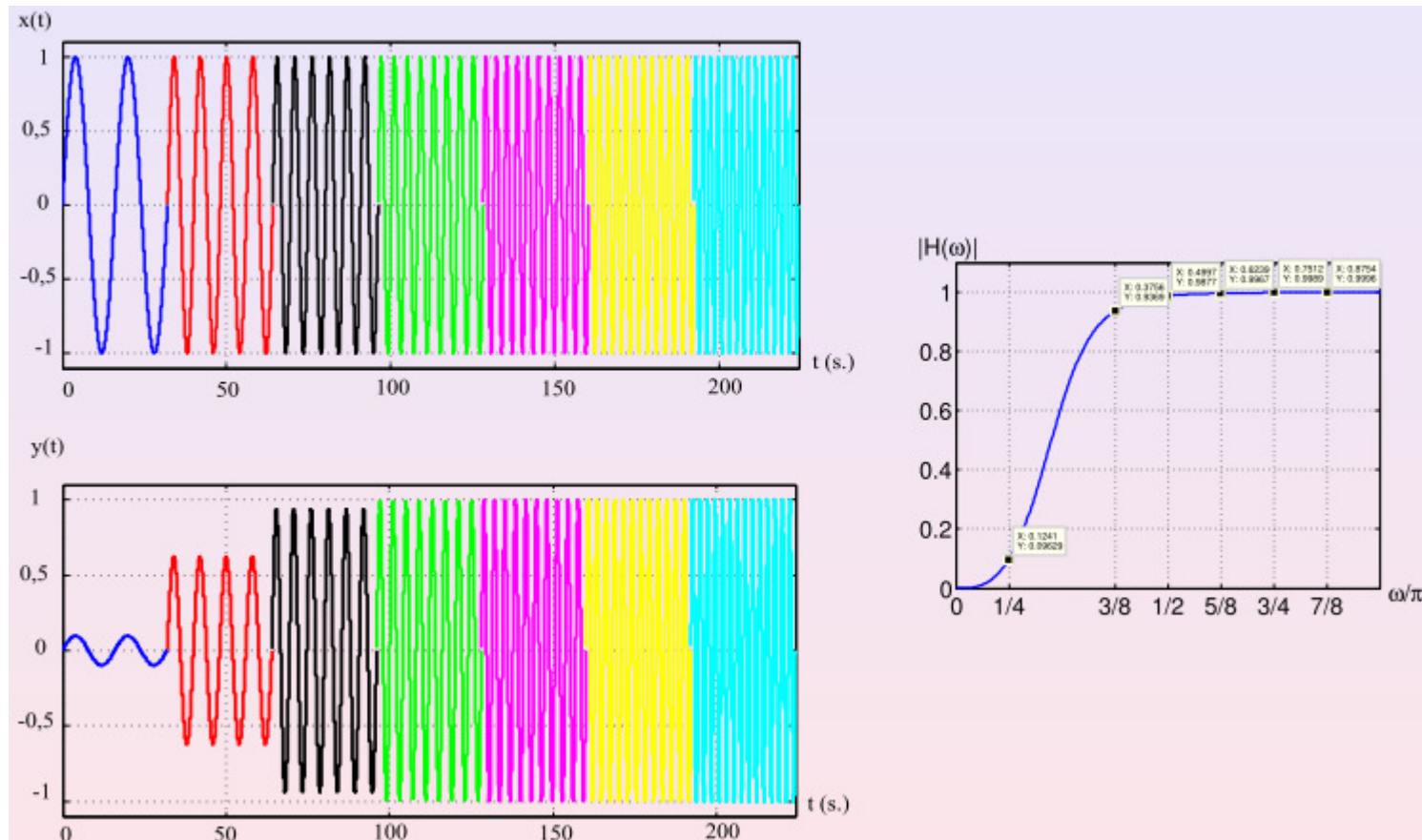




Example: Band-pass filter

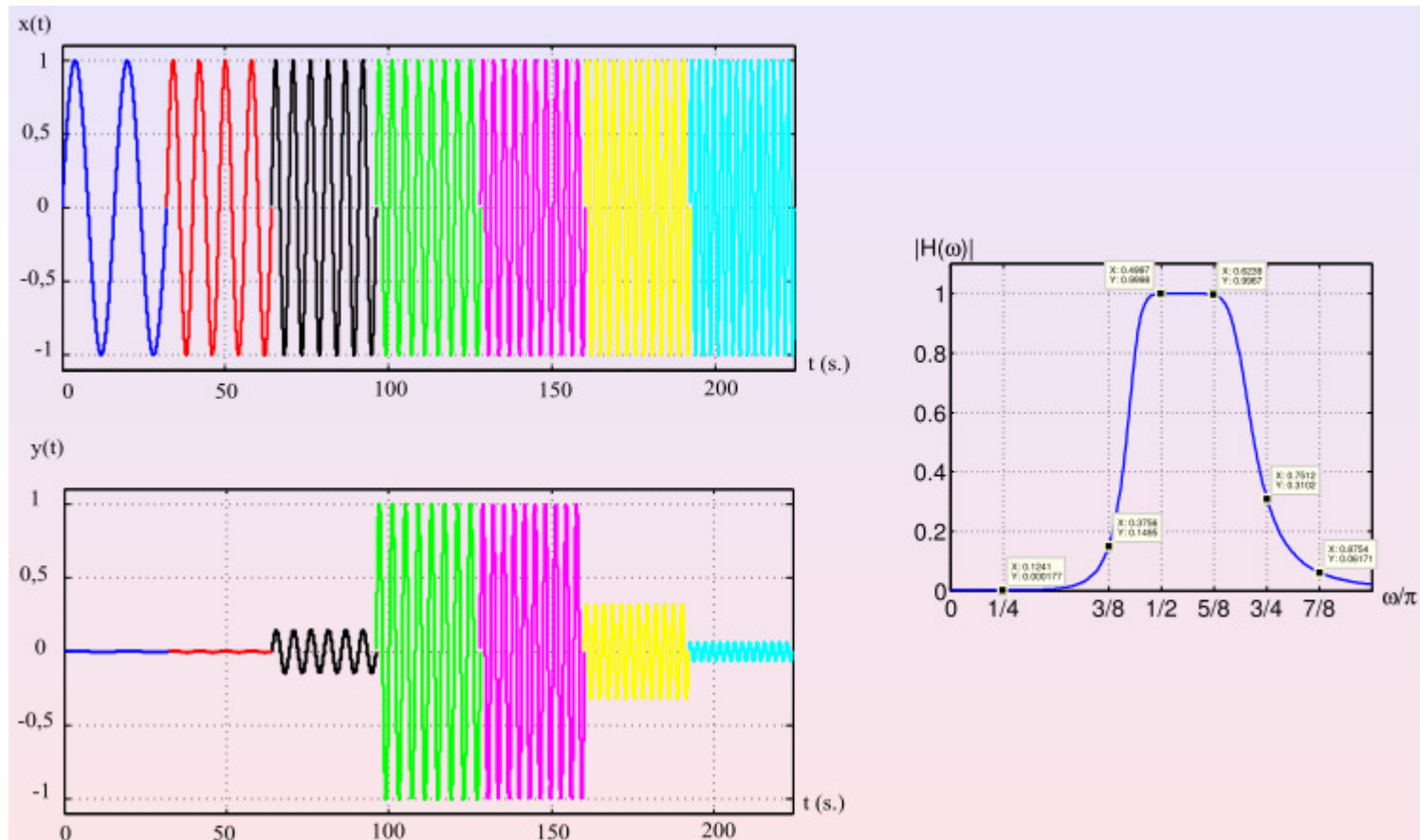




Example: Band-stop filter

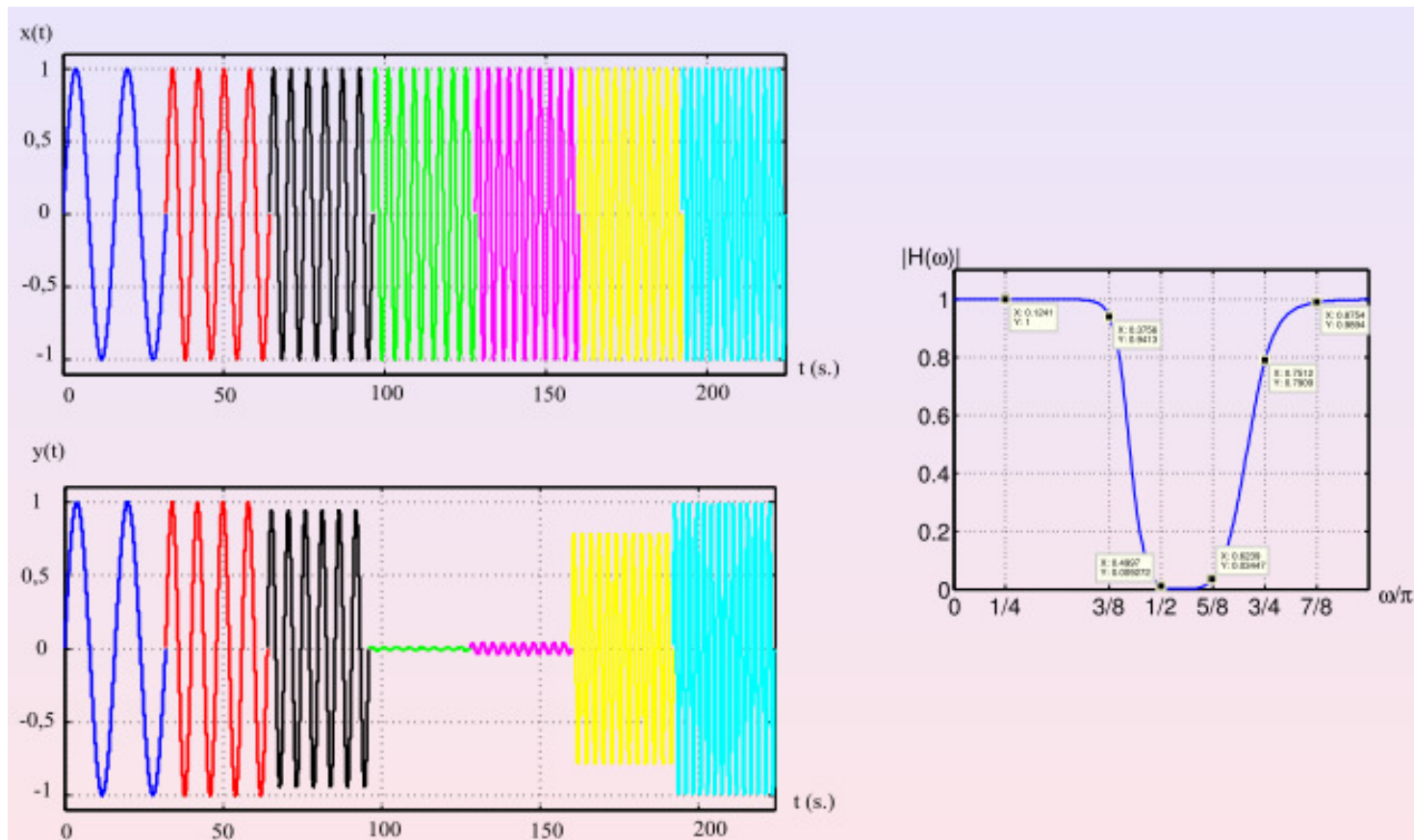



Ideal amplitude response

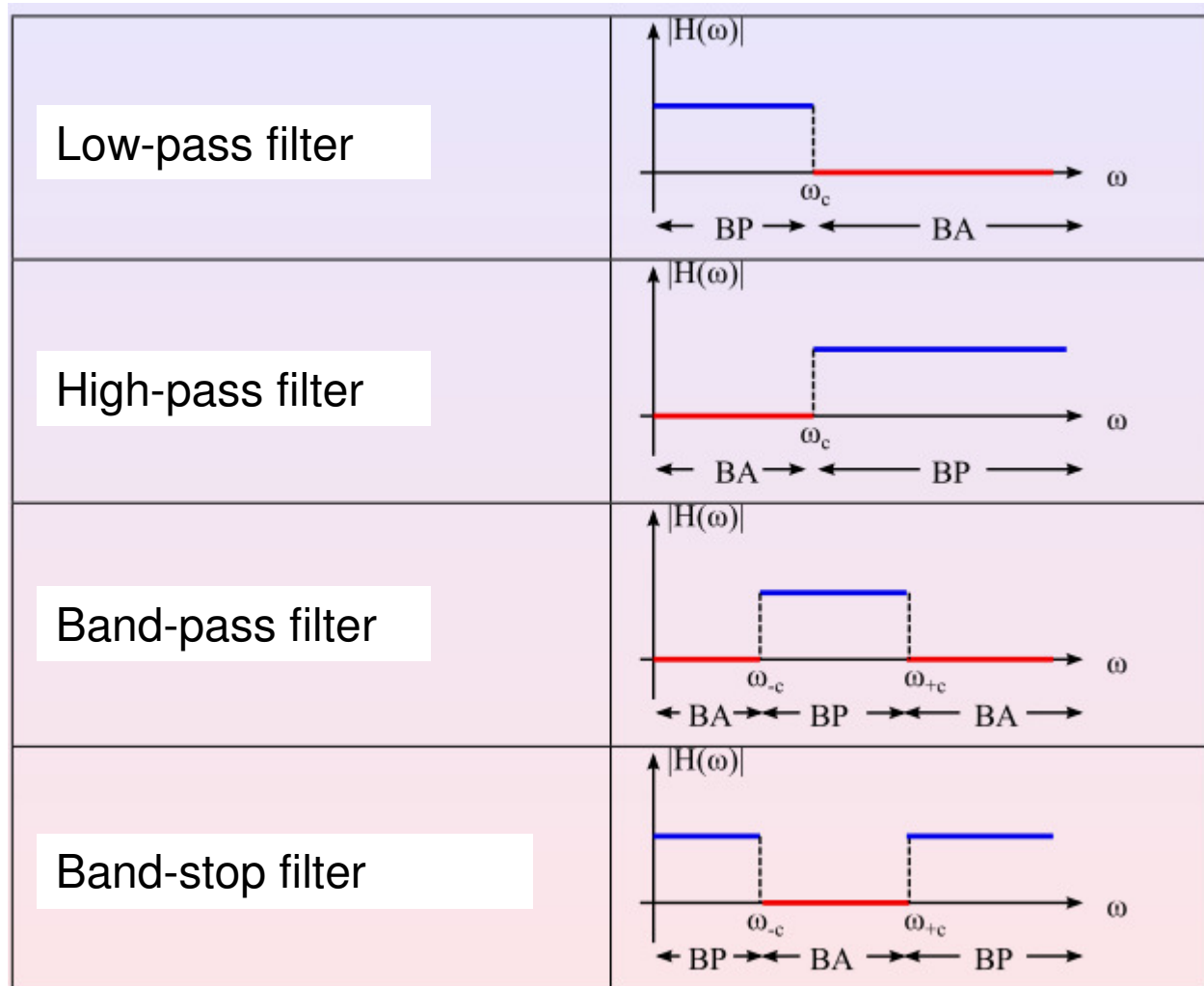

PB: Pass band, AB: Attenuation band, ω_c : Cut frequency




Impulse response of ideal filters

- Ideal filters can not be implemented in practice
- The real filter have to be approached to the ideal filter response using different methods
- The approached filters have not a constant response in the PB and are not entirely zero in the AB
- There exist a transition band between PB and AB
- The **order of the filter** coincides with the number of poles of $H(s)$
- The higher the order of the filter the close is his behavior as an ideal filter
- To design filters, layout templates with the tolerance margins are used




Layout templates for filter design

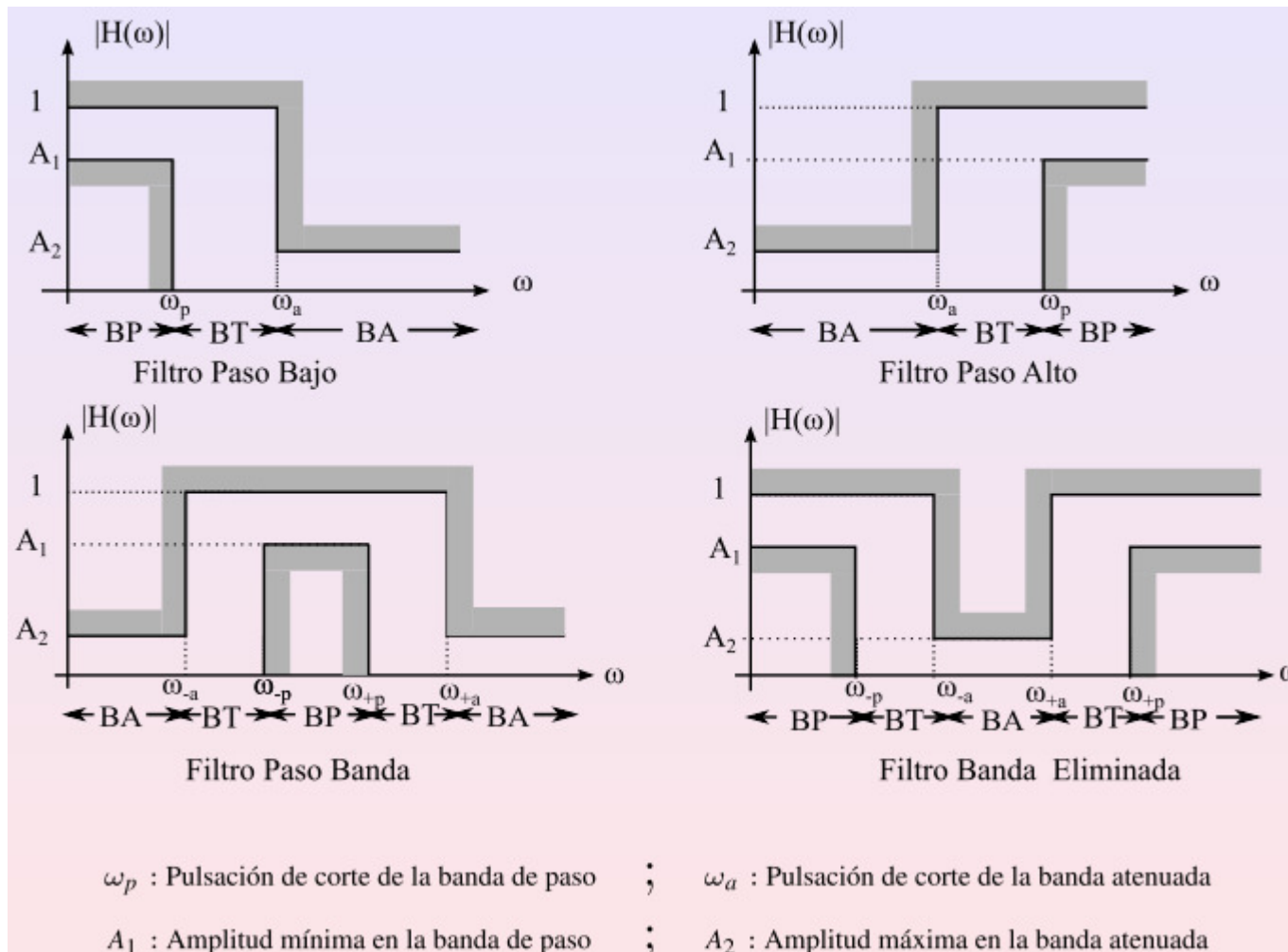





Examples of real filters

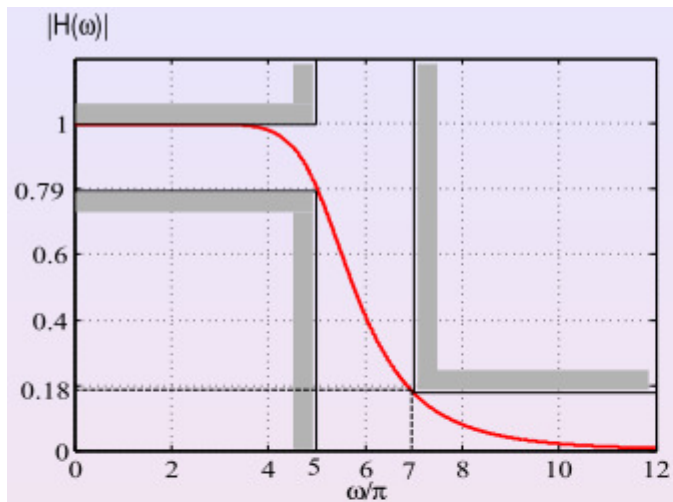

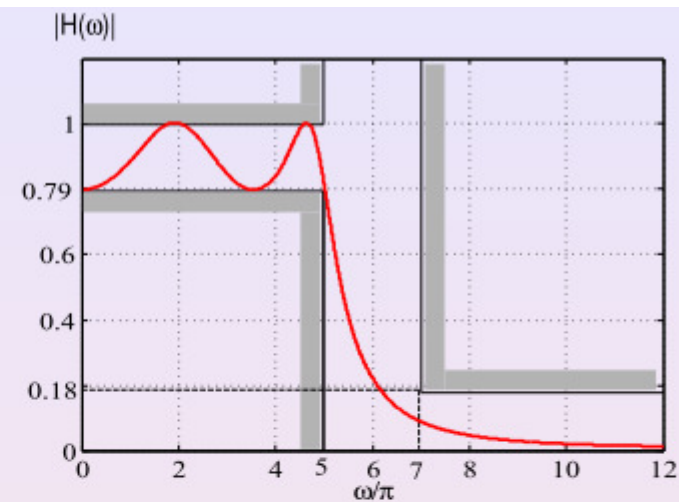
Filtro paso bajo de Butterworth de orden 6



Filtro paso bajo de Chebyshev de orden 4

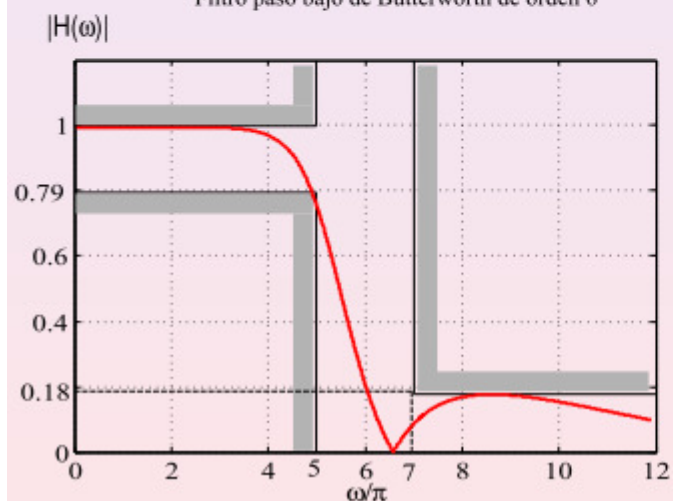

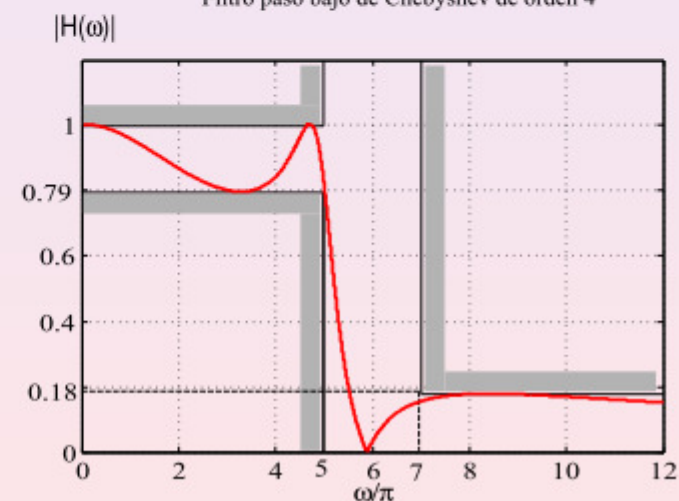Filtro paso bajo de Chebyshev inverso de orden 4



Filtro paso bajo Elíptico de orden 3



1st order low-pass filter

- Transfer function


$$H(s) = k \frac{\omega_c}{s + \omega_c}$$

where ω_c is the **cut frequency**, at this frequency the **attenuation** of the signal is **3dB**:

$$-20 \log_{10} \frac{|H(\omega)|_{\omega=\omega_c}}{|H(\omega)|_{\max}} = 3 \Rightarrow \frac{|H(\omega)|_{\omega=\omega_c}}{|H(\omega)|_{\max}} = \frac{1}{\sqrt{2}}$$

$$\Leftrightarrow |H(\omega)|_{\omega=\omega_c} = |H(\omega)|_{\max} 10^{\frac{-3}{20}}$$


$$|H(\omega)| = k \frac{\omega_c}{\sqrt{\omega^2 + \omega_c^2}}$$

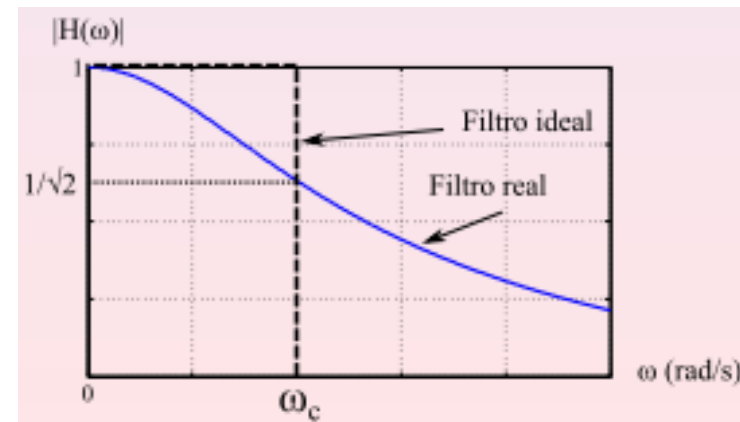



Examples 1st order low-pass filter

- Low-pass RC:

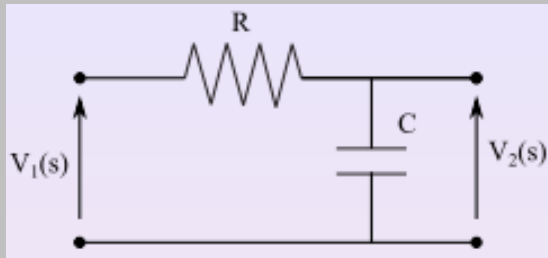


$$Z_C(\omega \rightarrow \infty) \rightarrow 0 \Rightarrow V_2 \rightarrow 0$$

$$Z_C(\omega = 0) \rightarrow \infty \Rightarrow V_2 \rightarrow V_1$$

$$H(\omega) = \frac{\frac{1}{RC}}{j\omega + \frac{1}{RC}},$$

$$\omega_c = \frac{1}{RC}$$

- Low-pass RL

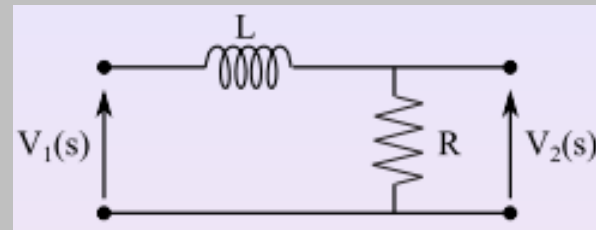

$$Z_L(\omega \rightarrow \infty) \rightarrow \infty \Rightarrow V_2 \rightarrow 0$$

$$Z_L(\omega = 0) = 0 \Rightarrow V_1 = V_2$$

$$H(\omega) = \frac{\frac{R}{L}}{j\omega + \frac{R}{L}},$$

$$\omega_c = \frac{R}{L}$$



1st order high-pass filter

- Transfer function


$$H(s) = k \frac{s}{s + \omega_c}$$

where ω_c is the **cut frequency**, at this frequency the **attenuation** of the signal is **3dB**:

$$-20 \log_{10} \frac{|H(\omega)|_{\omega=\omega_c}}{|H(\omega)|_{\max}} = 3 \Rightarrow \frac{|H(\omega)|_{\omega=\omega_c}}{|H(\omega)|_{\max}} = \frac{1}{\sqrt{2}}$$

$$|H(\omega)|_{\omega=\omega_c} = |H(\omega)|_{\max} 10^{\frac{-3}{20}}$$


$$|H(\omega)| = k \frac{\omega}{\sqrt{\omega^2 + \omega_c^2}}$$

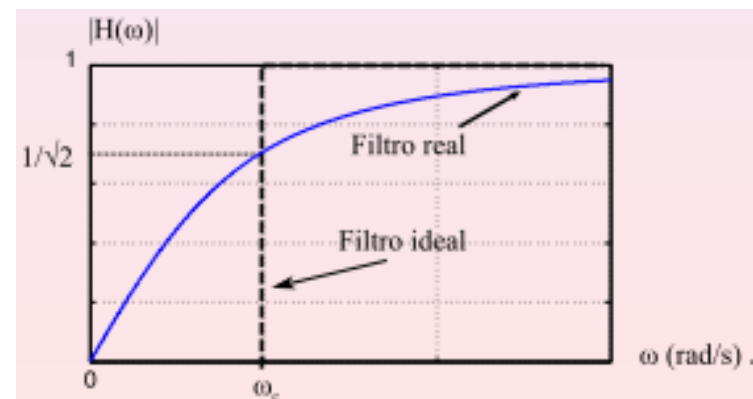



Examples 1st order high-pass filter

- High-pass RC:

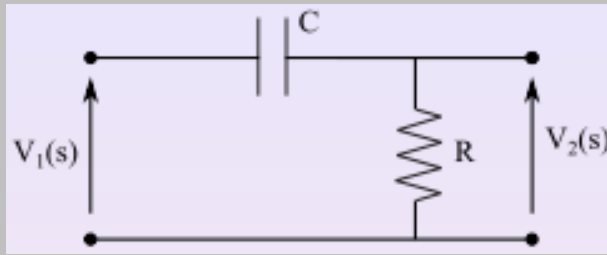


$$Z_C(\omega = 0) \rightarrow \infty \Rightarrow V_2 \rightarrow 0$$

$$Z_C(\omega \rightarrow \infty) = 0 \Rightarrow V_2 = V_1$$

$$H(\omega) = \frac{j\omega}{j\omega + \frac{1}{RC}},$$

$$\omega_c = \frac{1}{RC}$$

- High-pass RL

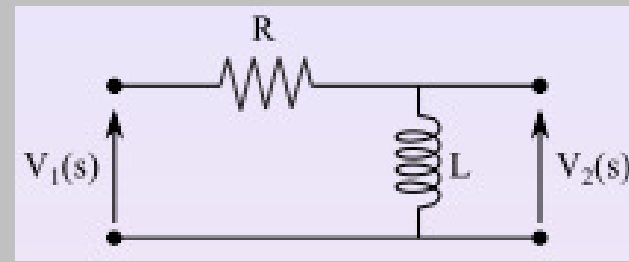

$$Z_L(\omega = 0) = 0 \Rightarrow V_2 = 0$$

$$Z_L(\omega \rightarrow \infty) \rightarrow \infty \Rightarrow V_2 \rightarrow V_1$$

$$H(\omega) = \frac{j\omega}{j\omega + \frac{R}{L}},$$

$$\omega_c = \frac{R}{L}$$



2st order passive filters

- Transfer function:

$$H(s) = k \frac{N_2(s)}{s^2 + a_1s + a_2} = k \frac{N_2(s)}{s^2 + 2\xi\omega_0s + \omega_0^2} = k \frac{N_2(s)}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

- $N_2(s)$: Polynomial of order ≤ 2
- ξ : **Damping coefficient**
- ω_0 : **Characteristic frequency** of the filter
- $Q=1/(2\xi)$: **Quality factor** of the circuit
- *For band-pass and band stop filters:*

$B = \omega_0 / Q$: **Band width** of the circuit

$$k = \left| H(\omega) \right|_{\max} (= H_0)$$



2nd order passive filters

- With 2nd order filter the four type of filters can be obtained (with 1st order only two)
- The poles of $H(s)$ are:

$$s_{p1,2} = -\omega_0 \left(\xi \pm j\sqrt{1-\xi^2} \right) = -\frac{\omega_0}{2Q} \left(1 \pm j\sqrt{4Q^2 - 1} \right)$$

- Depending on the value of ξ (or Q) we distinguish the following two poles:
 - Real and different ($\xi > 1$ or $Q < 1/2$)
 - Real and equal ($\xi = 1$ or $Q = 1/2$)
 - Complex conjugated ($\xi < 1$ or $Q > 1/2$)
- Depending on $N_2(s)$ we have the following special cases:



2nd order filters

- Low-pass filter
- High-pass filter
- Band-pass filter
- Band-stop filter

$$H(s) = k \cdot \frac{\omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

$$H(s) = k \cdot \frac{s^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

$$H(s) = k \cdot \frac{\frac{\omega_0}{Q}s}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$




$$H(s) = k \cdot \frac{s^2 + \omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$



2nd order low-pass filter

$$H(s) = k \frac{\omega_0^2}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$

Example:

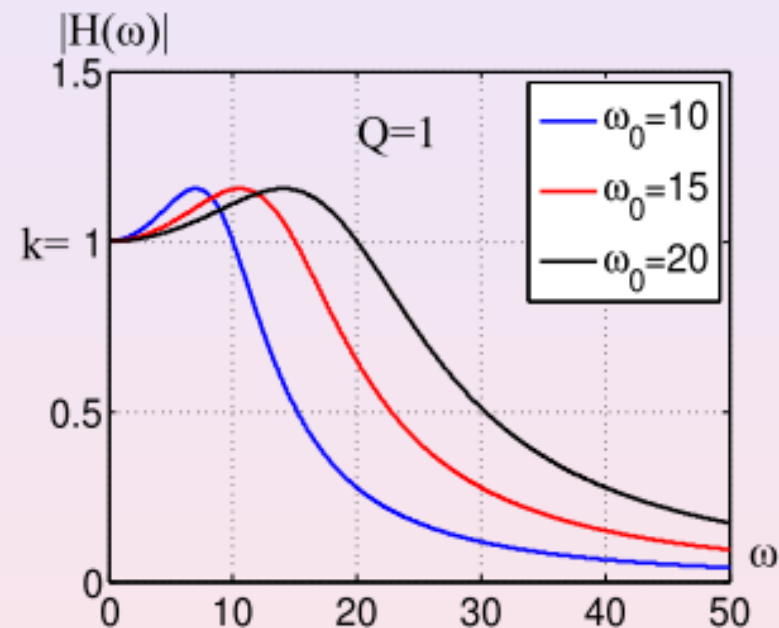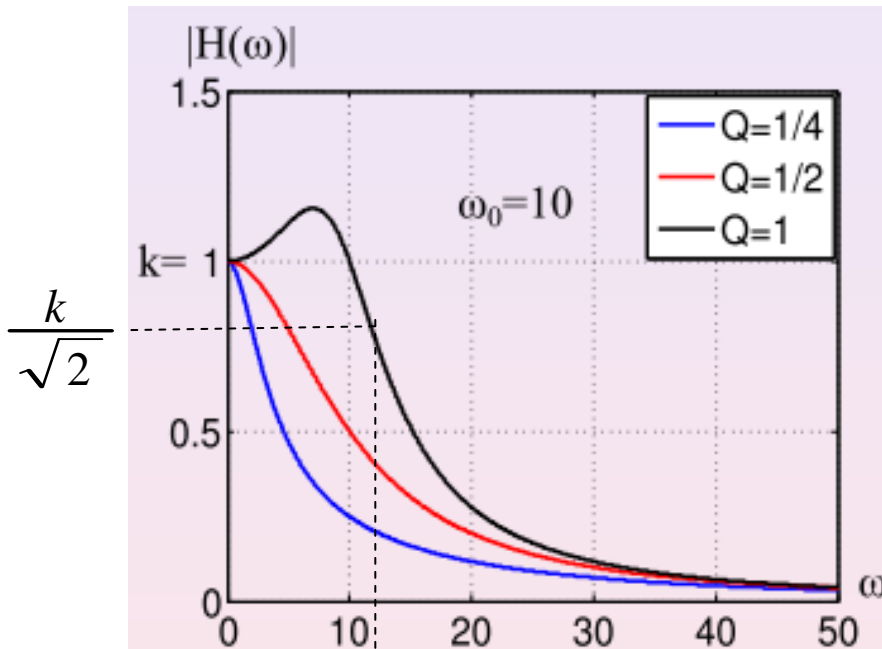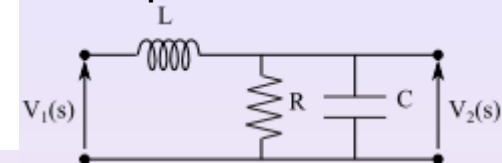




Cut frequency: ω_C



2nd order high-pass filter

$$H(s) = k \frac{s^2}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$

Example:

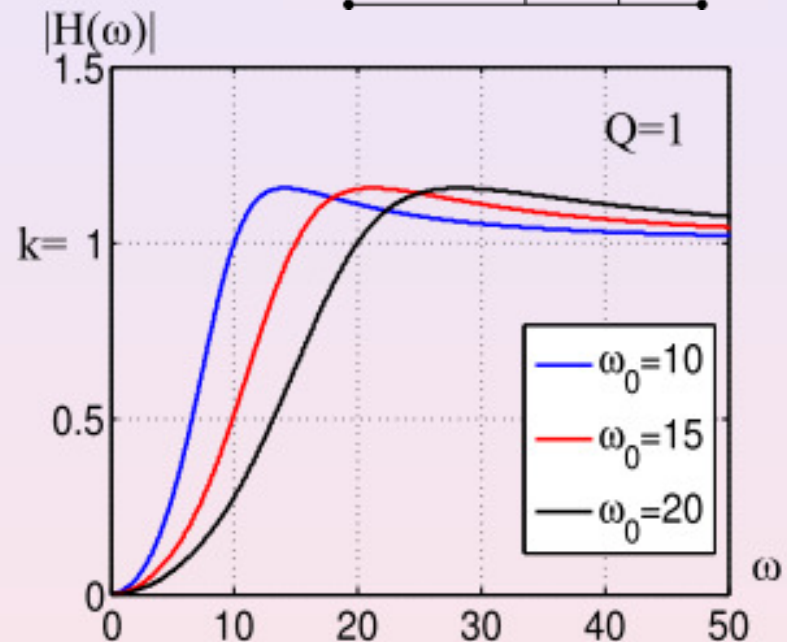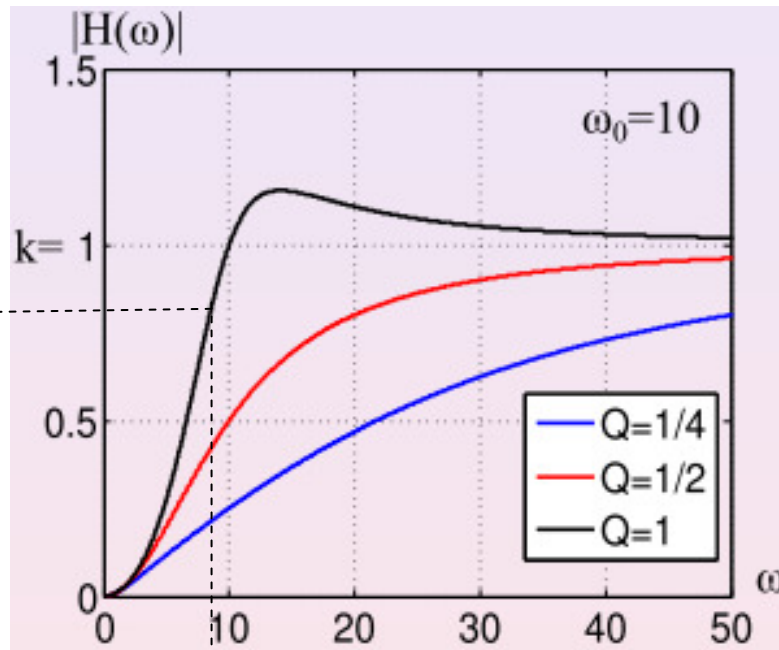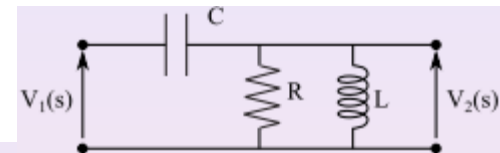




Cut frequency: ω_C



2nd order band-pass filter

$$H(s) = k \frac{\frac{\omega_0}{Q} s}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2} = k \frac{Bs}{s^2 + Bs + \omega_0^2}$$

Example:

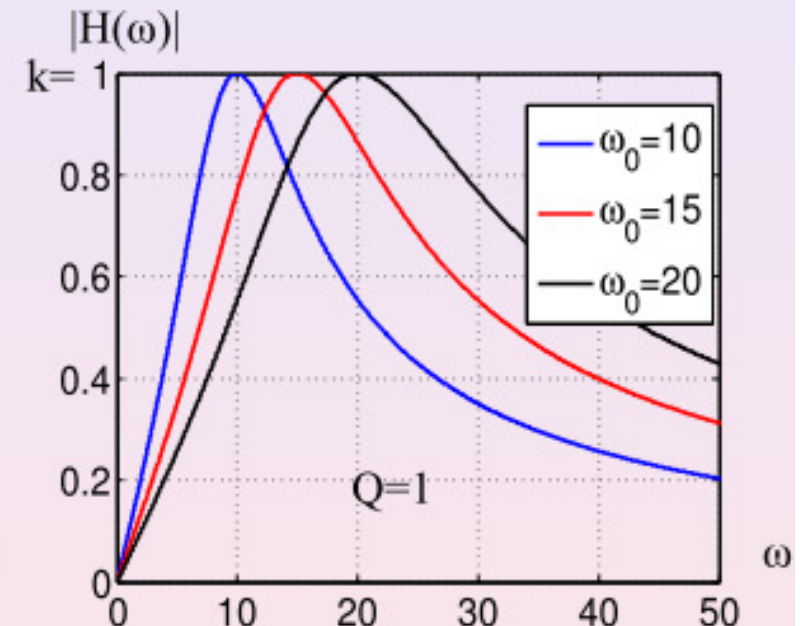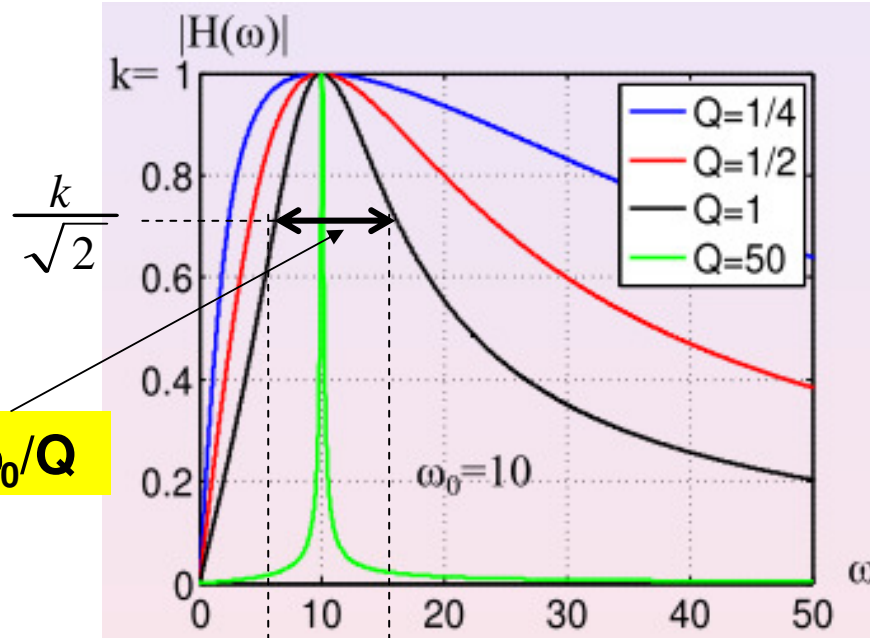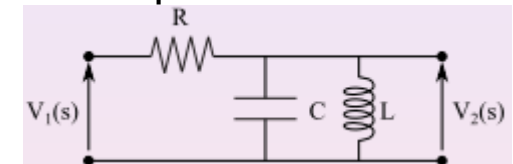

$B = \omega_0 / Q$

Cut frequencies: $\omega_{C,1}$

$\omega_{C,2}$



$B = \omega_{C,2} - \omega_{C,1}$




2nd order Band-stop filter

$$H(s) = k \frac{s^2 + \omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

Example:

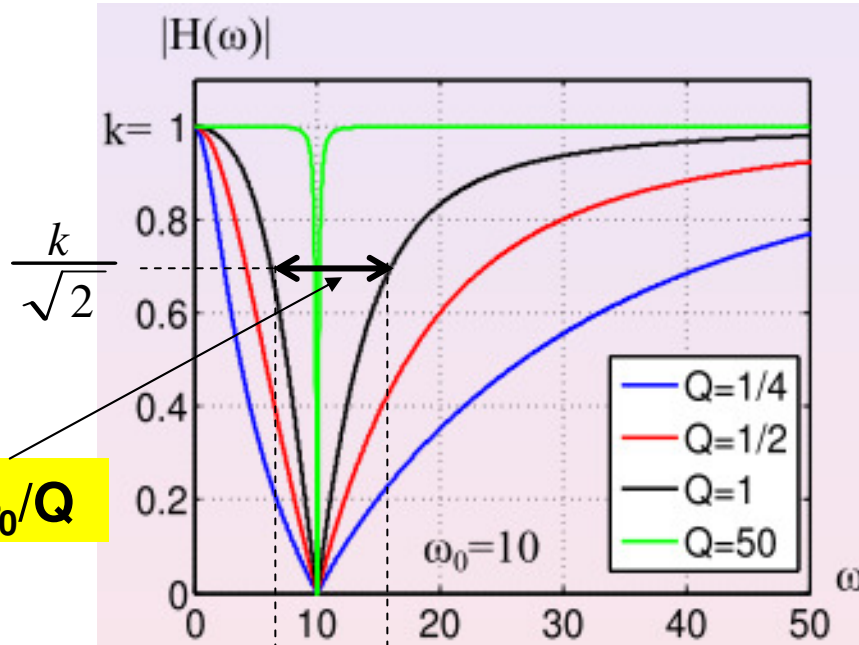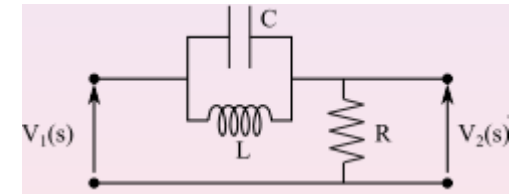

$B = \omega_0 / Q$

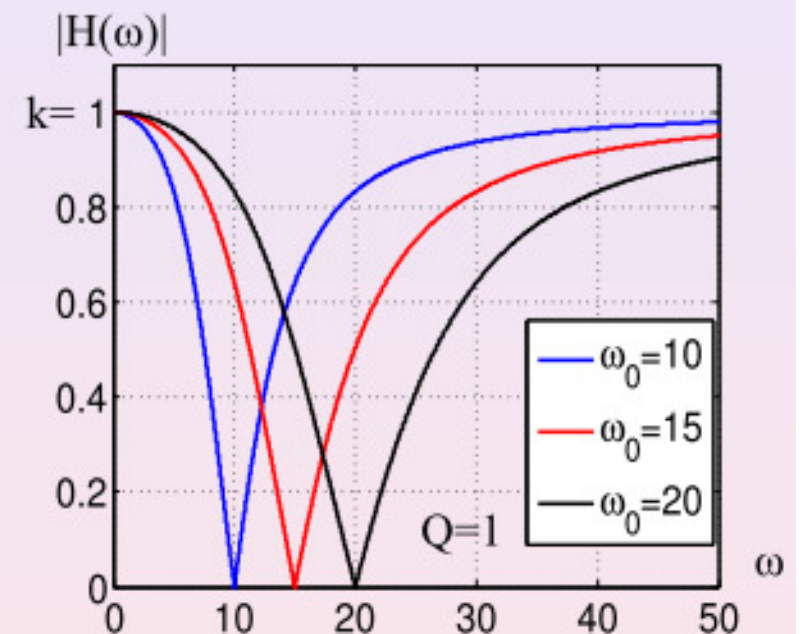

Cut frequencies: $\omega_{C,1}$

$\omega_{C,2}$

$B = \omega_{C,2} - \omega_{C,1}$



Examples 2nd order filters

	$H(s) = \frac{\frac{1}{LC}}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$ F.P. Bajo
	$H(s) = \frac{s^2}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$ F.P. Alto
	$H(s) = \frac{\frac{1}{RC}s}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$ F.P. Banda
	$H(s) = \frac{s^2 + \frac{1}{LC}}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$ F.Banda Eliminada

Siendo: $\omega_0 = \frac{1}{\sqrt{LC}}$; $Q = R\omega_0 C = \frac{R}{\omega_0 L} = R\sqrt{\frac{C}{L}}$