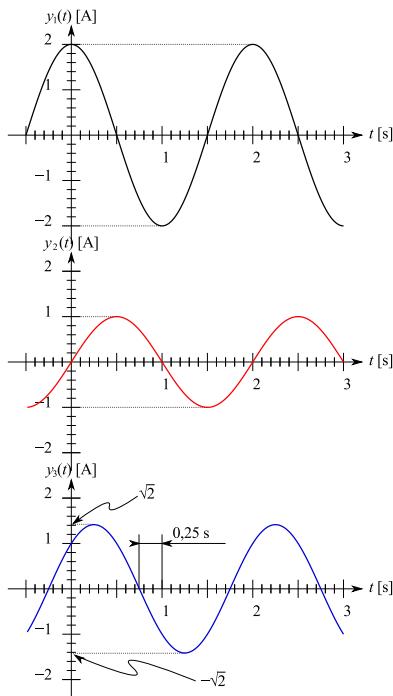


EXERCISES MODULE 2: AC CIRCUITS SINUSOIDAL STEADY-STATE ANALYSIS

October 25, 2016

PROBLEM 2.1



Given the signals in Figure 1, compute:

- a) $x_1(t) = y_1(t) + y_2(t)$
- b) $x_2(t) = y_1(t) + y_3(t)$
- c) $x_3(t) = y_1(t) + y_2(t) - y_3(t)$

Figure 1

Result

1. $x_1(t) = \sqrt{5} \cos(\pi t - 0.463) = \sqrt{5} \sin(\pi t + 1.107)$
2. $x_2(t) = \sqrt{10} \cos(\pi t - 0.3217) = \sqrt{10} \sin(\pi t + 1.249)$
3. $x_3(t) = \cos(\pi t) = \sin\left(\pi t + \frac{\pi}{2}\right)$

PROBLEM 2.2

For the circuit in Figure 2, the signals $e(t)$ and $i(t)$ are shown in the graphs of Figure 3. Obtain the value of R and C .

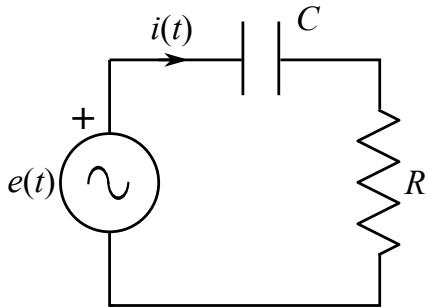


Figure 2

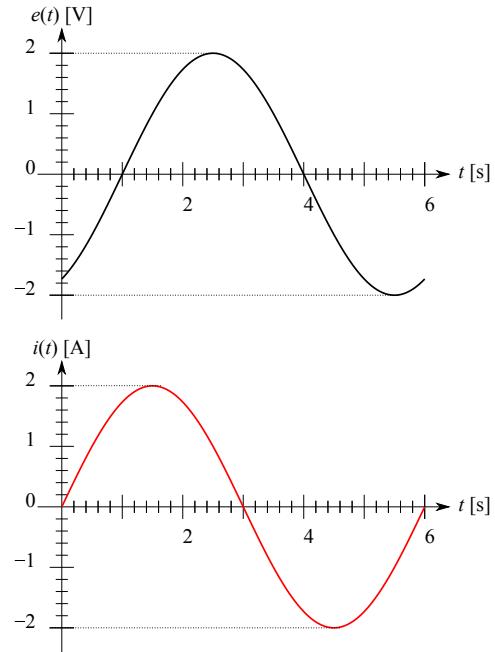


Figure 3

Result

$$R = \frac{1}{2} \Omega; C = \frac{2\sqrt{3}}{\pi} = 1.103 \text{ F}$$

PROBLEM 2.3

For the circuit in Figure 4, currents $i_1(t)$ and $i_2(t)$ are shown in the graphs of Figure 5. If the power delivered by the source $e(t)$ is of 2 W, find the value of R_1 , R_2 and L .

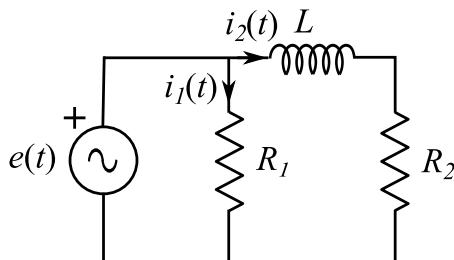


Figure 4

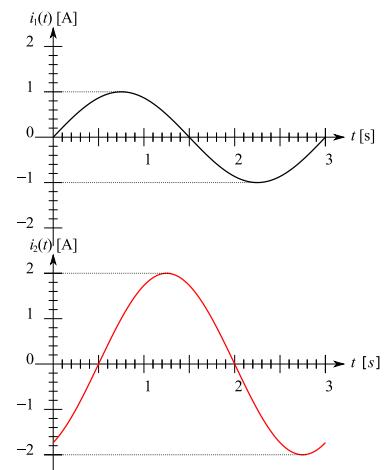


Figure 5

Result

$$R_1 = 2 \Omega; \quad R_2 = \frac{1}{2} \Omega; \quad L = \frac{3\sqrt{3}}{4\pi} = 0.413 \text{ H}$$

PROBLEM 2.4

For the circuit in Figure 6, the graphs of Figure 7 represent the source $e(t)$ and the current $i_1(t)$. If $R_2 = 1 \Omega$:

- a) Compute the value of R_1 and C .
- b) Determine the power of the source $e(t)$.

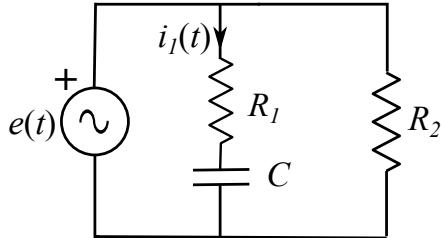


Figure 6

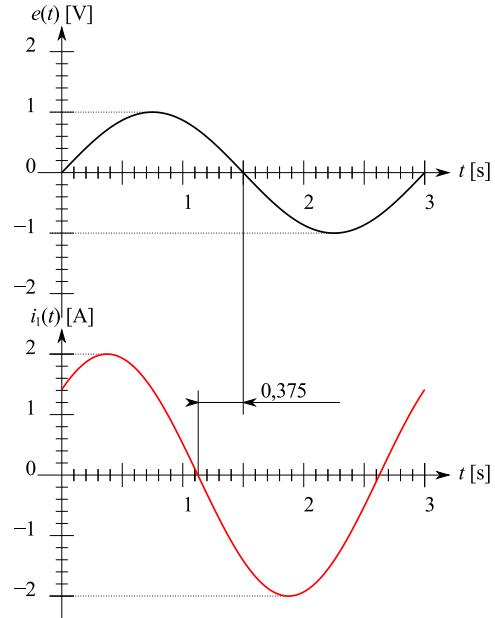


Figure 7

Result

$$\text{a)} \quad \begin{cases} R_1 = \frac{1}{2\sqrt{2}} = 0.354 \Omega \\ C = \frac{3\sqrt{2}}{\pi} = 1.35 \text{ F} \end{cases}$$

$$\text{b)} \quad P_{e(t)} = 1.207 \text{ W}$$

PROBLEM 2.5

For the circuit in Figure 8, when $e(t)$ is substituted by the signal $e_1(t)$ shown in Figure 9 the current $i_C(t)$ is equal to 1 A. If $R = 1 \Omega$, determine the difference of phase between the source and the current $i(t)$ when $e(t)$ follows the signal $e_2(t)$ shown in Figure 9.

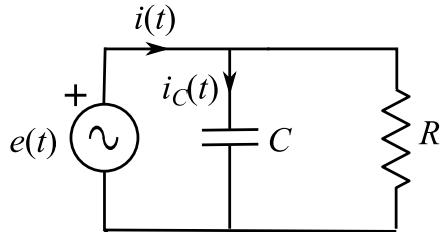


Figure 8

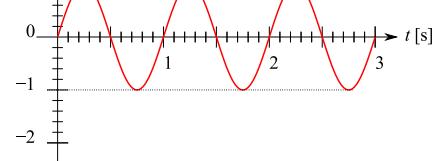
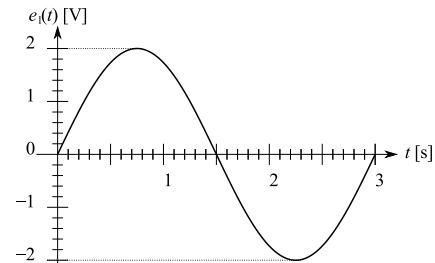



Figure 9

Result

$$\varphi_{i(t)} - \varphi_{e(t)} = 0.983 \text{ rad}$$

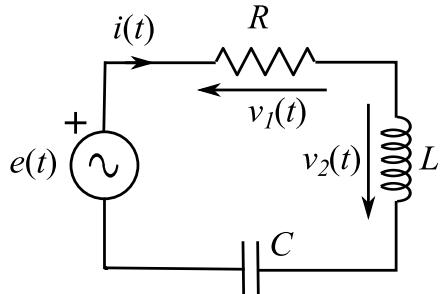PROBLEM 2.6

For the circuit in Figure 10 obtain the time-domain expressions for $i(t)$, $v_1(t)$ and $v_2(t)$.



Data:

$$e(t) = \sqrt{2} \cos\left(10^6 t - \frac{\pi}{4}\right) \text{ V}; \quad L = 2 \mu\text{H}$$

$$C = 1 \mu\text{F}; \quad R = 1 \Omega$$


Figure 10

Result

$$\begin{cases} i(t) = \cos\left(10^6 t - \frac{\pi}{2}\right) \text{ A} \\ v_1(t) = \cos\left(10^6 t - \frac{\pi}{2}\right) \text{ V} \\ v_2(t) = 2 \cos\left(10^6 t + \pi\right) \text{ V} \end{cases}$$

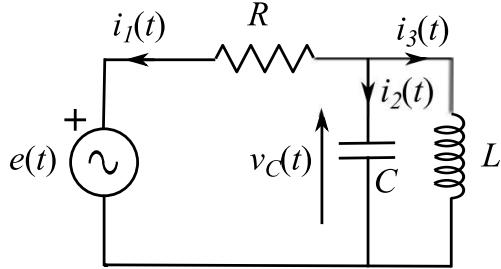PROBLEM 2.7

For the circuit in Figure 11 obtain the time-domain expressions $v_C(t)$, $i_1(t)$, $i_2(t)$ and $i_3(t)$ and represent the phasor diagram of the circuit.



Data:


$$e(t) = 2 \cos\left(10^6 t + \frac{\pi}{2}\right) \text{ V}; \quad L = 2 \mu\text{H}$$

$$C = 1 \mu\text{F}; \quad R = 2 \Omega$$

Figure 11

Result


$$\begin{cases} v_C(t) = \sqrt{2} \cos\left(10^6 t + \frac{\pi}{4}\right) \text{ V} \\ i_1(t) = \frac{\sqrt{2}}{2} \cos\left(10^6 t - \frac{\pi}{4}\right) \text{ A} \\ i_2(t) = \sqrt{2} \cos\left(10^6 t + \frac{3\pi}{4}\right) \text{ A} \\ i_3(t) = \frac{\sqrt{2}}{2} \cos\left(10^6 t - \frac{\pi}{4}\right) \text{ A} \end{cases}$$

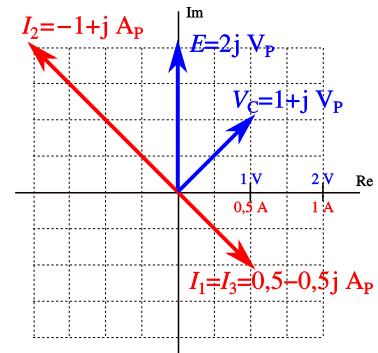

PROBLEM 2.8

For the circuit in Figure 12 obtain;

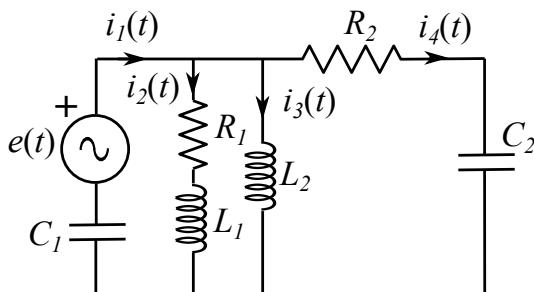- a) The time-domain expressions for $i_1(t)$, $i_2(t)$, $i_3(t)$ and $i_4(t)$.
- b) Power of the source $e(t)$.
- c) Power absorbed by all the passive components of the circuit.
- d) Power balance.



Data:

$$e(t) = \sqrt{2} \cos\left(10^6 t + \frac{\pi}{4}\right) \text{ V}; \quad L_1 = 1 \mu\text{H}$$

$$L_2 = 1 \mu\text{H}; \quad C_1 = 2 \mu\text{F}$$

$$C_2 = 1 \mu\text{F}, \quad R_1 = R_2 = 1 \Omega$$

Figure 12


Result

$$\text{a) } \begin{cases} i_1(t) = 2\sqrt{2} \cos\left(10^6 t + \frac{\pi}{4}\right) \text{ A} \\ i_2(t) = \sqrt{2} \cos\left(10^6 t + \frac{\pi}{4}\right) \text{ A} \\ i_3(t) = 2 \cos(10^6 t) \text{ A} \\ i_4(t) = \sqrt{2} \cos\left(10^6 t + \frac{3\pi}{4}\right) \text{ A} \end{cases}$$

- b) $P_{e(t)} = 2 \text{ W.}$
- c) $P_{R_1} = P_{R_2} = 1 \text{ W.}$
- d) $P_{e(t)} = P_{R_1} + P_{R_2} = 2 \text{ W.}$

PROBLEM 2.9

In the circuit of Figure 13 obtain the modulus of the impedance of the inductor $|Z_L|$.

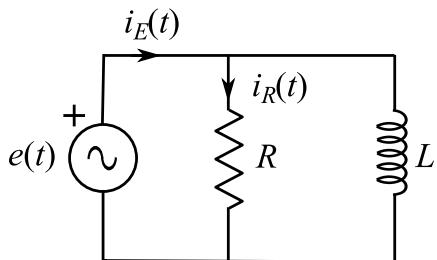

Data:

$$\begin{aligned} |I_R| &= 1 \text{ A} \\ |I_E| &= \sqrt{2} \text{ A} \\ R &= 1 \Omega \end{aligned}$$

Figure 13


Result

$$|Z_L| = 1 \Omega$$

PROBLEM 2.10

In the circuit of Figure 14 it is known that the source is delivering a power $P_{e(t)} = 2 \text{ W}$, and that the current $i_L(t)$ lags the voltage $e(t)$. Determine:

- Power of R_1 .
- Value of R_2 .
- Value of the modulus of the impedance of the capacitor $|Z_C|$.

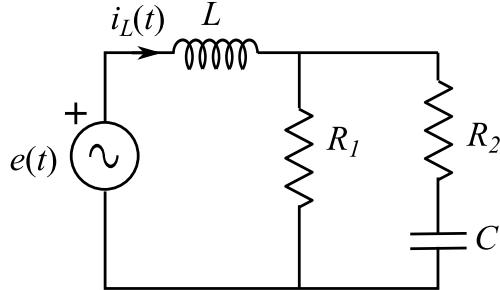

Data:

$$\begin{aligned} |E| &= 2 \text{ V} \\ |I_L| &= 2 \text{ A}_{ef} \\ R_1 &= 2 \Omega \\ |Z_L| &= 1 \Omega \end{aligned}$$

Figure 14

Result

a) $P_{R_1} = 1 \text{ W}$; b) $R_2 = \frac{2}{5} \Omega$; c) $|Z_C| = \frac{4}{5} \Omega$.

PROBLEM 2.11

For the circuit in Figure 15, voltage $v_{CD}(t)$ and current $i_R(t)$ are shown in Figure 16. Determine:

- Values of R and C .
- If $|I_E| = 1 \text{ A}_{ef}$, the value of L

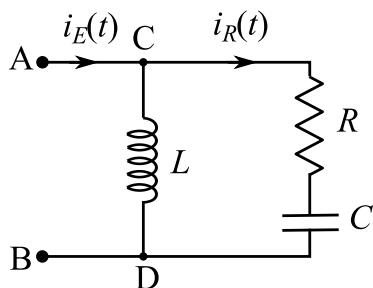


Figure 15

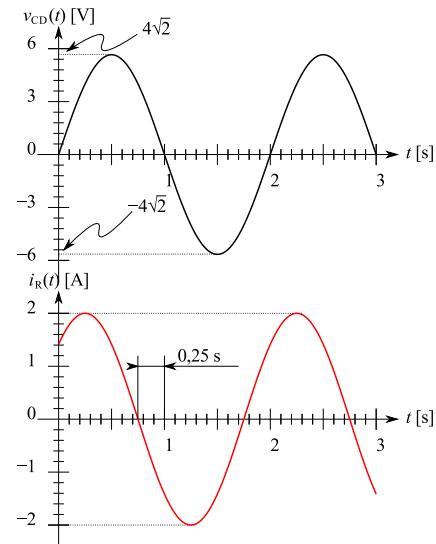


Figure 16


Result

a) $R = 2 \Omega; C = \frac{1}{2\pi} = 0.159 \text{ F}.$

b) $L = \frac{4}{\pi} = 1.273 \text{ H}.$

PROBLEM 2.12

For the circuit in Figure 17 determine the value of $|Z_C|$.

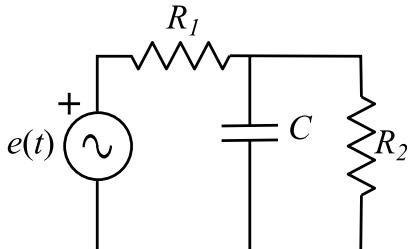

Data:

$$P_{R_2} = 9 \text{ W}$$

$$P_{e(t)} = 34 \text{ W}$$

$$R_1 = R_2 = 2 \Omega$$

Figure 17

Result

$$|Z_C| = \frac{3}{2} \Omega.$$

PROBLEM 2.13

For the circuit in Figure 18, obtain the expressions for V_1 , V_2 and V_3 as a function of I_1 , I_2 , ωL_1 , ωL_2 , ωM_{12} , ωM_{13} and ωM_{23} .

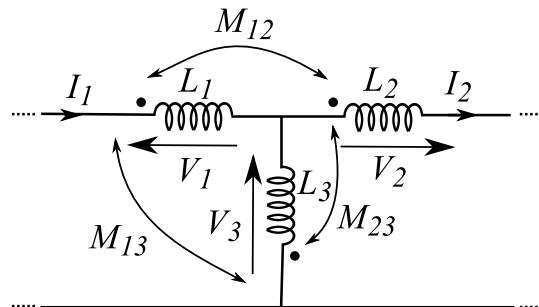


Figure 18

Result

$$\begin{cases} V_1 = j\omega(L_1 - M_{13}) \cdot I_1 + j\omega(M_{12} + M_{13}) \cdot I_2 \\ V_2 = j\omega(M_{23} - M_{12}) \cdot I_1 - j\omega(L_2 + M_{23}) \cdot I_2 \\ V_3 = j\omega(L_3 - M_{13}) \cdot I_1 - j\omega(L_3 + M_{23}) \cdot I_2 \end{cases}$$

PROBLEM 2.14

For the circuit in Figure 19 obtain the time-domain expressions for $v_1(t)$, $v_2(t)$, and $v_3(t)$.

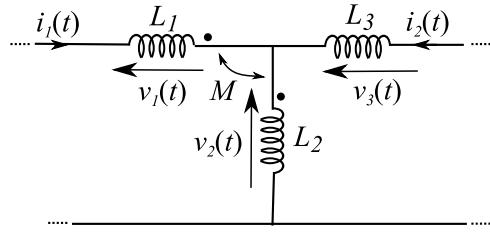


Figure 19

$$\text{Data : } i_1(t) = \sin(\omega t) \text{ A} \quad ; \quad i_2(t) = \sin\left(\omega t + \frac{\pi}{2}\right) \text{ A} \\ \omega L_1 = \omega L_2 = \omega L_3 = 2 \Omega \quad ; \quad k = \frac{1}{2}$$

Result

$$\begin{cases} v_1(t) = \sqrt{2} \cdot \sin\left(\omega t + \frac{\pi}{4}\right) \text{ V} \\ v_2(t) = \sqrt{5} \cdot \sin(\omega t + 2.678) \text{ V} \\ v_3(t) = 2 \cdot \sin(\omega t) \text{ V} \end{cases}$$

PROBLEM 2.15

For the circuit in Figure 20, compute the time-domain expression of the electric potential difference between terminals A and B .

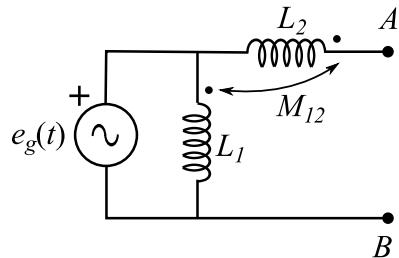


Figure 20

$$\text{Data: } e_g(t) = 2 \cdot \cos(\omega t) \text{ V} \quad ; \quad \omega L_1 = \omega L_2 = 2 \Omega \quad ; \quad k = 0.5$$

Result

$$v_{AB}(t) = 3 \cdot \cos(\omega t) \text{ V}$$

PROBLEM 2.16

For the circuit in Figure 21, obtain the relation $Z_{eq} = \frac{E}{I_1}$

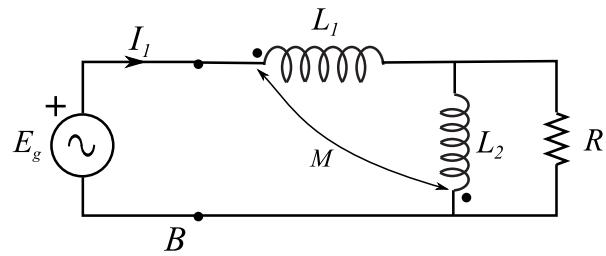


Figure 21

Data : $e_g(t) = E_0 \sin(10^3 t) \text{ V}; \quad R = 2 \Omega$
 $L_1 = 1 \text{ mH}; \quad L_2 = 2 \text{ mH}; \quad k = \frac{1}{\sqrt{2}}$

Result
 $Z_{eq} = \frac{1 + 3j}{4} \Omega$