

EXERCISES MODULE 3: SOURCES AND METHODS OF ANALYSIS. THEVENIN'S AND NORTON'S EQUIVALENT SOURCES.

November 22, 2016

PROBLEM 3.1

Given the circuit of Figure 1:

- a) Determine the equations that allow to solve the circuit using the mesh analysis method.
- b) Determine the equations that allow to solve the circuit using the nodal analysis method.

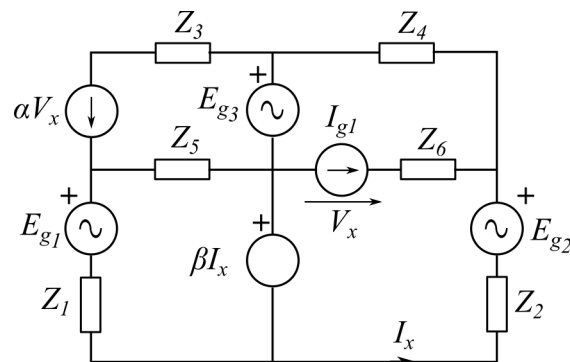


Figure 1

PROBLEM 3.2

Given the circuit in Figure 2:

- a) Determine the system of equations that allows to solve the circuit using the mesh analysis method.
- b) Determine the system of equations that allows to solve the circuit using the nodal analysis method.
- c) Solve the circuit using the equations obtained in a), and determine the potential of points A, B and C (V_A, V_B, V_C).

- d) Solve the circuit using the equations obtained in b), and determine the potential of points A, B and C (V_A, V_B, V_C).
- e) Do these potentials coincide independently of the method of analysis used to compute them?

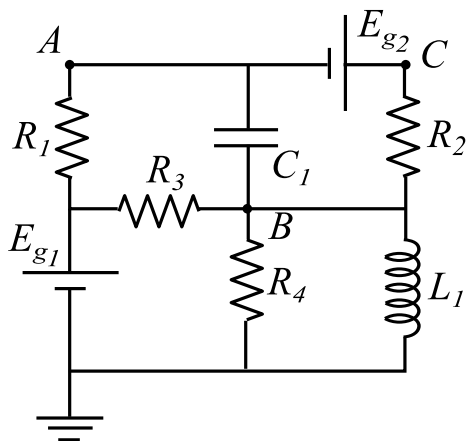


Figure 2

Data:

$$E_{g1} = 1 \text{ V}; \quad E_{g2} = 1 \text{ V}$$

$$R_1 = 1 \text{ } \Omega; \quad R_2 = 1 \text{ } \Omega$$

$$R_3 = 1 \text{ } \Omega; \quad R_4 = 2 \text{ } \Omega$$

$$C_1 = 1 \text{ } \mu\text{F}; \quad L_1 = 1 \text{ mF}$$

Result

$$V_A = 0 \text{ V}, \quad V_B = 0 \text{ V}, \quad V_C = 1 \text{ V}$$

PROBLEM 3.3

Given the circuit in Figure 3:

- Determine the system of equations that allows to solve the circuit using the mesh analysis method.
- Determine the system of equations that allows to solve the circuit using the nodal analysis method.
- Solve the circuit using the equations obtained in a), and determine the difference of potentials between points A and B, V_{AB} .
- Solve the circuit using the equations obtained in b), and determine the difference of potentials between points A and B, V_{AB} .
- Do these potentials coincide independently of the method of analysis used to compute them?

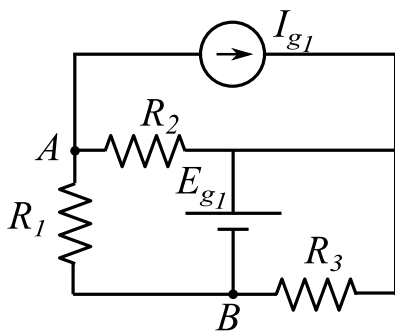


Figure 3

Data:

$$E_{g1} = 3 \text{ V}; \quad I_{g1} = 6 \text{ A}$$

$$R_1 = 1 \ \Omega; \quad R_2 = 2 \ \Omega$$

$$R_3 = 3 \ \Omega;$$

Result

$$V_{AB} = -3 \text{ V}$$

PROBLEM 3.4

Given the circuit in Figure 4:

- Determine the system of equations that allows to solve the circuit using the mesh analysis method.
- Determine the system of equations that allows to solve the circuit using the nodal analysis method.
- Solve the circuit using the equations obtained in a), and determine the difference of potentials between points B and A, V_{BA} .
- Solve the circuit using the equations obtained in b), and determine the difference of potentials between points B and A, V_{BA} .
- Do these difference of potentials coincide independently of the method of analysis used to compute them?

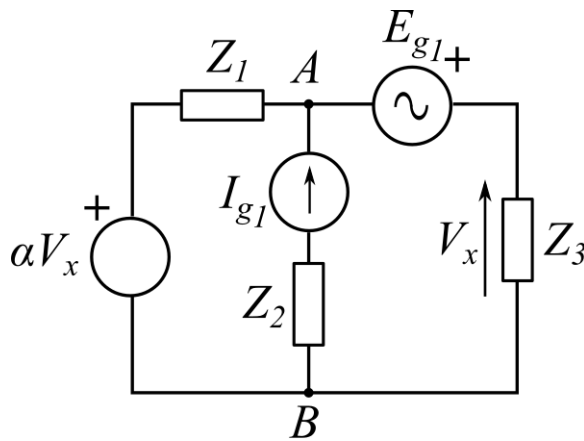


Figure 4

Data:

$$\begin{aligned} E_{g1} &= 2 + 2j \text{ V}; & I_{g1} &= 4j \text{ A} \\ Z_1 &= j \Omega; & Z_2 &= 1 + j \Omega \\ Z_3 &= 2 - j \Omega; & \alpha &= 2 \end{aligned}$$

Result

$$V_{BA} = 3j \text{ V}$$

PROBLEM 3.5

Given the circuit in Figure 5:

- Determine the system of equations that allows to solve the circuit using the mesh analysis method.
- Determine the system of equations that allows to solve the circuit using the nodal analysis method.
- Solve the circuit using the equations obtained in a), and determine the difference of potentials between points C and D, V_{CD} .
- Solve the circuit using the equations obtained in b), and determine the difference of potentials between points C and D, V_{CD} .
- Do these difference of potentials coincide independently of the method of analysis used to compute them?

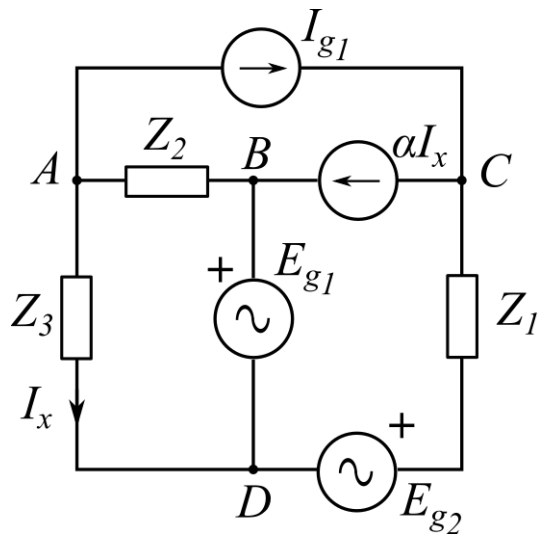


Figure 5

Data:

$$\begin{aligned}
 E_{g1} &= 2 + j \text{ V}; & E_{g2} &= 1 - 3j \text{ V} \\
 Z_1 &= -j \Omega; & Z_2 &= 1 \Omega \\
 Z_3 &= 1 \Omega; & I_{g1} &= j \text{ A} \\
 \alpha &= 1;
 \end{aligned}$$

Result

$$V_{CD} = 2 - 2j \text{ V}$$

PROBLEM 3.6

Given the circuit in Figure 6:

- Determine the system of equations that allows to solve the circuit using the mesh analysis method.
- Determine the system of equations that allows to solve the circuit using the nodal analysis method.
- Solve the circuit using the equations obtained in a), and determine the current $i_x(t)$.
- Solve the circuit using the equations obtained in b), and determine the current $i_x(t)$.
- Do the expressions for $i_x(t)$ coincide independently of the method of analysis used to obtain them?

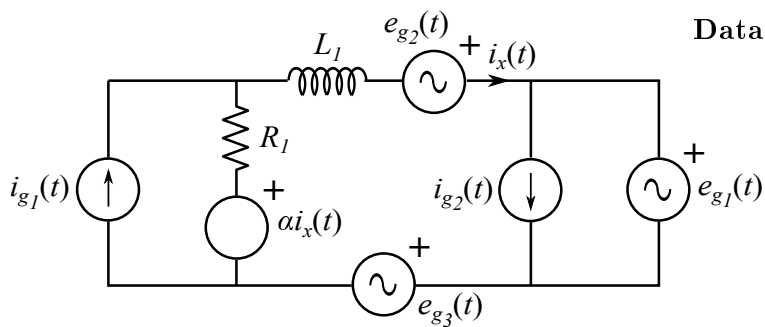


Figure 6

Data:

$$e_{g1}(t) = \cos\left(t - \frac{\pi}{2}\right) \text{ V}$$

$$e_{g2}(t) = 2 \cos(t) \text{ V}$$

$$e_{g3}(t) = \cos\left(t + \frac{\pi}{2}\right) \text{ V}$$

$$i_{g1}(t) = 2 \cos\left(t + \frac{\pi}{2}\right) \text{ A}$$

$$i_{g2}(t) = \cos\left(t - \frac{\pi}{2}\right) \text{ A}$$

$$R_1 = 1 \Omega$$

$$L_1 = 1 \text{ H}$$

$$\alpha = 2 \Omega$$

Result

$$i_x(t) = 2 \cos\left(t - \frac{\pi}{2}\right) \text{ A}$$

PROBLEM 3.7

Given the circuit in Figure 7:

- Determine the system of equations that allows to solve the circuit using the mesh analysis method.
- Determine the system of equations that allows to solve the circuit using the nodal analysis method.
- Solve the circuit using the equations obtained in a), and determine the voltage $v_x(t)$.
- Solve the circuit using the equations obtained in b), and determine the voltage $v_x(t)$.
- Do the expressions for $v_x(t)$ coincide independently of the method of analysis used to obtain them?
- Compute the power of the source $i_{g1}(t)$ and the power absorbed by L_1 and R_2 .

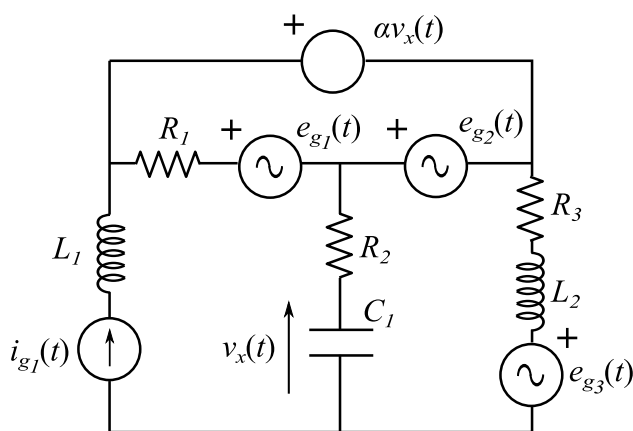


Figure 7

Data:

$$e_{g1}(t) = \sqrt{2} \cos\left(t - \frac{\pi}{4}\right) \text{ V}$$

$$e_{g2}(t) = \cos\left(t + \frac{\pi}{2}\right) \text{ V}$$

$$e_{g3}(t) = \cos\left(t - \frac{\pi}{2}\right) \text{ V}$$

$$i_{g1}(t) = \cos(t) \text{ A}$$

$$R_1 = 1 \Omega$$

$$R_2 = 1 \Omega$$

$$R_3 = 1 \Omega$$

$$C_1 = 1 \text{ F}$$

$$L_1 = 1 \text{ H}$$

$$L_2 = 1 \text{ H}$$

$$\alpha = 1$$

Result

$$v_x(t) = \frac{1}{\sqrt{2}} \cos\left(t - \frac{\pi}{4}\right) \text{ V}; \quad P_{I_{g1}} = \frac{3}{4} \text{ W}; \quad P_{Z_{L1}} = 0 \text{ W}; \quad P_{R2} = \frac{1}{4} \text{ W}$$

PROBLEM 3.8

Given the circuit in Figure 8:

- Determine the system of equations that allows to solve the circuit using the mesh analysis method.
- Determine the system of equations that allows to solve the circuit using the nodal analysis method.
- Solve the circuit using the equations obtained in a), and determine the difference of potentials between points A and B, V_{AB} .
- Solve the circuit using the equations obtained in b), and determine the difference of potentials between points A and B, V_{AB} .
- Do these difference of potentials coincide independently of the method of analysis used to compute them?
- Compute the power of the source βV_x and the power absorbed by the impedance Z_1 .

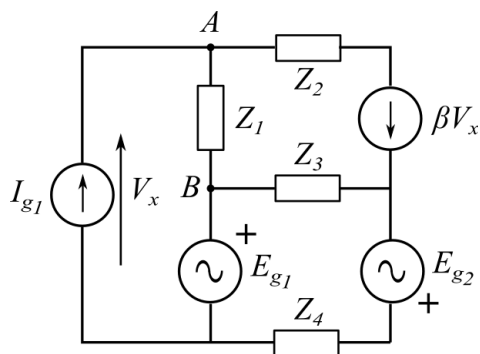


Figure 8

Data:

$$E_{g1} = 2 + 2j \text{ V}; \quad E_{g2} = -1 \text{ V}$$

$$I_{g1} = 2 + j \text{ A};$$

$$Z_1 = 2 \Omega; \quad Z_2 = 1 + j \Omega$$

$$Z_3 = 2 \Omega; \quad Z_4 = -2j \Omega$$

$$\beta = \frac{1}{2} \Omega^{-1}$$

Result

$$V_{AB} = 1 \text{ V}; \quad P_{\beta V_x} = \frac{17}{8} \text{ W}; \quad P_{Z_1} = \frac{1}{4} \text{ W}.$$

PROBLEM 3.9

Determine the Thevenin's equivalent source from terminals A and B for the circuit in Figure 9.

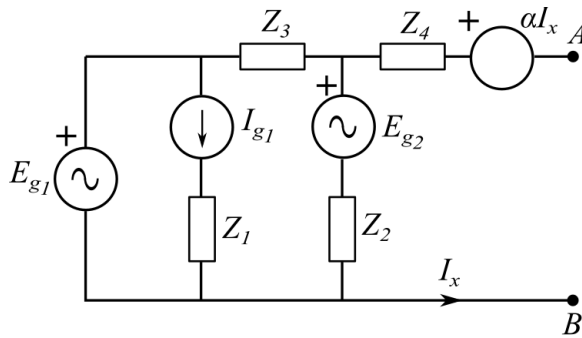


Figure 9

Data:

$$\begin{aligned} E_{g1} &= 4 + 3j \text{ V}; & E_{g2} &= 3 \text{ V} \\ I_{g1} &= 1 \text{ A}; \\ Z_1 &= 1 \Omega; & Z_2 &= 1 - j \Omega \\ Z_3 &= 1 + j \Omega; & Z_4 &= 1 + j \Omega \\ \alpha &= 1 \Omega \end{aligned}$$

Result

$$E_{Th} = 5 + j \text{ V}; \quad Z_{Th} = 1 + j \Omega$$

PROBLEM 3.10

Determine the Thevenin's equivalent source from terminals A and B for the circuit in Figure 10.

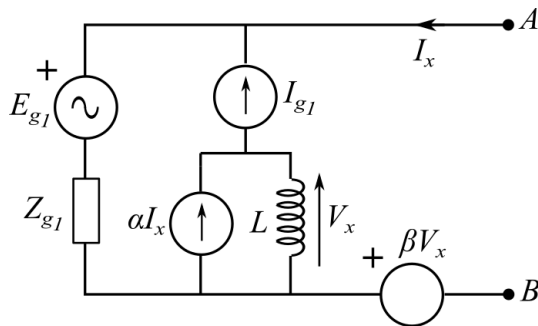


Figure 10

Data:

$$\begin{aligned} E_{g1} &= 10\sqrt{2} \cdot e^{-j\frac{\pi}{4}} \text{ V}; & I_{g1} &= \sqrt{2} \cdot e^{j\frac{\pi}{4}} \text{ A} \\ Z_{g1} &= 1 + j \Omega; & Z_L &= j \Omega \\ \alpha &= \frac{1}{2}; & \beta &= 2 \end{aligned}$$

Result

$$E_{Th} = 12 - 10j \text{ V}; \quad Z_{Th} = 1 + 2j \Omega$$

PROBLEM 3.11

Determine the Norton's equivalent source from terminals A and B for the circuit in Figure 11.

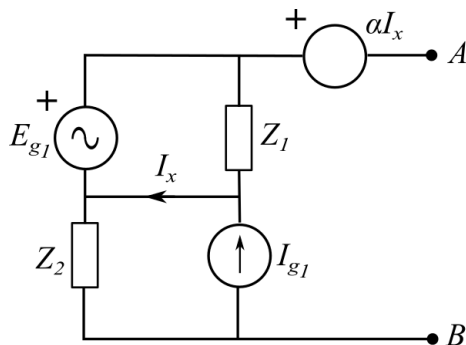


Figure 11

Data:

$$\begin{aligned} E_{g1} &= 2j \text{ V}; & I_{g1} &= 1 \text{ A} \\ Z_1 &= j \Omega; & Z_2 &= 2 - j \Omega \\ \alpha &= 1 \Omega \end{aligned}$$

Result

$$I_N = \frac{-3+j}{5} \text{ A}; \quad Z_N = 2 - j \Omega$$

PROBLEM 3.12

Determine the Thevenin's equivalent source from terminals A and B for the circuit in Figure 12.

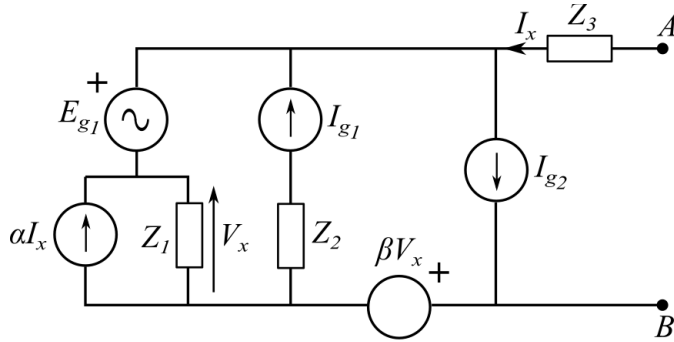


Figure 12

Data:

$$\begin{aligned} E_{g1} &= j \text{ V}; & I_{g1} &= 2 \text{ A}; \\ I_{g2} &= 1 \text{ A} & Z_1 &= \frac{1}{2}j \Omega; \\ Z_2 &= j \Omega; & Z_3 &= 2j \Omega \\ \alpha &= 1; & \beta &= 2 \end{aligned}$$

Result

$$E_{Th} = \frac{j}{2} \text{ V}; \quad Z_{Th} = j \Omega$$

PROBLEM 3.13

Determine the Norton's equivalent source from terminals A and B for the circuit in Figure 13.

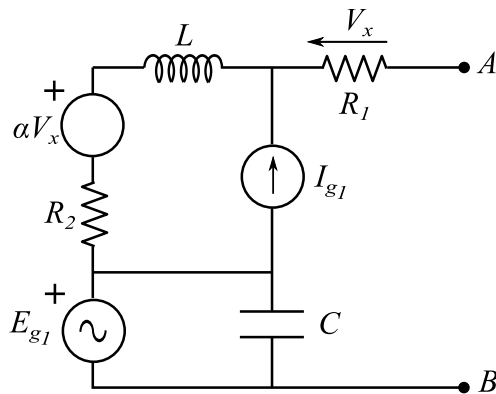


Figure 13

Data:

$$\begin{aligned} E_{g1} &= 2 \text{ V}; & I_{g1} &= 2 \text{ A} \\ R_1 &= 1 \Omega; & R_2 &= 1 \Omega \\ Z_L &= j \Omega; & \alpha &= 2 \\ Z_C &= -j \Omega; \end{aligned}$$

Result

$$I_N = 2 - 4j \text{ A}; \quad Z_N = j \Omega$$

PROBLEM 3.14

For the circuit in Figure 14:

- Determine the Norton's equivalent source from terminals A and B towards the left.
- Power absorbed by the load R_L .

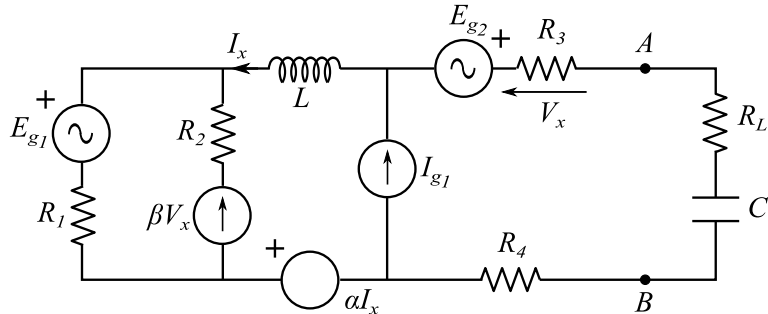


Figure 14

Data:

$$E_{g1} = 2 \text{ V}; \quad E_{g2} = 1 - j \text{ V} \quad I_{g1} = j \text{ A}; \quad R_L = 3 \Omega; \quad R_1 = R_2 = R_3 = R_4 = 1 \Omega;$$

$$Z_L = j \Omega; \quad Z_C = -j \Omega; \quad \alpha = 2 \Omega; \quad \beta = 2 \Omega^{-1}$$

Result

$$\text{a) } I_N = \frac{4 + 2j}{5} \text{ A}; \quad Z_N = (3 + j) \Omega.$$

$$\text{b) } P_{R_L} = \frac{1}{3} \text{ W}$$

PROBLEM 3.15

For the circuit in Figure 15:

- Determine the Thevenin's equivalent source from terminals A and B towards the left.
- Power absorbed by the load R_L .

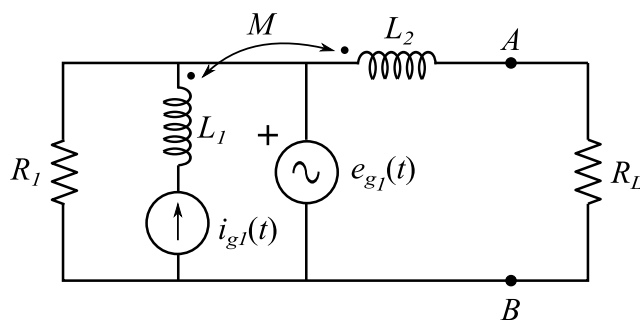


Figure 15

Data:

$$L_1 = 4 \text{ mH}; \quad L_2 = 9 \text{ mH};$$

$$R_L = 45 \Omega; \quad R_g = 200 \Omega;$$

$$k = \frac{1}{2}$$

$$i_{g1}(t) = 2 \cos\left(5 \cdot 10^3 t - \frac{\pi}{2}\right) \text{ A};$$

$$e_{g1}(t) = 50 \cos(5 \cdot 10^3 t) \text{ V}.$$

Result

a) $e_{Th}(t) = 80 \cos(5 \cdot 10^3 t) \text{ V}; \quad Z_{Th} = 45j \Omega$


b) $P_{R_L} = \frac{320}{9} \text{ W}$

PROBLEM 3.16

In the circuit shown in Figure 16 there is a perfect coupling between the two inductors.

a) Determine the Thevenin's equivalent source from terminals A and B towards the right.

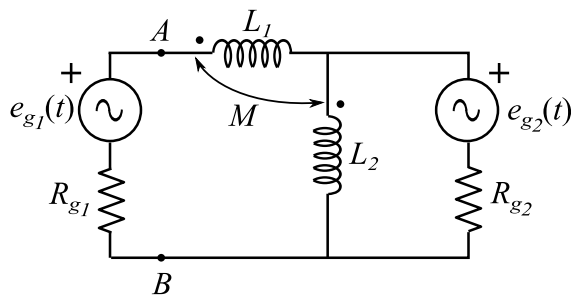b) Compute the power of the source $e_{g_1}(t)$.



Data:

$$e_{g_1}(t) = 2\sqrt{2} \sin\left(10^3 t + \frac{\pi}{4}\right) \text{ V};$$

$$e_{g_2}(t) = \sin(10^3 t) \text{ V};$$

$$R_{g_1} = 2 \Omega;$$

$$R_{g_2} = 1 \Omega;$$

$$L_1 = L_2 = 1 \text{ mH};$$

$$k = 1$$

Figure 16

Result

a) $e_{TH}(t) = \sqrt{2} \sin\left(10^3 t + \frac{\pi}{4}\right) \text{ V}; \quad Z_{TH} = 2 + 2j \Omega$

b) $P_{E_{g_1}} = \frac{4}{10} \text{ W}$