


# EXERCISES MODULE 4: THEOREMS OF LINEARITY AND TRANSFORMERS.

December 16, 2016

## PROBLEM 4.1

For the circuit in Figure 1:

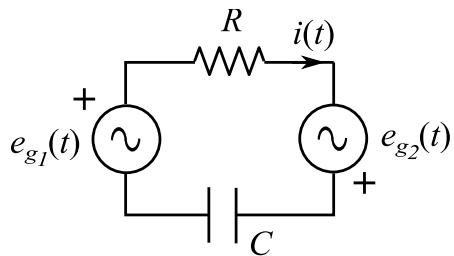- a) Obtain the value of current  $i(t)$ .
- b) Compute the power absorbed by resistor  $R$ .



**Data:**

$$e_{g_1}(t) = \sqrt{2} \sin\left(10^3 t + \frac{\pi}{4}\right) \text{ V}; \quad R = 1 \text{ k}\Omega$$

$$e_{g_2}(t) = \cos(2 \cdot 10^3 t) \text{ V}; \quad C = 1 \mu\text{F}$$

Figure 1

### Result


a)  $i(t) = \sin\left(10^3 t + \frac{\pi}{2}\right) + \frac{2}{\sqrt{5}} \cos(2 \cdot 10^3 t + 0,464) \text{ mA.}$

b)  $P_R = \frac{9}{10} \text{ mW}$

## PROBLEM 4.2

For the circuit in Figure 1:

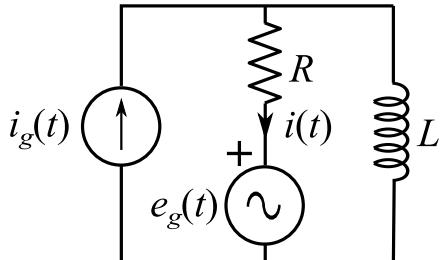- a) Obtain the value of current  $i(t)$ .
- b) Compute the power absorbed by resistor  $R$ .



**Data:**

$$e_g(t) = 5\sqrt{2} \sin\left(2 \cdot 10^6 t + \frac{\pi}{4}\right) \text{ V}; \quad R = 1 \text{ k}\Omega$$

$$i_g(t) = 5 \cos\left(\frac{1}{2} \cdot 10^6 t\right) \text{ mA}; \quad L = 1 \text{ mH}$$

Figure 1

### Result


a)  $i(t) = \sqrt{10} \sin(2 \cdot 10^6 t + 2,82) + \sqrt{5} \cos\left(\frac{1}{2} \cdot 10^6 t + 1,107\right) \text{ mA.}$

b)  $P_R = \frac{15}{2} \text{ mW}$

## PROBLEM 4.3

For the circuit in Figure 1:

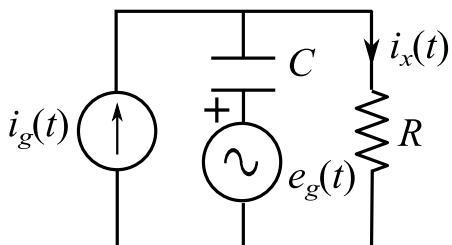- a) Obtain the current  $i_x(t)$ .
- b) Compute the power absorbed by resistor  $R$ .



**Data:**

$$i_g(t) = 5\sqrt{2} \sin\left(2 \cdot 10^3 t + \frac{\pi}{4}\right) \text{ mA}; \quad R = 2 \text{ k}\Omega$$

$$e_g(t) = \sqrt{2} \sin\left(10^3 t - \frac{\pi}{4}\right) \text{ V}; \quad C = \frac{1}{2} \mu\text{F}$$

Figure 1

### Result


a)  $i_x(t) = \sqrt{10} \sin(2 \cdot 10^3 t - 0.346) + \frac{1}{2} \sin(10^3 t) \text{ mA.}$

b)  $P_R = \frac{41}{4} \text{ mW}$
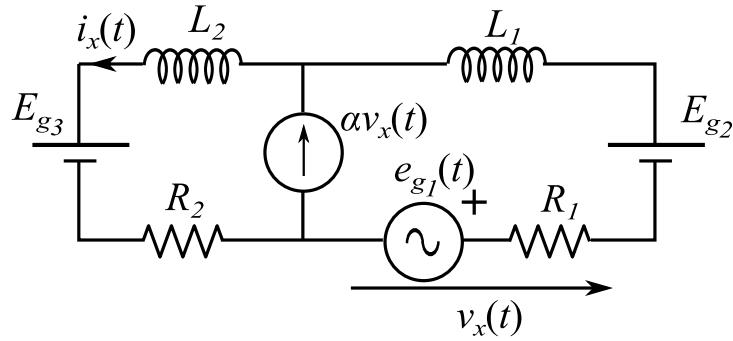
## PROBLEM 4.4

For the circuit in Figure 1:

- Obtain the expression for current  $i_x(t)$ .
- Compute the power of the sources  $\alpha v_x(t)$  and  $E_{g_3}$ , and the power absorbed by resistor  $R_2$ .
- Determine the new value of current  $i_x(t)$ , if we substitute the source  $e_{g_1}(t)$  for a different source  $e'_{g_1}(t) = 2\sqrt{2} \cos\left(10^6 t + \frac{\pi}{4}\right)$  V



**Data:**

Figure 1

$$\begin{aligned} R_1 &= 1 \text{ k}\Omega; & R_2 &= 2 \text{ k}\Omega; \\ L_1 &= 1 \text{ mH}; & L_2 &= 3 \text{ mH} \\ E_{g_2} &= 3 \text{ V}; & E_{g_3} &= 2 \text{ V} \\ \alpha &= 2 \text{ m}\Omega^{-1}; & e_{g_1}(t) &= 4\sqrt{2} \cos\left(10^6 t + \frac{\pi}{4}\right) \text{ V.} \end{aligned}$$

## Result

a)  $i_x(t) = 1 + 4\sqrt{2} \cos\left(10^6 t - \frac{3\pi}{4}\right)$  mA.

b)  $P_{\alpha V_x} = 136 \text{ mW}; \quad P_{E_{g_3}} = -2 \text{ mW}; \quad P_{R_2} = 34 \text{ mW}$

c)  $i'_x(t) = 1 + 2\sqrt{2} \cos\left(10^6 t - \frac{3\pi}{4}\right)$  mA.

## PROBLEM 4.5

For the circuit in Figure 1:

- Determine the expression of current  $i_1(t)$ .
- Compute the power for the sources  $\alpha i_x(t)$  and  $E_g$ , and the power absorbed by resistor  $R_2$ .
- If we substitute the source  $E_g$  for a novel source  $E'_g = 6 \text{ V}$ , obtain the new value of the power absorbed by resistor  $R_2$ .

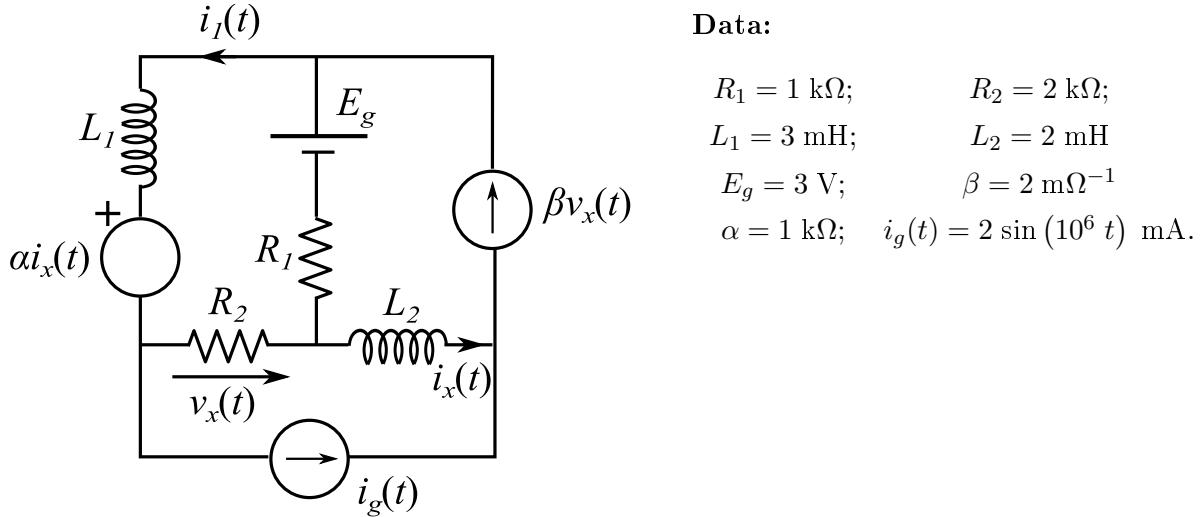


Figure 1

### Result

- $i_1(t) = 1 + \sqrt{2} \sin\left(10^6 t - \frac{\pi}{4}\right) \text{ mA.}$
- $P_{\alpha I_x} = 5 \text{ mW}; \quad P_{E_g} = 15 \text{ mW}; \quad P_{R_2} = 4 \text{ mW}$
- $P'_{R_2} = 10 \text{ mW}$

### PROBLEM 4.6

For the circuit in Figure 1:

- Obtain the expression of current  $i_1(t)$ .
- Determine the power of sources  $\alpha v_x(t)$ ,  $E_{g2}$  and  $e_{g1}(t)$ , and the power absorbed by resistor  $R$ . Verify the power balance principle.
- If we substitute source  $e_{g1}(t)$  for a new source  $e'_{g1}(t) = 4 \cos(10^6 t) \text{ V}$ , obtain the new power for the source  $\alpha v_x(t)$ .

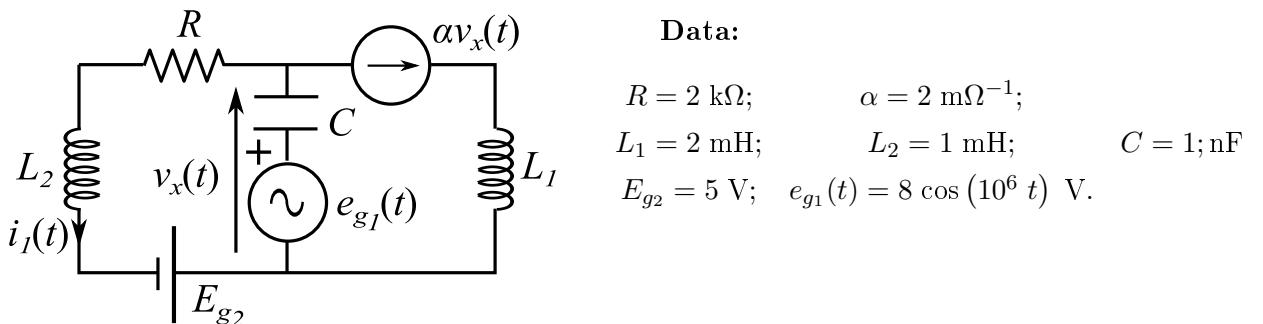


Figure 1

### Result

a)  $i_1(t) = 2 + \sqrt{2} \cos\left(10^6 t + \frac{\pi}{4}\right)$  mA.

b)  $P_{\alpha V_x} = -12$  mW;  $P_{E_{g2}} = 10$  mW;  $P_{e_{g1}(t)} = 12$  mW;  $P_{R_1} = 10$  mW

c)  $P'_{\alpha V_x} = -4.5$  mW

## PROBLEM 4.7

For the circuit in Figure 1:

a) Determine the current  $i_1(t)$ .

b) Compute the power of the source  $\alpha v_x(t)$ , and the power absorbed by resistor  $R_2$ .

c) If we substitute sources  $i_g(t)$ ,  $e_{g1}(t)$  and  $e_{g2}(t)$  for the following new sources:

$$\begin{cases} i'_g(t) = 2 \cos\left(10^6 t + \frac{\pi}{2}\right) \text{ mA;} \\ e'_{g1}(t) = 4 \cos\left(10^6 t\right) \text{ V;} \\ e'_{g2}(t) = 2 \cos\left(10^6 t\right) \text{ V} \end{cases}$$

Obtain the new value of the power of the dependent source  $\alpha v_x(t)$ .

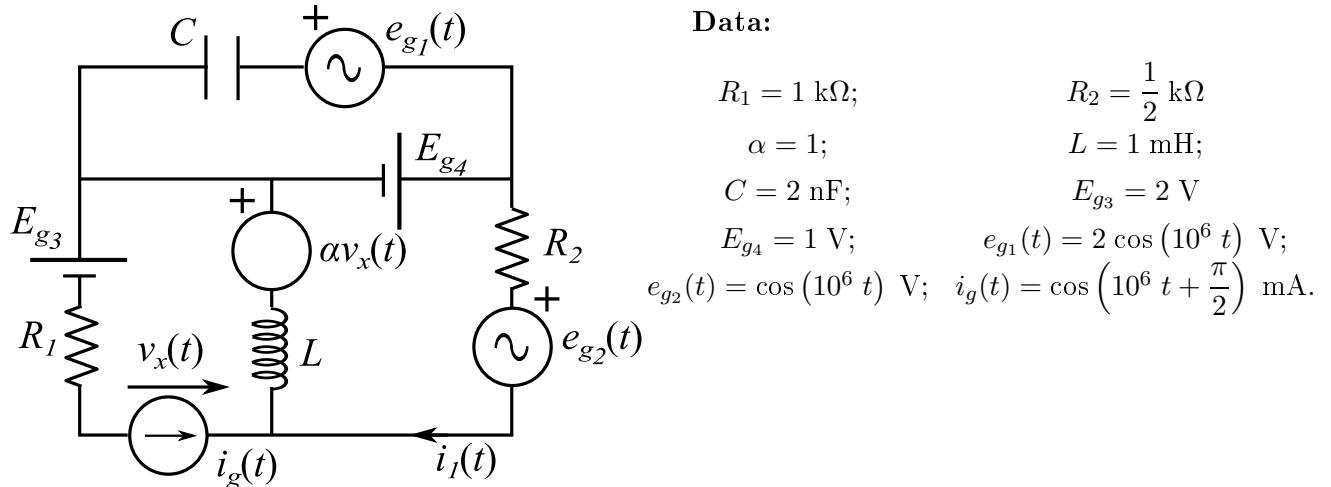


Figure 1

## Result

a)  $i_1(t) = 4 + \cos\left(10^6 t + \frac{\pi}{2}\right)$  mA.

b)  $P_{\alpha V_x} = 4.5$  mW;  $P_{R_2} = 8.25$  mW

c)  $P'_{\alpha V_x} = 6$  mW

## PROBLEM 4.8

For the circuit in Figure 1 obtain the power of sources  $e_g(t)$  and  $i(t)$ .

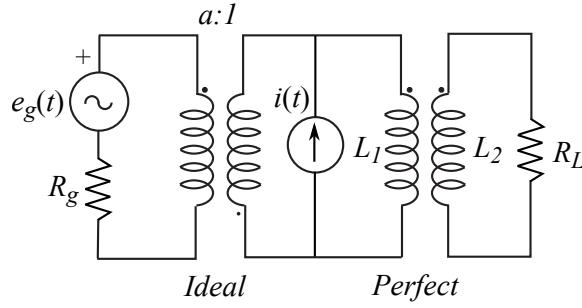


Figure 1

Data :  $e_g(t) = 4 \sin(\omega t)$  V ;  $i(t) = 2 \sin(\omega t)$  A ;  $R_g = 2 \Omega$  ;  $R_L = 2 \Omega$   
 $\omega L_1 = \frac{1}{4} \Omega$  ;  $\omega L_2 = 1 \Omega$  ;  $a = 2$

### Result

$$P_{E_g} = \frac{7}{2} W \text{ (delivered)}; \quad P_I = -\frac{1}{4} W \text{ (absorbed)}.$$

### PROBLEM 4.9

For the circuit in Figure 1, obtain the Thevenin's equivalent source from terminals A and B.

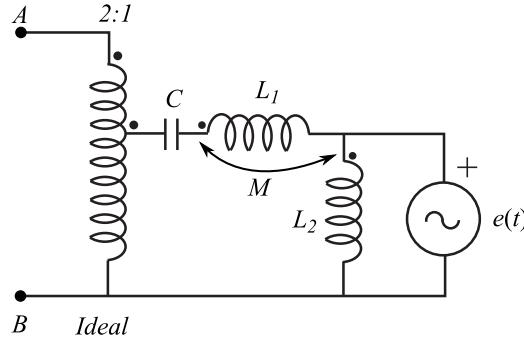


Figure 1

Data :  $e(t) = 3 \sin(t)$  V ;  $C = 4 F$  ;  $L_1 = 4 H$  ;  $L_2 = 1 H$  ;  $K = 0.5$

### Result

$$e_{Th}(t) = 12 \sin(t) \text{ V}; \quad Z_{Th} = 11j \Omega.$$

### PROBLEM 4.10

For the circuit in Figure 1:

- Obtain the Thevenin's equivalent source from terminals A – B towards the left.
- Determine the equivalent impedance ( $Z_s$ ) from terminals A – B towards the right .
- Obtain the power absorbed by resistor R.

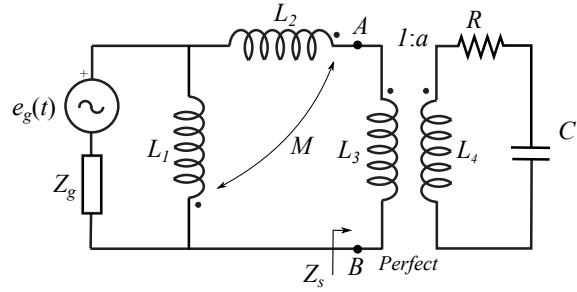


Figure 1

Data:

$$e_g(t) = 5 \sin(10^3 t) \text{ V}; \quad L_1 = L_2 = 2 \text{ mH}; \quad L_3 = 1 \text{ mH}; \quad a = \sqrt{10}$$

$$Z_g = (1 - 2j) \Omega; \quad k_{12} = \frac{1}{2}; \quad R = 1 \Omega; \quad C = \frac{1}{7} \text{ mF}$$

### Result

a)  $e_{Th}(t) = 5 \sin\left(10^3 t + \frac{\pi}{2}\right) \text{ V}; \quad Z_{Th} = (1 + 2j) \Omega.$

b)  $Z_s = (1 - 2j) \Omega.$

c)  $P_R = \frac{25}{8} \text{ W}$

### PROBLEM 4.11

For the circuit in Figure 1 we know that the coupling coefficient for  $L_p$  and  $L_s$  is  $k_{ps} = \frac{1}{\sqrt{2}}$ .

- a) Compute the equivalent impedance of the circuit from terminals  $C - D$  towards the right.
- b) Obtain the Thevenin's equivalent source from terminals  $A - B$  towards the right.
- c) Determine the power absorbed by sources  $e(t)$  and  $i(t)$ .

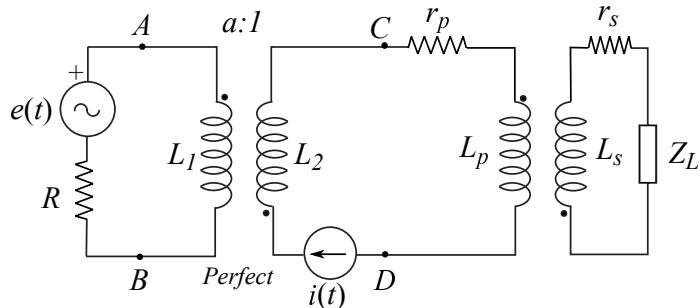


Figure 1

Data:

$$e(t) = 4 \cos(\omega t) \text{ V}; \quad \omega L_1 = 2 \Omega; \quad \omega L_2 = 8 \Omega; \quad \omega L_p = \omega L_s = 2 \Omega; \quad Z_L = -2j \Omega$$

$$i(t) = 4 \cos\left(\omega t - \frac{\pi}{2}\right) \text{ A}; \quad r_p = 1 \Omega; \quad r_s = 2 \Omega; \quad R = 2 \Omega$$

### Result

- a)  $Z_{CD} = (2 + 2j) \Omega$ .  
 b)  $e_{Th}(t) = 16 \cdot \cos(\omega t) \text{ V}$ ,  $Z_{Th} = 2j \Omega$ .  
 c)  $P_E = -6 \text{ W}$ ,  $P_I = 40 \text{ W}$ .

## PROBLEM 4.12

Obtain the Thevenin's equivalent source  $(e_{Th}(t), Z_{Th})$  from terminals  $A - B$  for the circuit shown in Figure 1.

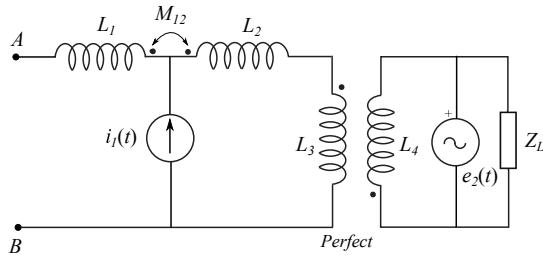


Figure 1

Data:  
 $i(t) = \sin(10^6 t) \text{ A}$ ;  $e(t) = 2 \sin(10^6 t) \text{ V}$ ;  $L_1 = 1 \mu\text{H}$ ;  $L_2 = 4 \mu\text{H}$   
 $L_3 = 4 \mu\text{H}$ ;  $L_4 = 1 \mu\text{H}$ ;  $k_{12} = \frac{1}{2}$ ;  $Z_L = 100 \Omega$

## Result

$$e_{Th}(t) = 5 \sin(10^6 t + 2.4981) \text{ V}; \quad Z_{Th} = 3j \Omega.$$

## PROBLEM 4.13

For the circuit shown in Figure 1:

- a) Determine the equivalent impedance from terminals  $AB$  towards the right,  $Z_{AB}$ .  
 b) Obtain the time-domain expression for the current passing through resistor  $R_2$ ,  $i(t)$ .

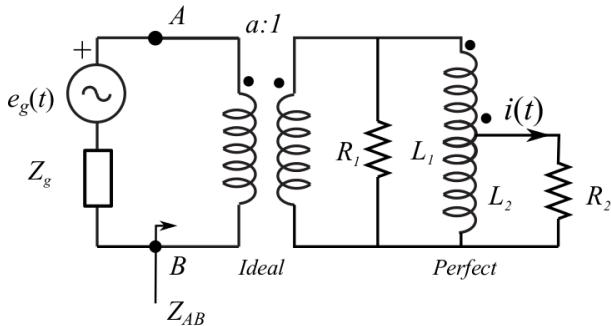


Figure 1

**Data:**

$$e_g(t) = 12 \cos(10^3 t) \text{ V}; \quad Z_g = 9 + 9j \Omega; \quad L_1 = \frac{9}{2} \text{ mH}; \quad L_2 = \frac{1}{2} \text{ mH}$$

$$a = 2 \quad R_1 = 9 \Omega; \quad R_2 = 1 \Omega$$

## Result

a)  $Z_{AB} = 9(1 + j) \Omega$ .

b)  $i(t) = \cos(10^3 t) \text{ A}$

## PROBLEM 4.14

For the circuit shown in Figure 1, obtain the power of the source  $e_g(t)$ .

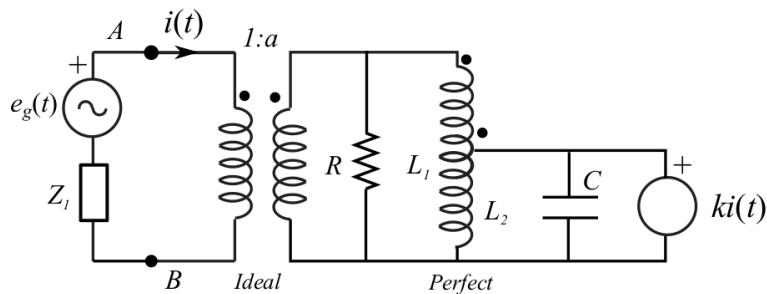


Figure 1

### Data:

$$e_g(t) = 12 \cos(10^6 t) \text{ V}; \quad Z_1 = 6(1 - 2j) \Omega; \quad C = 7 \mu\text{F}; \quad L_1 = 3 \mu\text{H};$$

$$L_2 = \frac{1}{3} \mu\text{H}; \quad a = 2; \quad k = 4 \Omega; \quad R = 9 \Omega.$$

## Result

$$P_{E_g} = 3 \text{ W}$$